

# Network Theorems

---

- ILOs – Day7
  - State and explain DC network theorems
    - Norton's theorem
    - Maximum power transfer theorem

# Network Theorems

---

- **Norton's theorem**
- Maximum power transfer theorem

# Norton's Theorem

---

- Used for solution of complicated circuits
- It allows to replace a complicated circuit with a simple equivalent circuit containing only a **single current source in parallel with a single resistor**

# Norton's Theorem


---

- *The Theorem states that:*
- Any linear, bilateral, active network **between two terminals** can be replaced by an equivalent circuit consisting of a single current source (**called the Norton's current source,  $I_N$** ) in parallel with a single resistance (**called the Norton's resistance,  $R_N$** ).
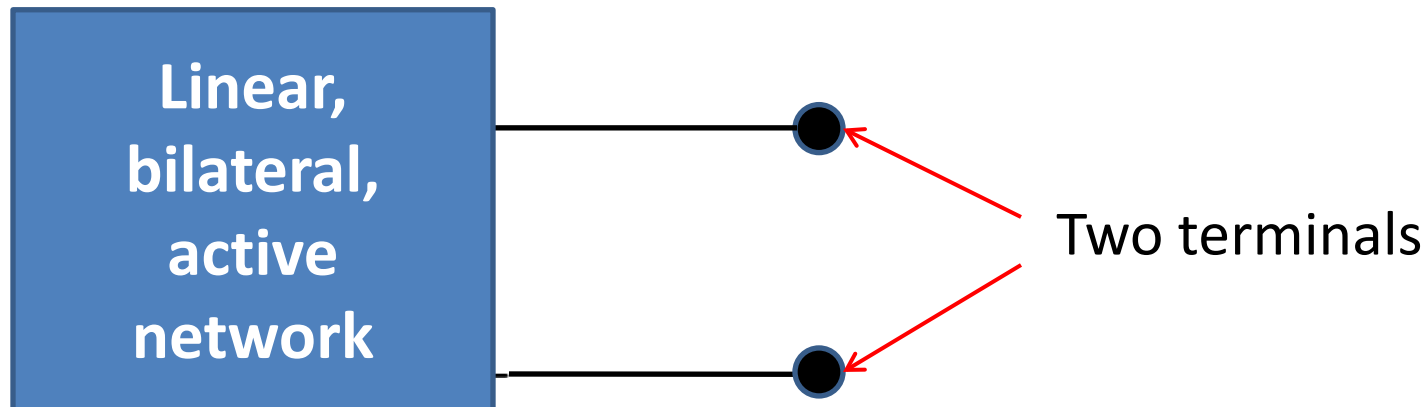
# Norton's Theorem




---

- *The Theorem states that:*
- Any linear, bilateral, active network
- **Between two terminals**
- Can be replaced by an equivalent circuit consisting of
- A single current source (**called the Norton's current source,  $I_N$** )
- In parallel with a single resistance (**called the Norton's resistance,  $R_N$** ).




# Norton's Theorem


---

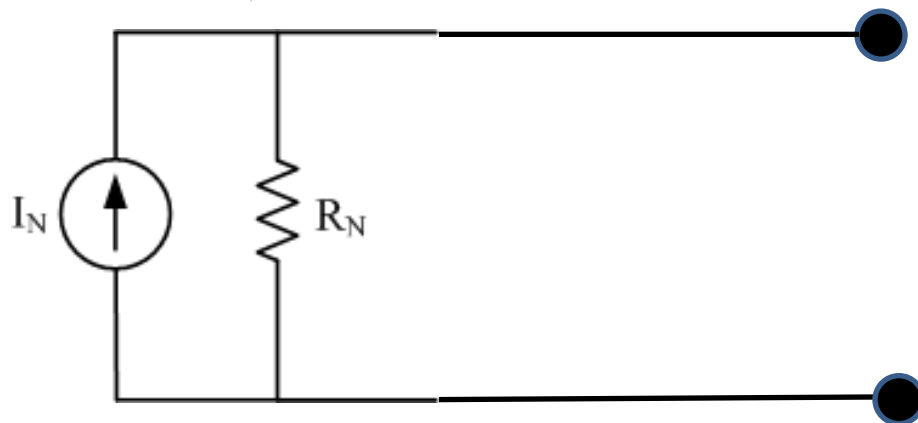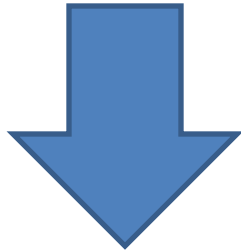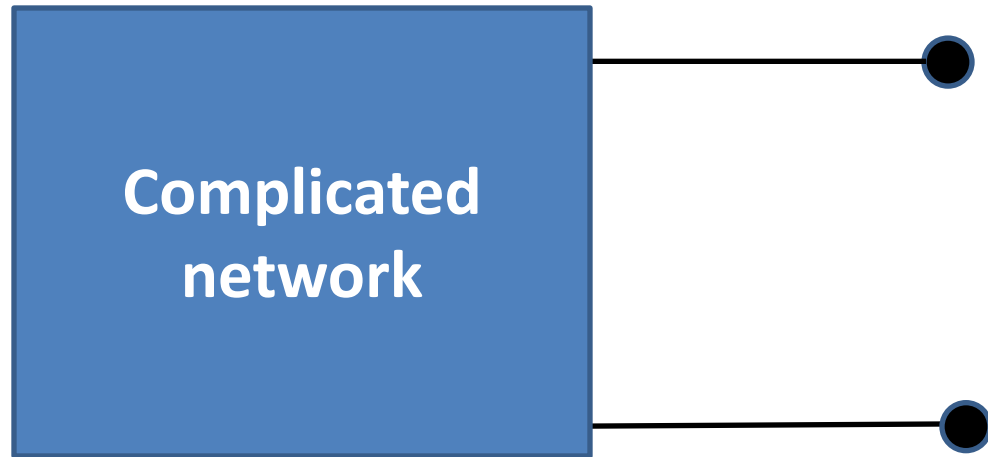

# Norton's Theorem- $I_N$

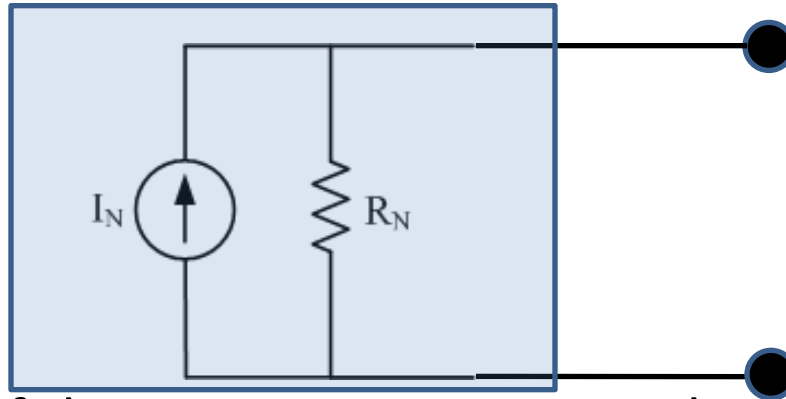

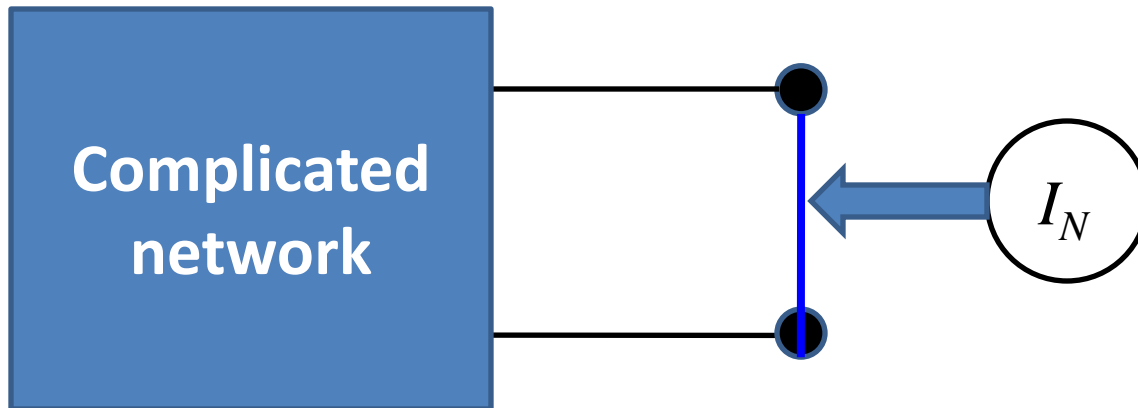
- Value of this current source  $I_N$  is obtained as the short circuit current between these two terminals.
- Make the two terminals **SHORTED**
- Measure the current through it using an ammeter


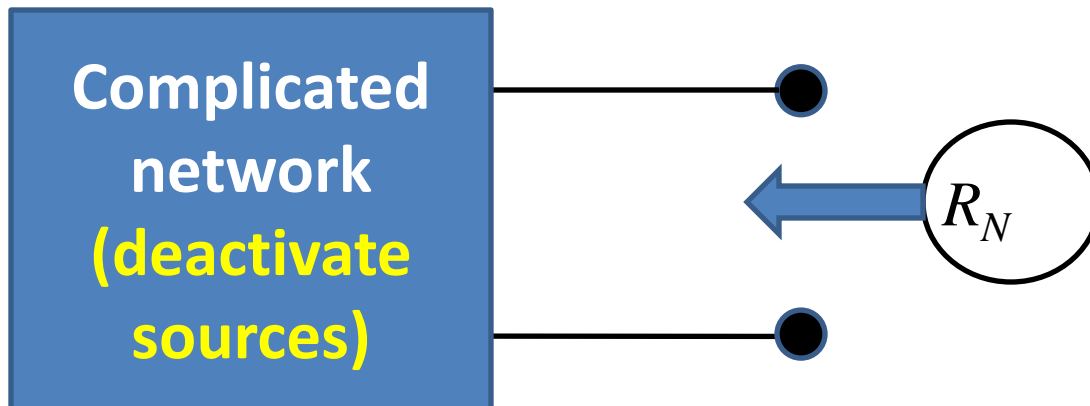
# Norton's Theorem- $R_N$

---

- The Norton's resistance  $R_N$  is calculated as
- The **equivalent resistance of the network measured between the two open circuited terminals**
- By deactivating all sources in the circuit.





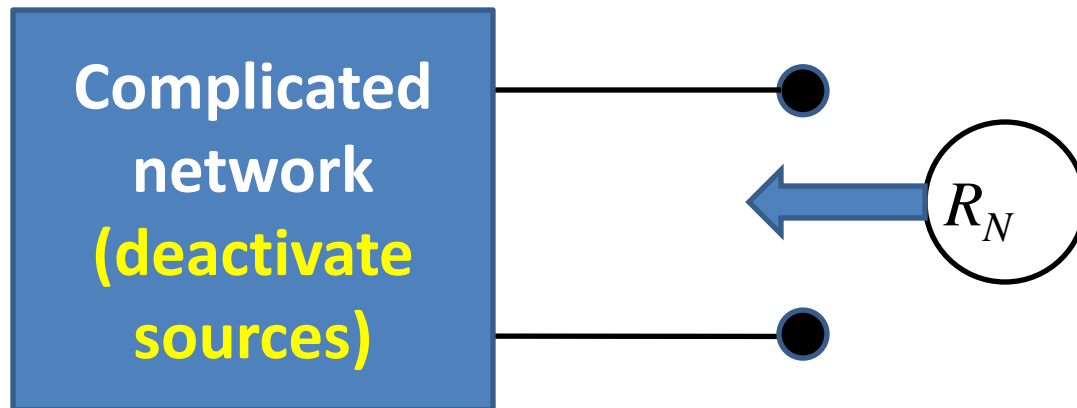
# Norton's Theorem- $R_N$


---

- To make a voltage source inactive, it must be replaced by its internal resistance (**short circuit for an ideal voltage source**)
- To make a current source inactive, it must be replaced by its internal resistance (**open-circuited for an ideal current source**)




Practically, the definition of  $R_{Th}$  and  $R_N$  are the same. Thus for a given circuit, the values of  $R_{Th}$  and  $R_N$  are same.
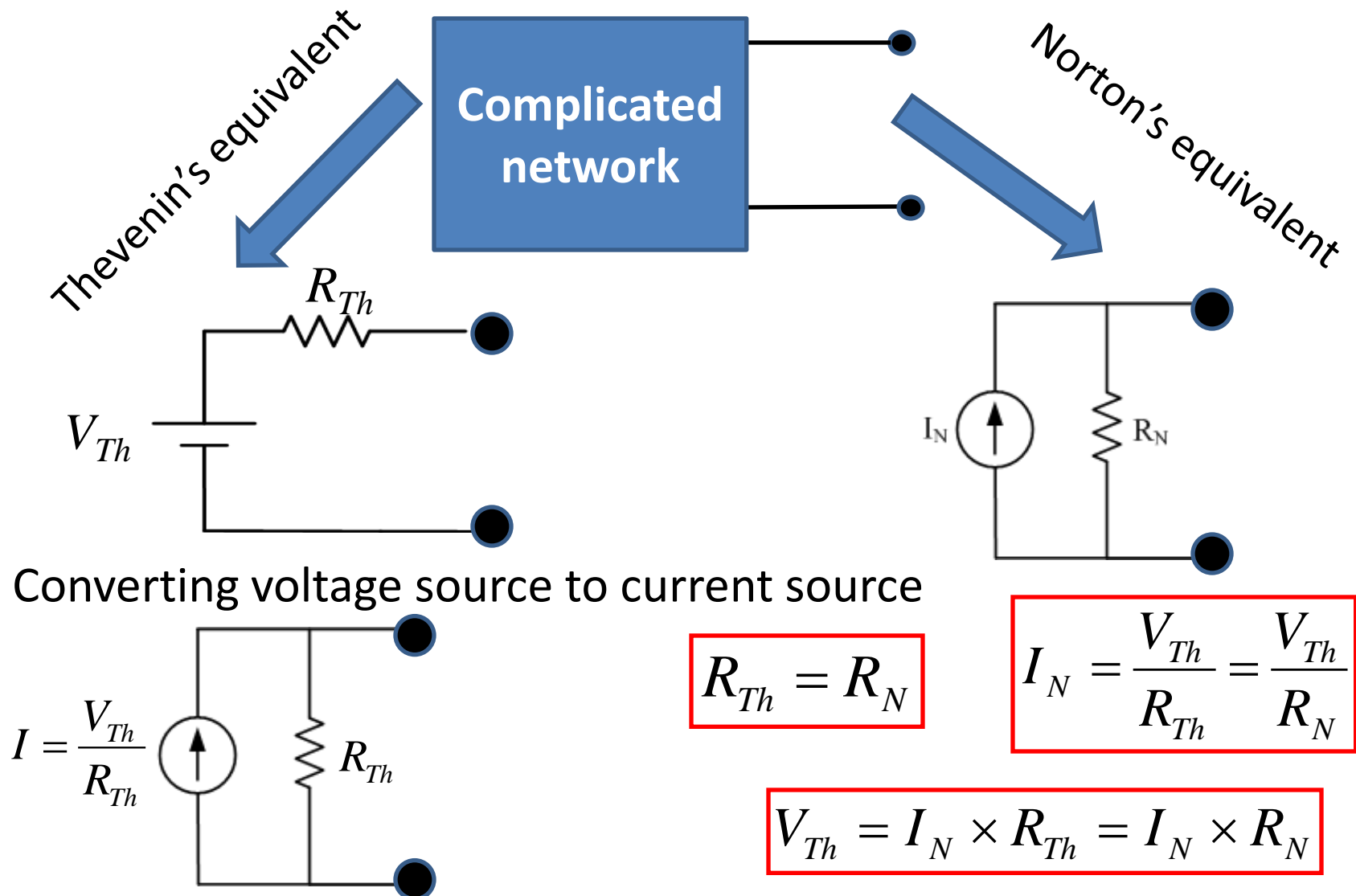
# Relationships between Thevenin's and Norton's equivalent parameters




# Find current through the load resistance of  $2.5\ \Omega$  using Norton's theorem.

---

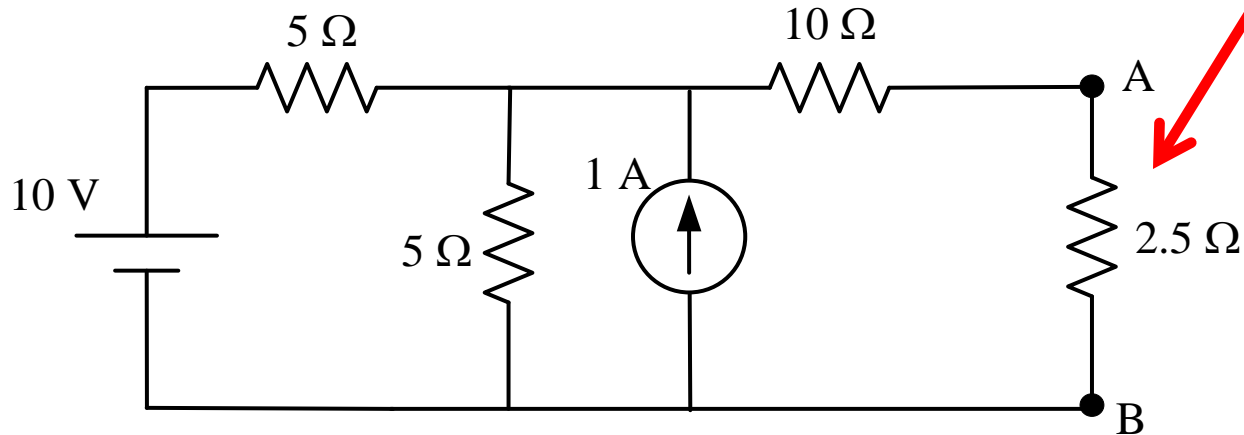
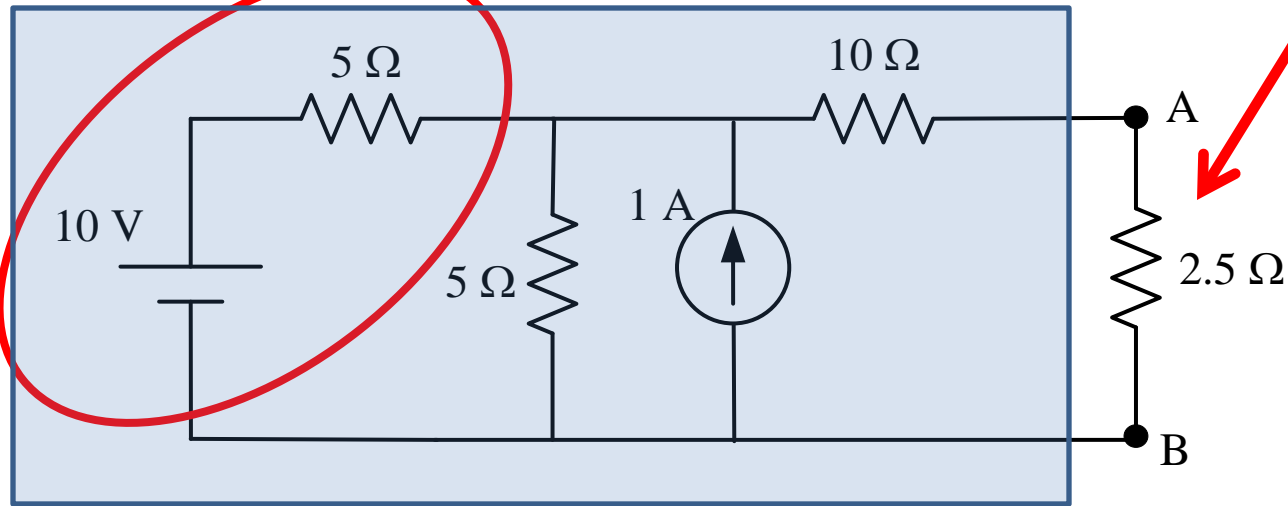
# Find current through the load resistance of  $2.5\ \Omega$  using Norton's theorem.




- We are to find out the Norton's equivalent circuit of the network across the  $2.5\ \Omega$  resistance (i.e. between the terminals A and B).

**Step 1:**

Convert the  $10\text{ V}$  source with  $5\ \Omega$  series resistance into an equivalent current source in parallel with the resistance  $5\ \Omega$ :


# Find current through the load resistance of  $2.5\ \Omega$  using Norton's theorem.

---

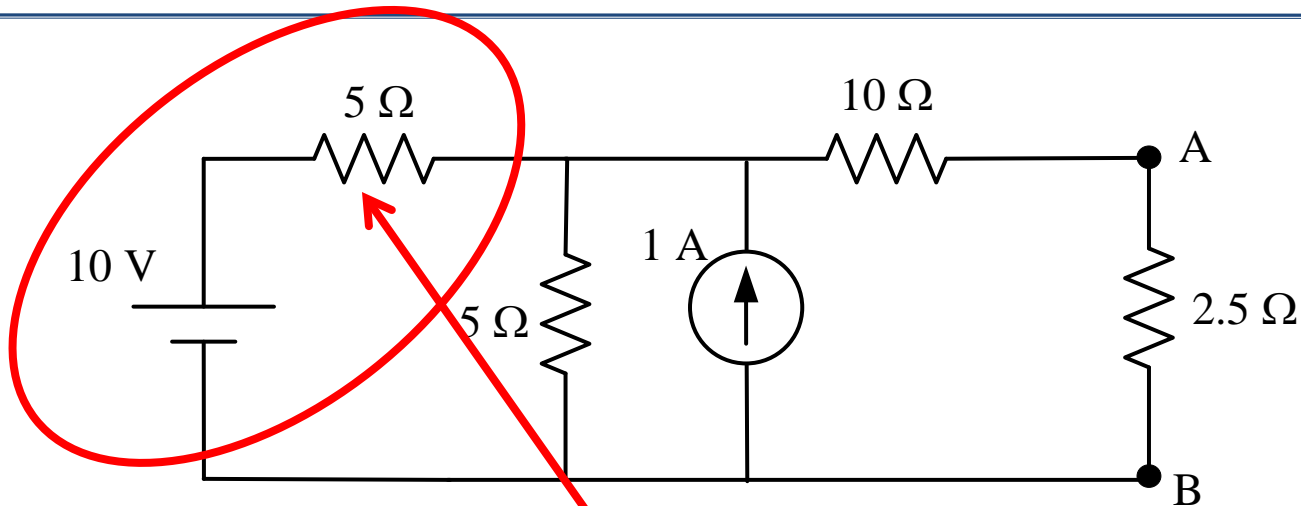


Value of the equivalent current source:  $I = \frac{V}{R} = \frac{10}{5} = 2\text{ A}$

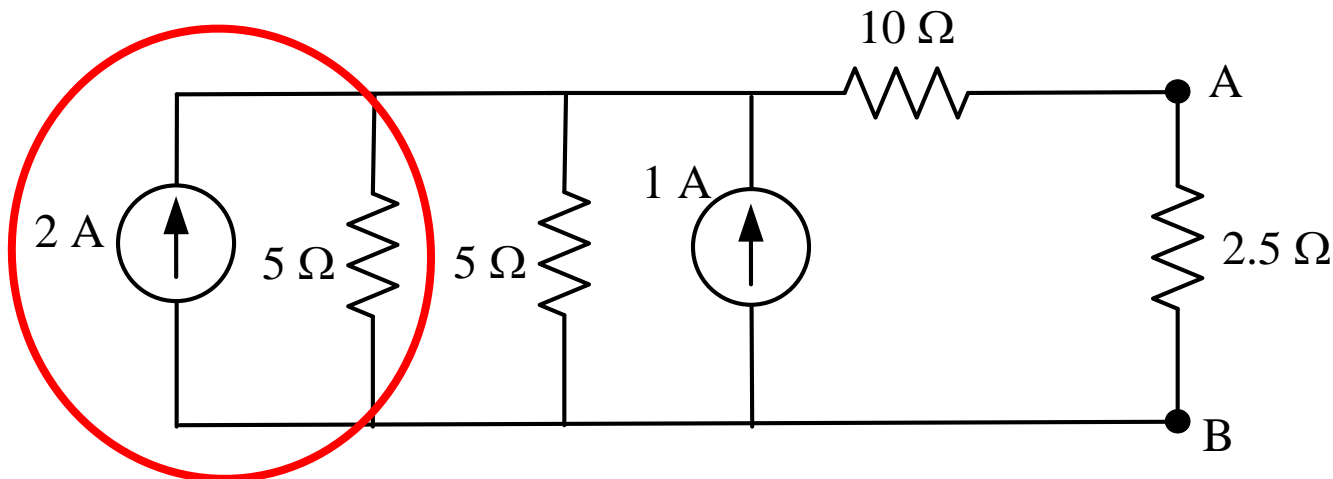In parallel with the same resistance  $5\ \Omega$




# Find current through the load resistance of  $2.5\ \Omega$  using Norton's theorem.

---

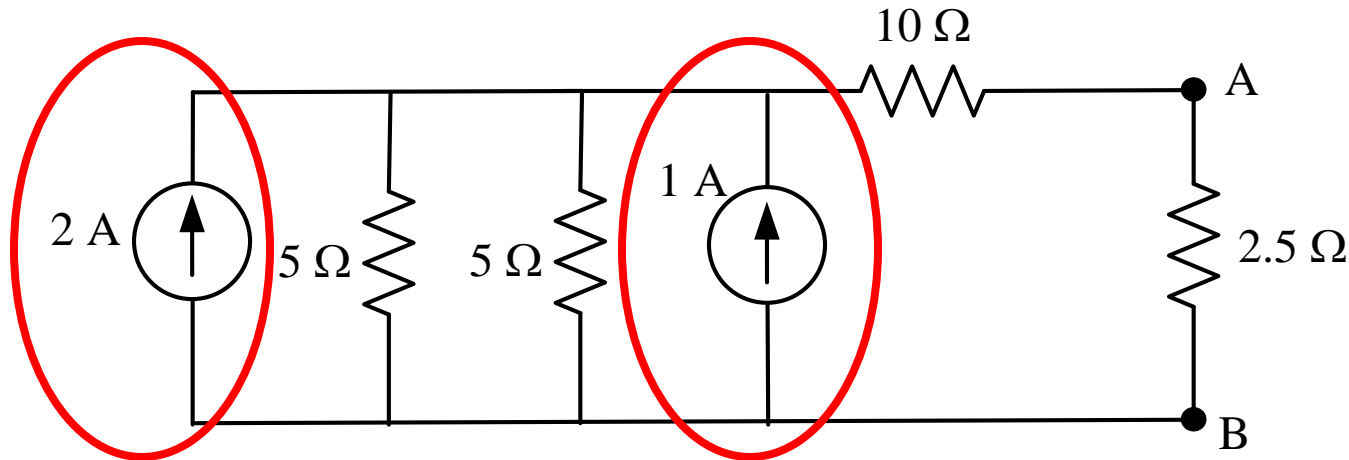


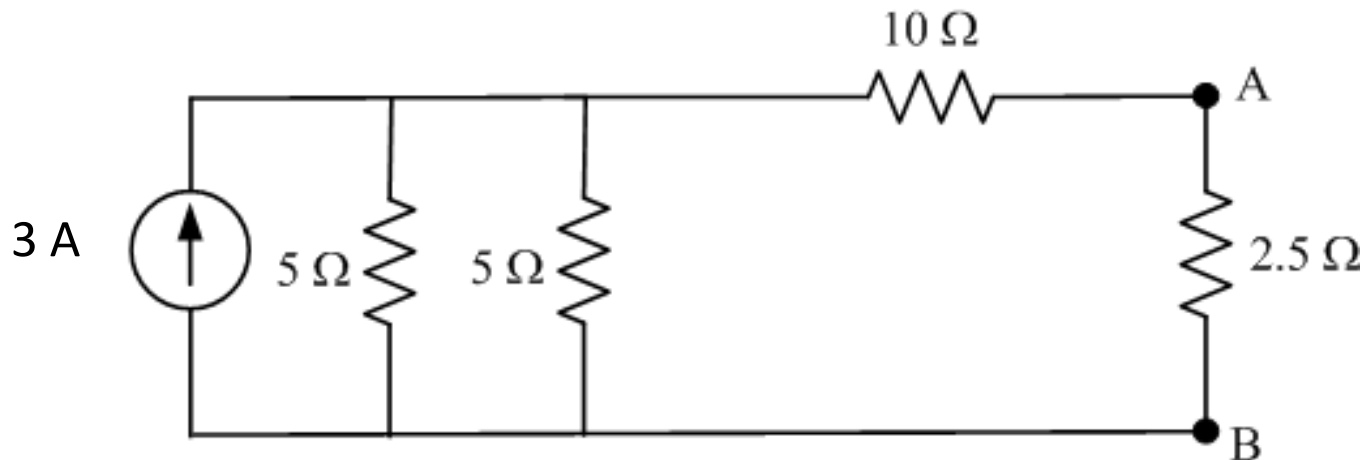The two current sources,  $2\text{ A}$  and  $1\text{ A}$  are in parallel, so they can be added up to make a single current source of value  $2 + 1 = 3\text{ A}$ .




# Find current through the load resistance of  $2.5\ \Omega$  using Norton's theorem.

---

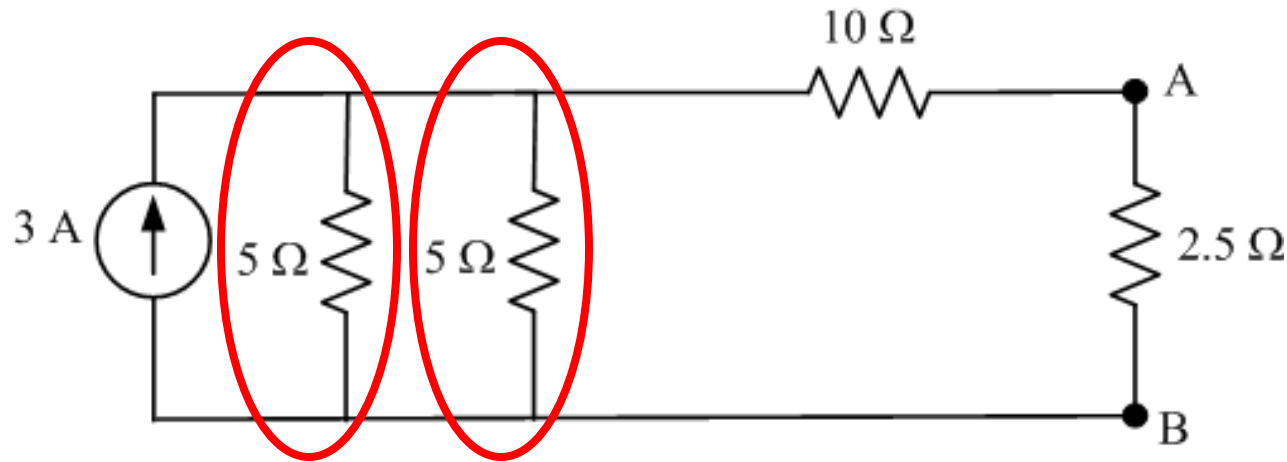


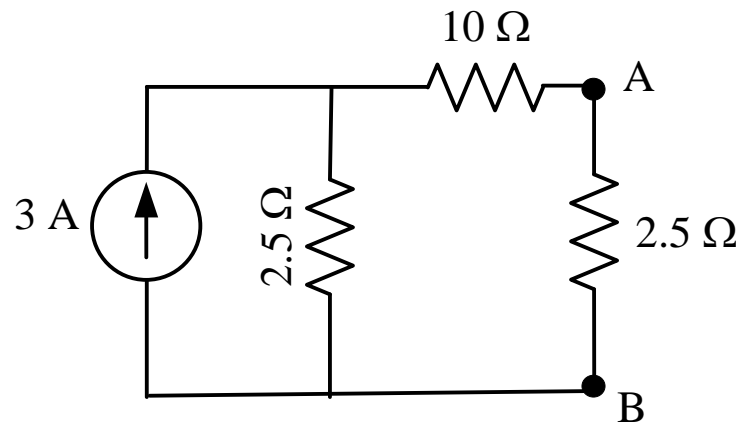The two  $5\ \Omega$  resistances in parallel can be combined into a single resistance of value  $2.5\ \Omega$ :




# Find current through the load resistance of  $2.5\ \Omega$  using Norton's theorem.

---

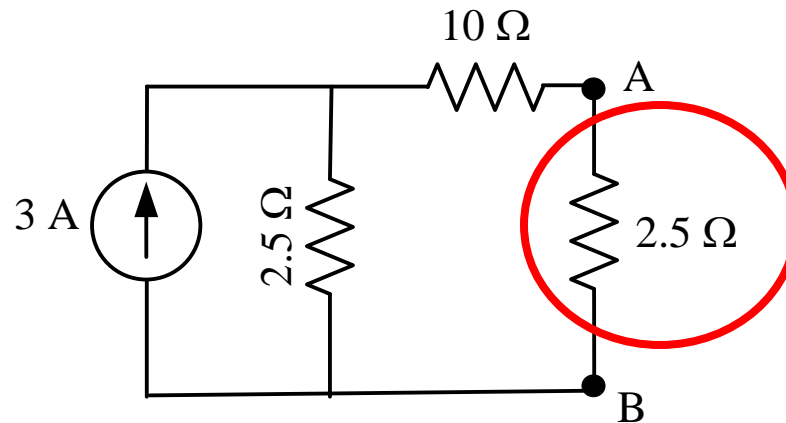

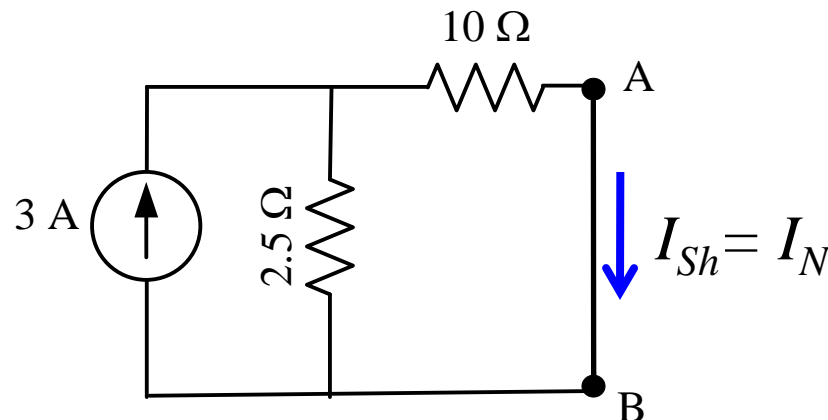
To find the Norton's current, remove the  $2.5\ \Omega$  resistance and short circuit the terminals A-B. Then find out current through the shorted path A-B:





# Find current through the load resistance of  $2.5\ \Omega$  using Norton's theorem.

---

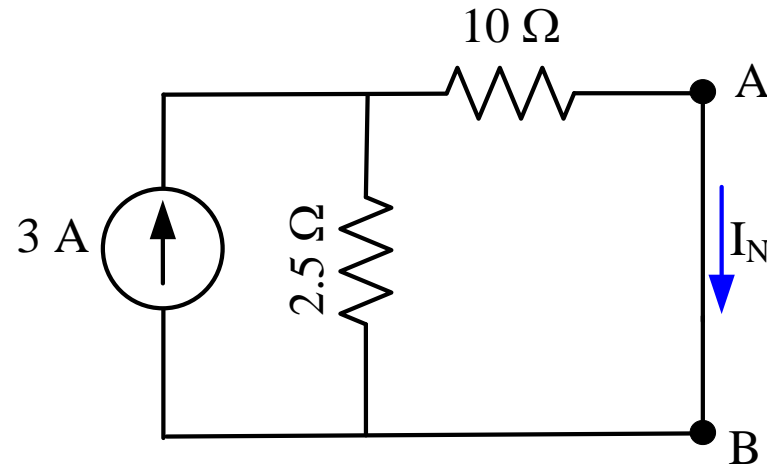

Use current division rule to find out current through the shorted path A-B:


$$I_N = I_{Sh} = 3 \times \frac{2.5}{2.5 + 10} = 3 \times \frac{2.5}{12.5} = 0.6\ A$$

## # Find current through the load resistance of $2.5\ \Omega$ using Norton's theorem.

---

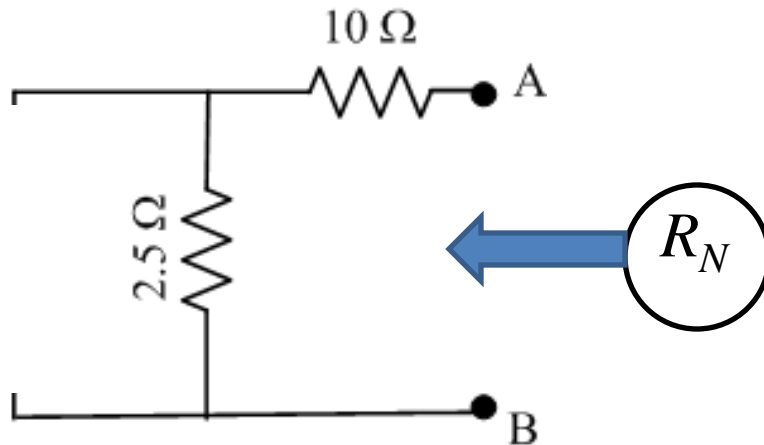
### Step 2: Calculate $R_N$

- To calculate  $R_N$  we keep the terminals A and B open circuited
- Replace the 3 A current source by open circuit and
- Calculate the equivalent resistance of the circuit between the two points A and B:



# Find current through the load resistance of  $2.5\ \Omega$  using Norton's theorem.

---

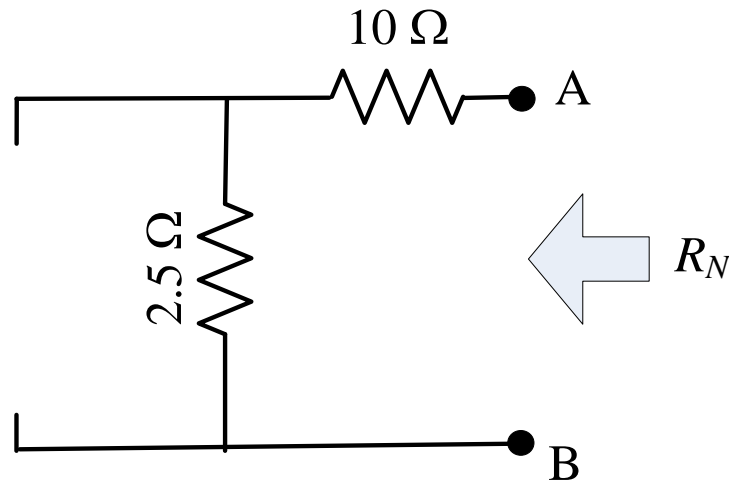

Between A-B, the two resistances 10 and 2.5 are in series:


$$\therefore R_N = R_{AB} = 2.5 + 10 = 12.5\ \Omega$$

# # Find current through the load resistance of $2.5\ \Omega$ using Norton's theorem

$$I_N = 0.6\text{ A}$$


$$R_N = 12.5\ \Omega$$

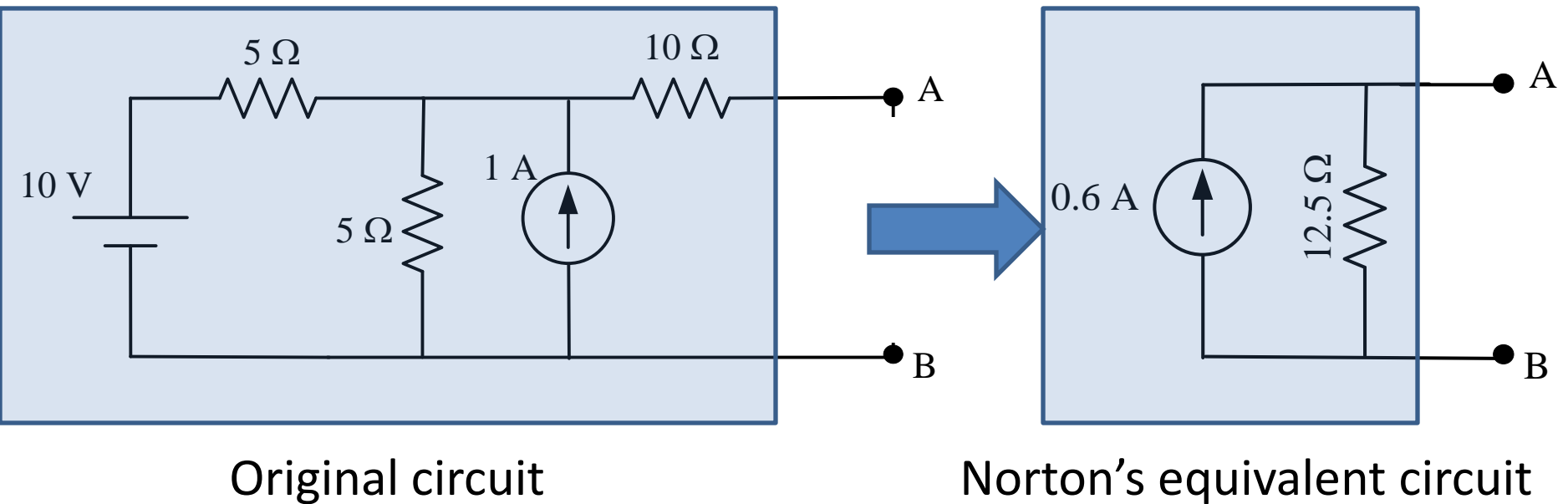The Norton's equivalent circuit that can be drawn between terminals A and B is thus:


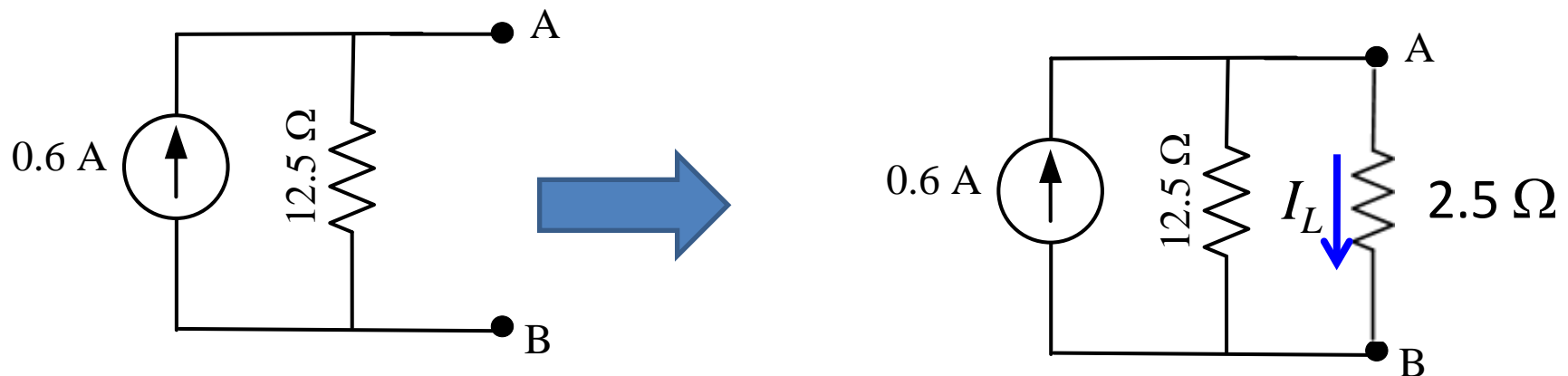
## # Find current through the load resistance of $2.5\ \Omega$ using Norton's theorem

To calculate the load current through the  $2.5\ \Omega$  resistance, connect it back between the output terminals A-B so that the total circuit becomes:



$\therefore$  The current ( $I_L$ ) through the load resistance  $2.5\ \Omega$  is:

$$I_L = I_{AB} = 0.6 \times \frac{12.5}{12.5 + 2.5} = 0.6 \times \frac{12.5}{15} = 0.5\text{ A}$$

# Network Theorems

---

- Norton's theorem
- **Maximum power transfer theorem**

# Maximum Power Transfer Theorem

---

This theorem is used to find the value of load resistance in a circuit for which there would be maximum amount of power transfer from source to the load.

# Maximum Power Transfer Theorem

---


- *The Theorem states that:*
- A resistive load, being connected to a DC network, receives maximum power when the load resistance is equal to the internal resistance of the source network as seen from the load terminals.


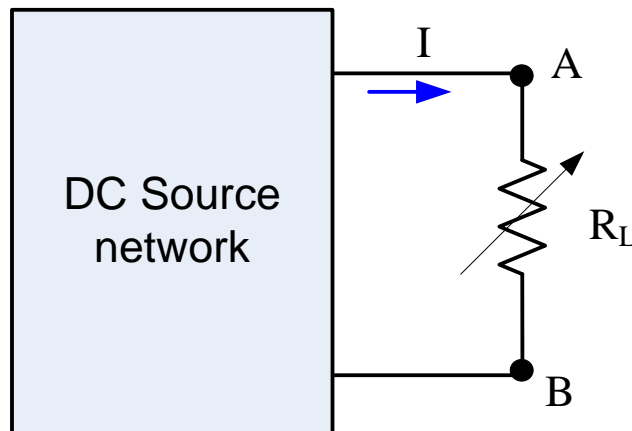
# Maximum Power Transfer Theorem

---


- *The Theorem states that:*
- A resistive load ( $R_L$ )
- Connected to a DC network (source network)
- Will receive maximum power from the source network
- When the load resistance is equal to
- The internal resistance of the source network


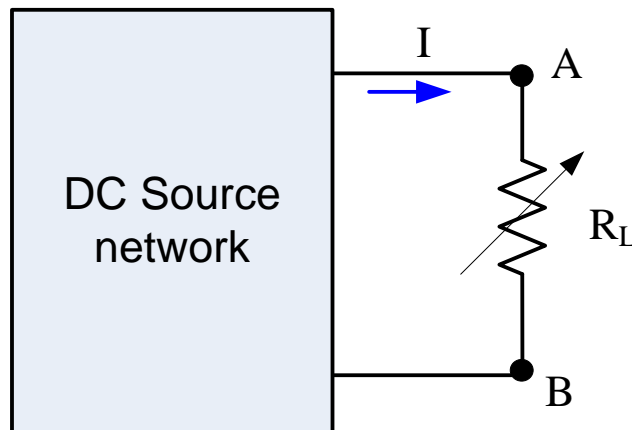
# Maximum Power Transfer Theorem

---


- *The Theorem states that:*
- A resistive load ( $R_L$ )
- Connected to a DC network (source network)
- Will receive maximum power from the source network
- When the load resistance is equal to
- The internal resistance of the source network


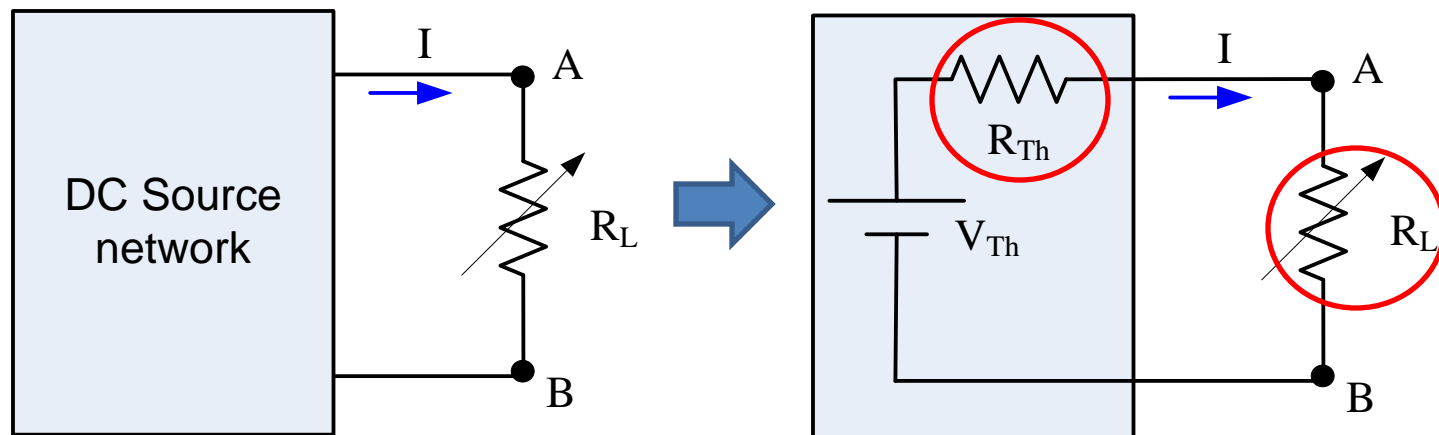
# Maximum Power Transfer Theorem

- When the load resistance is equal to
- The internal resistance of the source network

*Internal resistance of the source network is nothing but its Thevenin's equivalent resistance between the terminals A- B*



*For maximum power transfer,  $R_L = R_{Th}$*


# Maximum Power Transfer Theorem

---

*Proof:*

In the circuit:

$$I = \frac{V_{Th}}{R_{Th} + R_L}$$

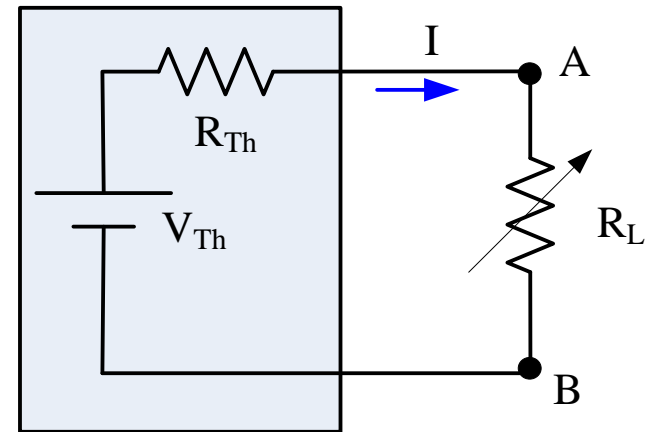

Power received by the load resistance is:

$$P_L = I^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

For maximum power transfer to load, we set:

$$\frac{dP_L}{dR_L} = 0$$

# Maximum Power Transfer Theorem

---

$$\frac{dP_L}{dR_L} = 0$$

$$\frac{dP_L}{dR_L} = \frac{d}{dR_L} \left[ \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L \right] = 0$$

$$V_{Th}^2 \frac{[(R_{Th} + R_L)^2 \times 1 - 2(R_{Th} + R_L)R_L]}{(R_{Th} + R_L)^4} = 0$$

$$R_{Th}^2 + R_L^2 + 2R_{Th}R_L - 2R_{Th}R_L - 2R_L^2 = 0$$

$$R_L^2 = R_{Th}^2$$

$$R_L = R_{Th}$$

Thus, it can be proved that power transfer from a DC source network to a resistive load is maximum when the load resistance is equal to the internal resistance of the DC source network.

# Maximum Power Transfer Theorem

Value of this maximum power can be calculated (with  $R_L = R_{Th}$ ) as:


$$P_{L\max} = P_L|_{R_L=R_{Th}} = I^2 R_L$$

$$P_{L\max} = I^2 R_{Th}$$

$$P_{L\max} = \left( \frac{V_{Th}}{R_{Th} + R_{Th}} \right)^2 R_{Th}$$

$$P_{L\max} = \left( \frac{V_{Th}}{2R_{Th}} \right)^2 R_{Th}$$

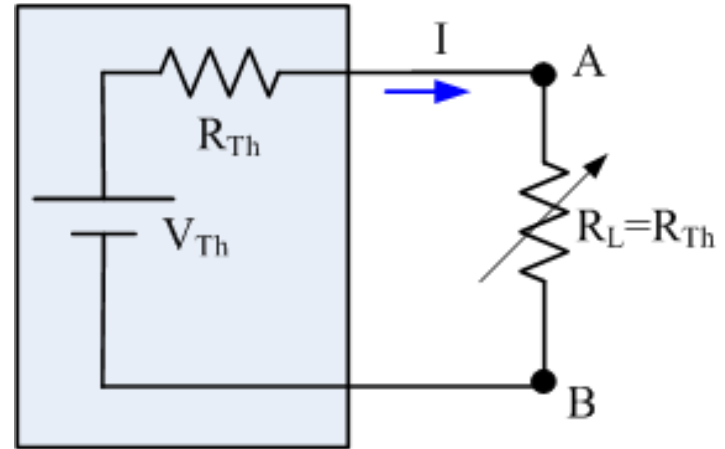
$$P_{L\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{V_{Th}^2}{4R_L}$$


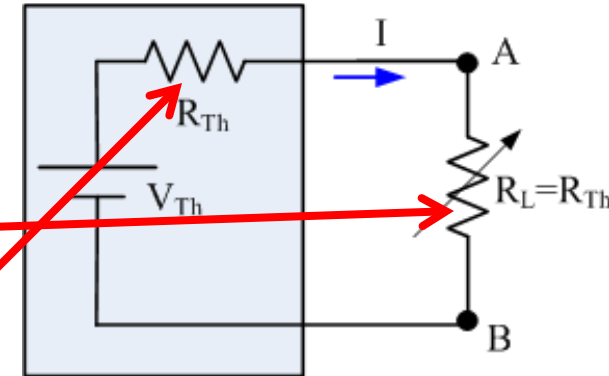
# Maximum Power Transfer Theorem

$$P_{L\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{V_{Th}^2}{4R_L}$$

- Note that this power is consumed by the load.
- In fact this same power is consumed by the internal resistance ( $R_{Th}$ ) of the source also.
- Thus, total power delivered by the source is:




$$P_T = \frac{V_{Th}^2}{4R_{Th}} + \frac{V_{Th}^2}{4R_{Th}} = \frac{V_{Th}^2}{2R_{Th}}$$

Thus, during maximum power transfer condition, the efficiency of power transfer becomes:

$$\eta = \frac{P_{L\max}}{P_T} \times 100\% = \frac{\frac{V_{Th}^2}{4R_L}}{\frac{V_{Th}^2}{2R_L}} \times 100\% = 50\%$$


# In the following circuit, find the value of  $R$  to obtain maximum power in it. Also calculate value of the maximum power.

---

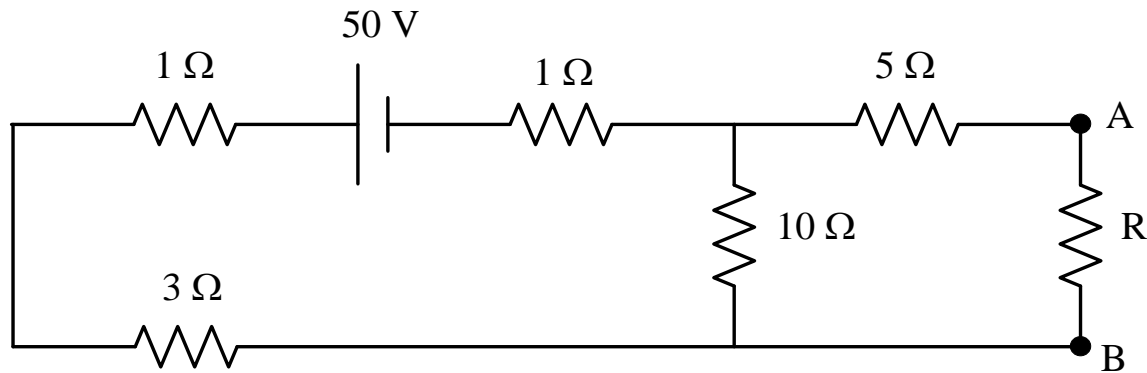



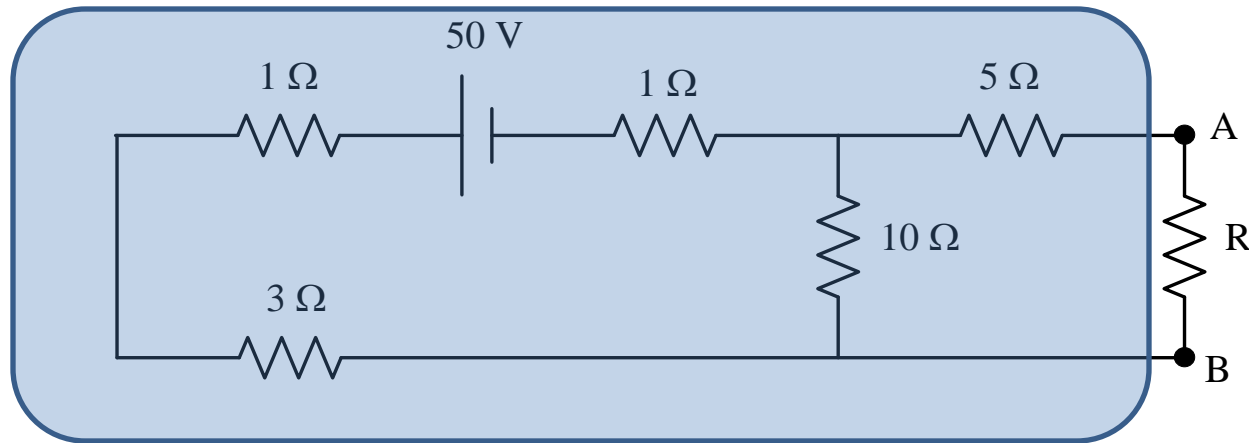
# In the following circuit, find the value of  $R$  to obtain maximum power in it. Also calculate value of the maximum power.




To calculate the value of load resistance  $R$  for obtaining maximum power in it, we need to convert the remaining part of the circuit, i.e. the circuit at the left hand side of the terminals A-B into its equivalent Thevenin's network.

# In the following circuit, find the value of  $R$  to obtain maximum power in it. Also calculate value of the maximum power.

---

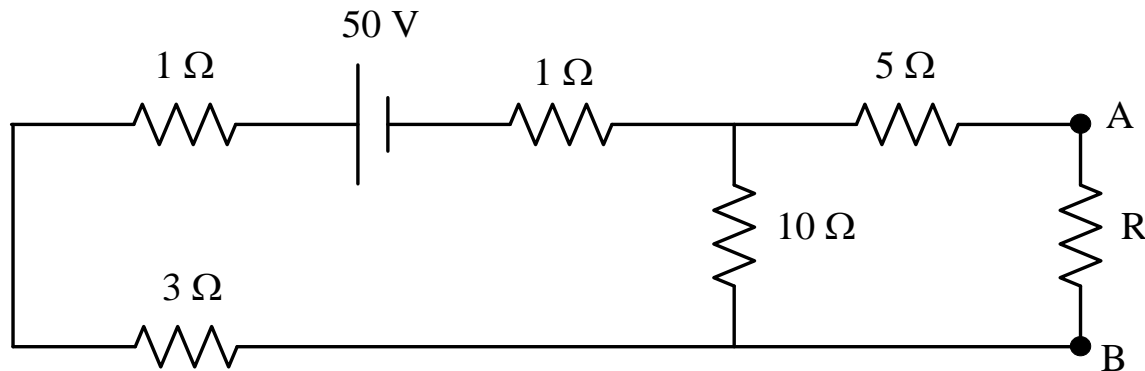

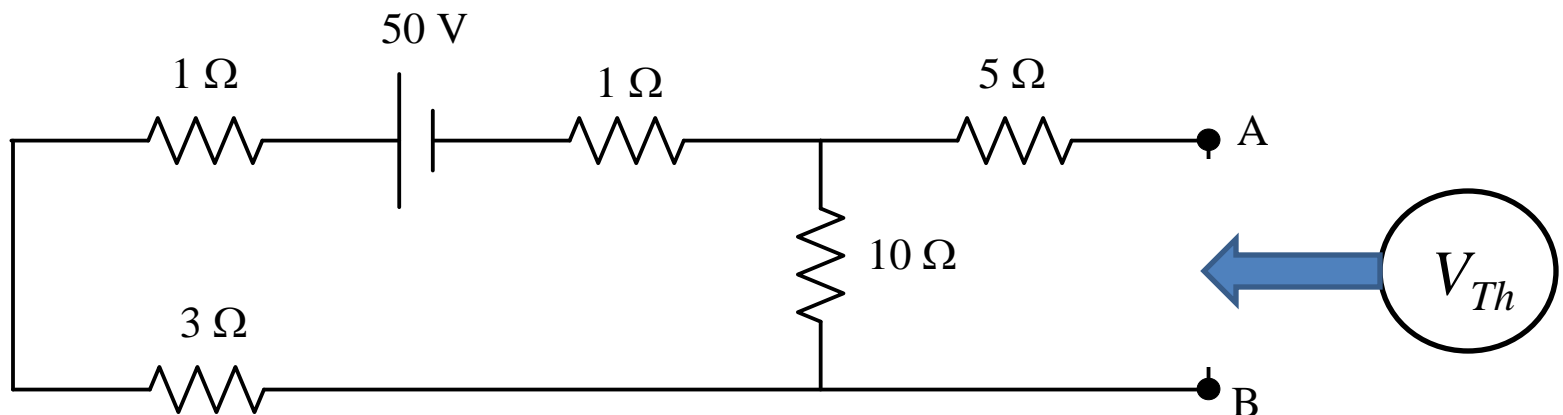
- Step 1: Calculate  $V_{Th}$
- Open circuit the terminals A-B and calculate the voltage across it:


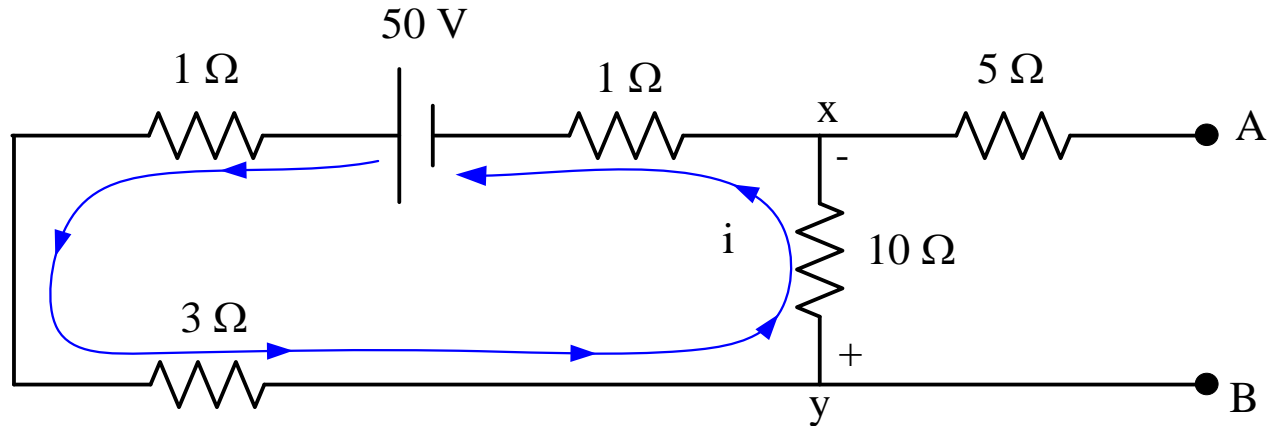
# In the following circuit, find the value of  $R$  to obtain maximum power in it. Also calculate value of the maximum power.

---

- Take the current  $i$  in the loop as shown:




- Since A-B is open, thus no current will flow to the output
- Thus, no voltage will be dropped in the  $5\Omega$  resistance
- Hence  $V_{xy} = V_{AB}$

$$V_{Th} = V_{AB} = V_{xy} = 10 \times (-i) = -10 \times \frac{50}{1+3+10+1} = -10 \times \frac{50}{15} = -\frac{100}{3} V$$
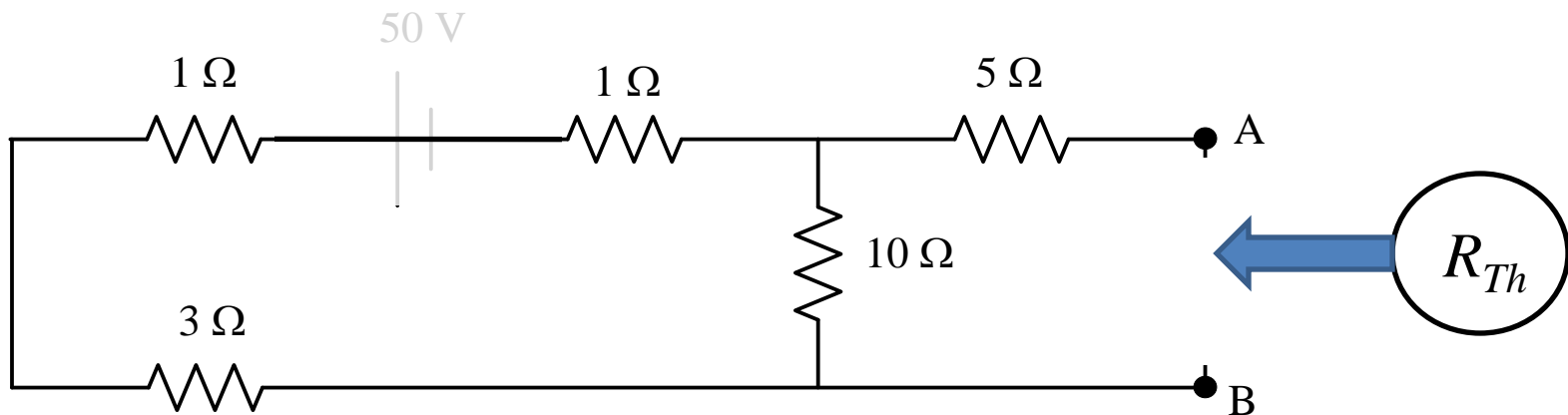
# In the following circuit, find the value of  $R$  to obtain maximum power in it. Also calculate value of the maximum power.


---

- Step 2: Calculate  $R_{Th}$
- Open circuit the terminals A-B
- Short the 50 V source and
- Calculate the equivalent resistance between terminals A-B:


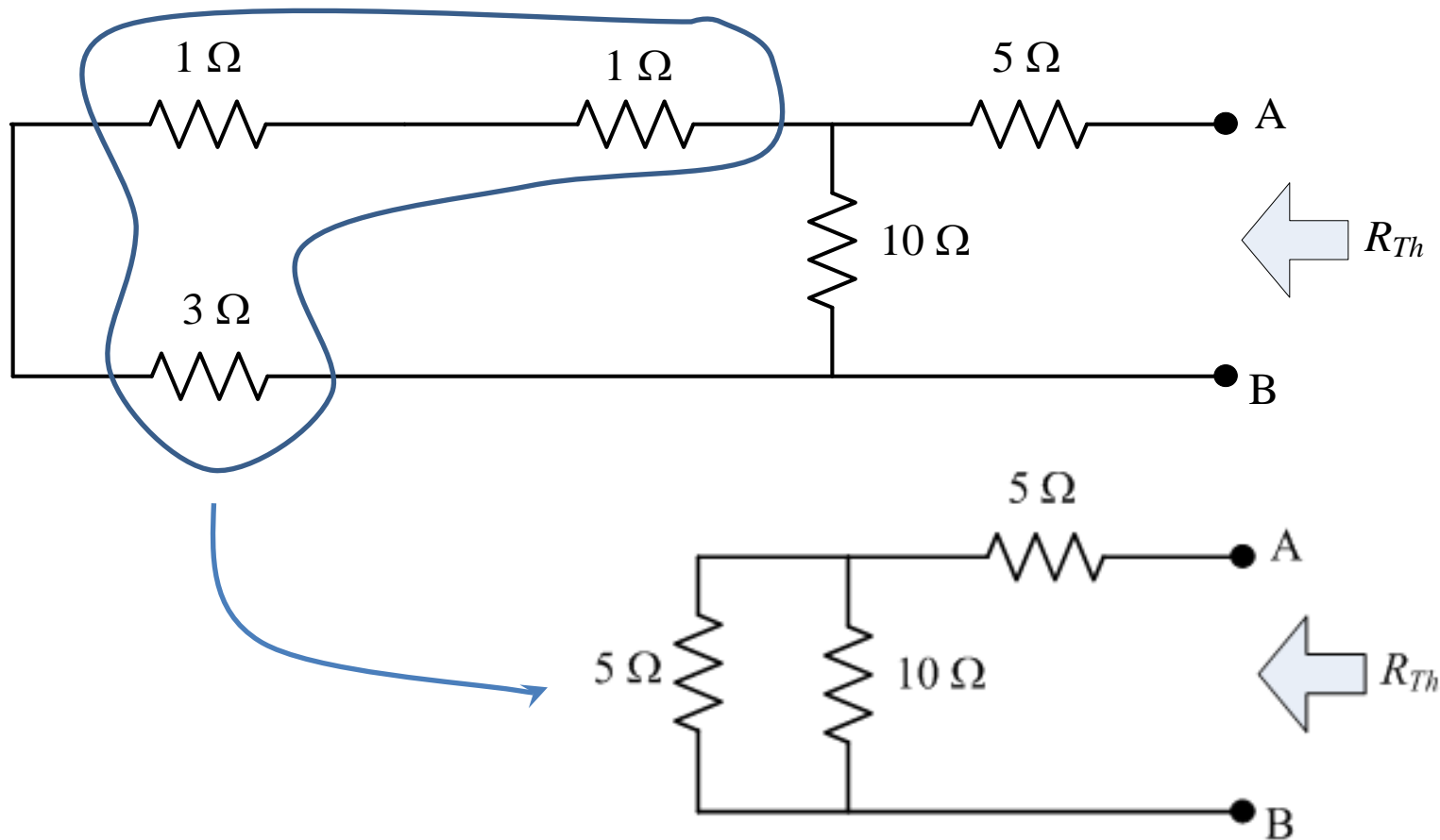
# In the following circuit, find the value of  $R$  to obtain maximum power in it. Also calculate value of the maximum power.


- Calculate  $R_{Th}$
- $1\ \Omega$ ,  $1\ \Omega$ , and  $3\ \Omega$  are in series ( $3 + 1 + 1 = 5$ )




# In the following circuit, find the value of  $R$  to obtain maximum power in it. Also calculate value of the maximum power.

---

- Calculate  $R_{Th}$

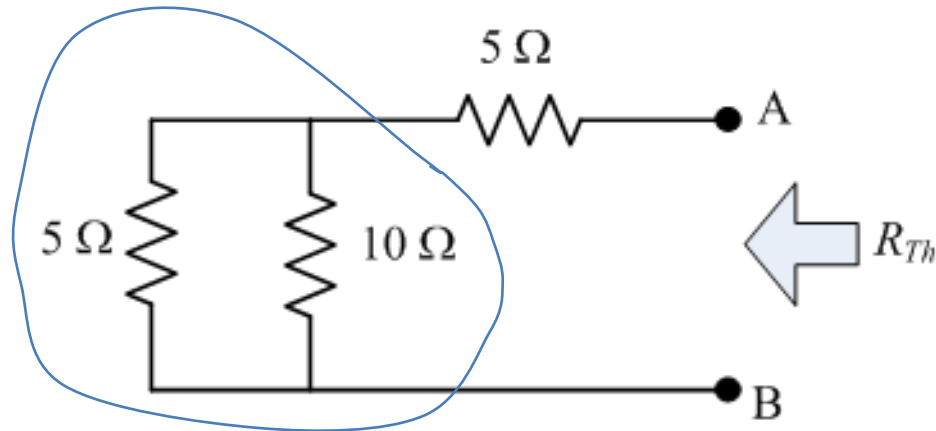

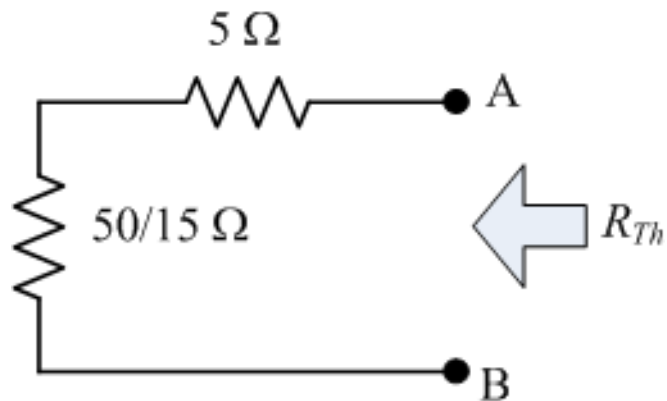
- This  $5\ \Omega$  and  $10\ \Omega$  are in parallel (equivalent =  $50/15$ )




# In the following circuit, find the value of  $R$  to obtain maximum power in it. Also calculate value of the maximum power.

---

- Calculate  $R_{Th}$

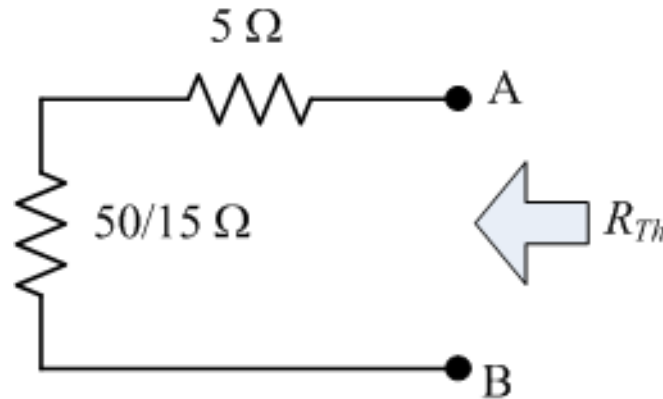

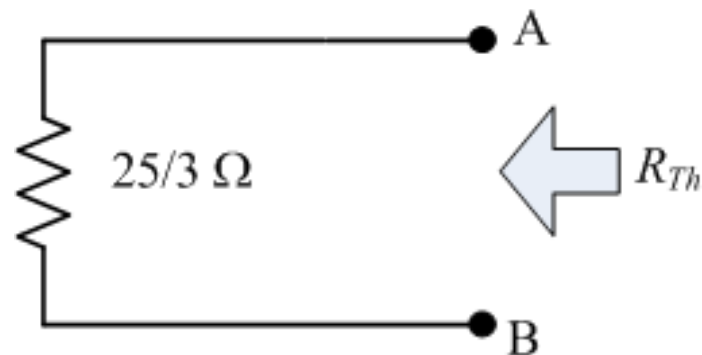- Finally,  $50/15$  and  $5$  are in series between A-B ( $50/15 + 5 = 25/3 \Omega$ )




$$R_{Th} = \frac{25}{3} \Omega$$

# In the following circuit, find the value of R to obtain maximum power in it. Also calculate value of the maximum power.

---

∴ The Thevenin's equivalent circuit is:

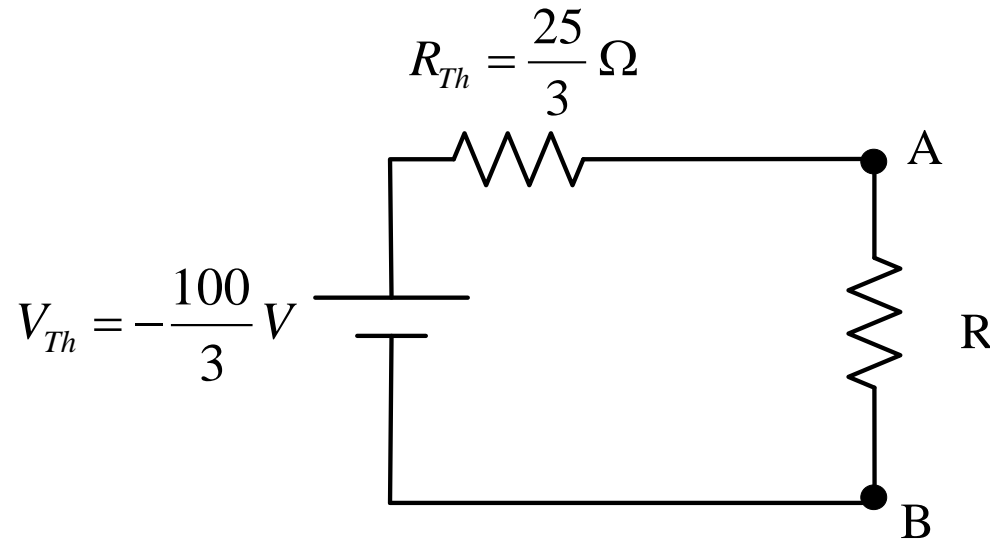


∴ According to maximum power transfer theorem, maximum power will be obtained by the resistance R when its value is equal to the Thevenin's equivalent resistance of the remaining part of the circuit, i.e. for

$$R = R_{Th} = \frac{25}{3} \Omega$$



# In the following circuit, find the value of R to obtain maximum power in it. **Also calculate value of the maximum power.**

---

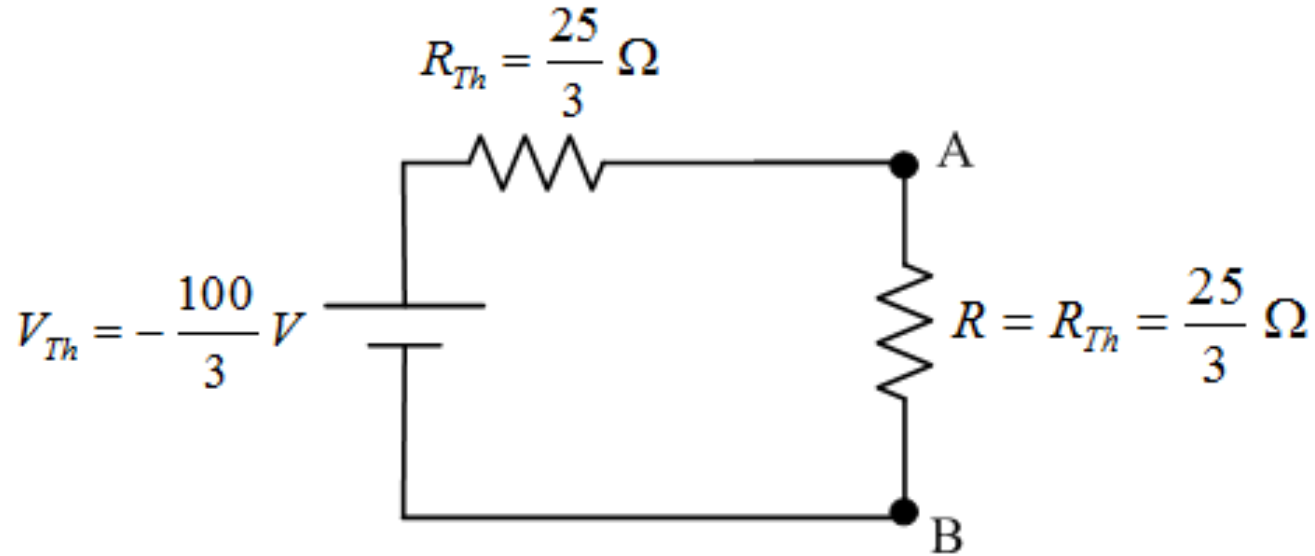

& Value of maximum power

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{\left(\frac{100}{3}\right)^2}{4 \times \frac{25}{3}} = 33.33 W$$