

AC Fundamentals

Day 11


RL Circuit

ILOs – Day 11

- For a resistive + inductive circuit with AC supply:
 - Derive the expression for current and power
 - Draw phasor diagram

AC circuit operation
with resistance and
inductance together

AC circuit operation with R + L

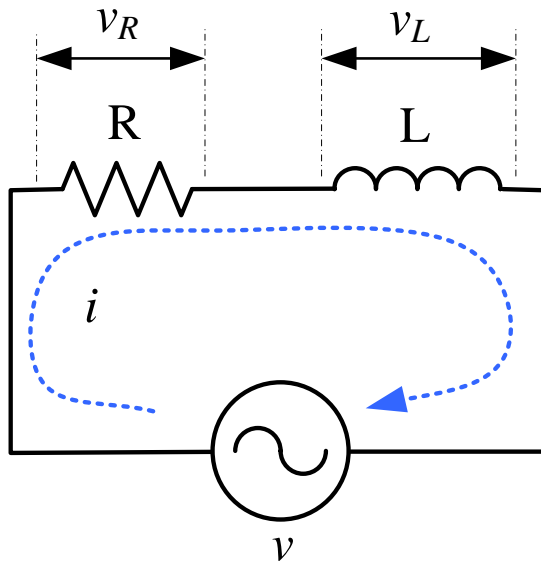


$$v = V_m \sin \omega t$$

Phasor diagram

- To draw the phasor diagram, we consider RMS values of the different signals
- These signals are: V_{RMS} , I_{RMS} , V_R , V_L
- The RMS value of current I_{RMS} is considered as the reference phasor and it is thus drawn along the X-axis
- *The general convention is to take the signal which is common to most part of the circuit as the reference phasor.*
- *(In a series circuit, current is common to all the elements)*


AC circuit operation with R + L

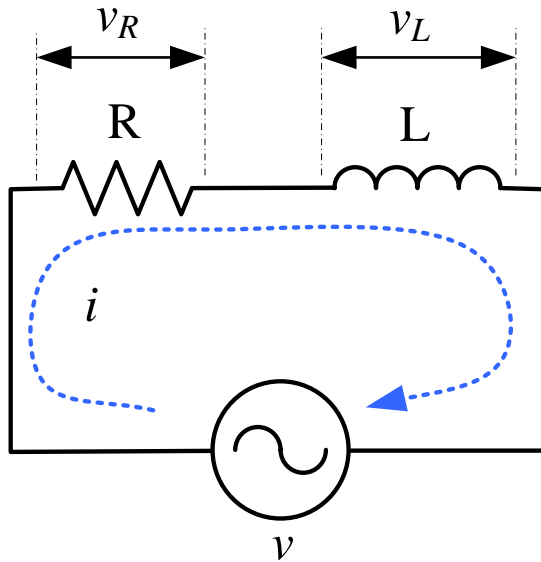


$$v = V_m \sin \omega t$$

Phasor diagram

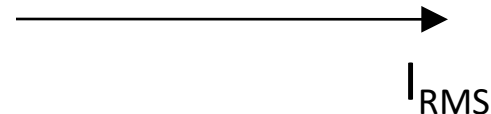- The RMS value of current I_{RMS} is drawn along the X-axis



AC circuit operation with R + L

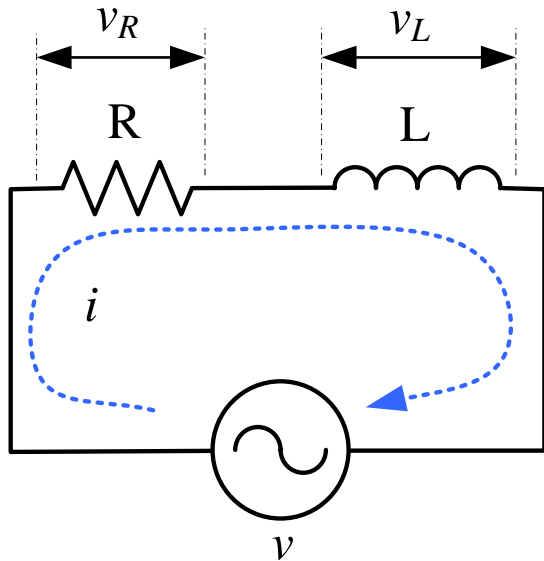


Phasor diagram

- Voltage drop across the resistance is
$$V_R = I_{RMS} R$$
- V_R phasor is drawn in the same direction as the current phasor
- *(remember, the current and voltage in a resistance are in the same phase)*



AC circuit operation with R + L

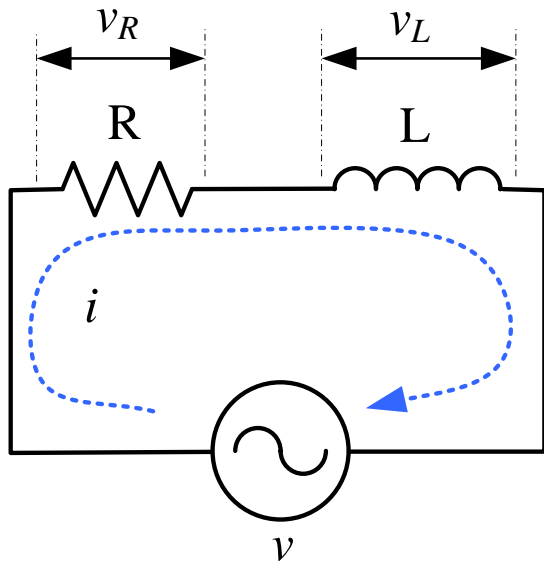


Phasor diagram


- Voltage drop across the inductor is

$$V_L = I_{RMS} X_L$$

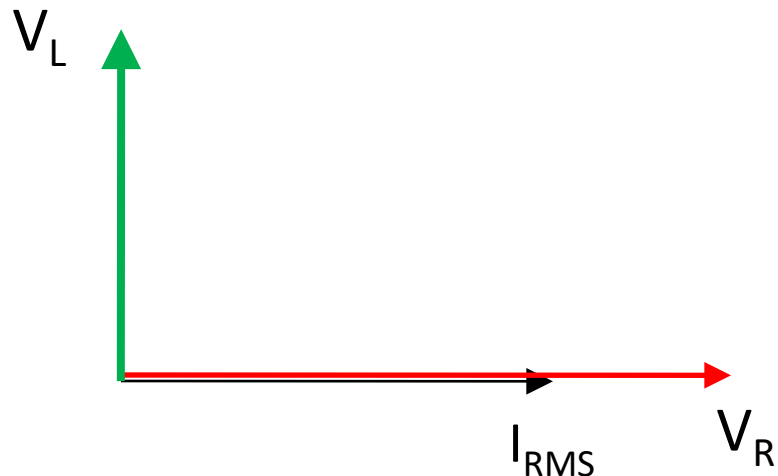- V_L phasor is drawn 90° leading to the current phasor
- (remember, voltage across an inductor leads the current through it by 90°)




AC circuit operation with R + L

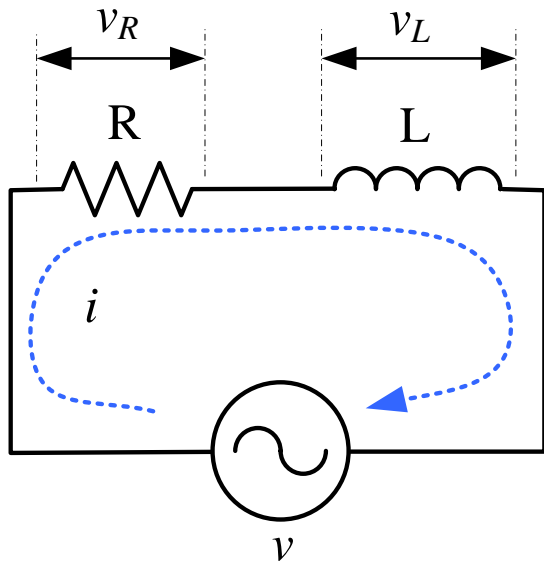


Phasor diagram

- According to KVL, the supply voltage must equal summation of the two voltage drops, one across the resistance and the other across the inductance
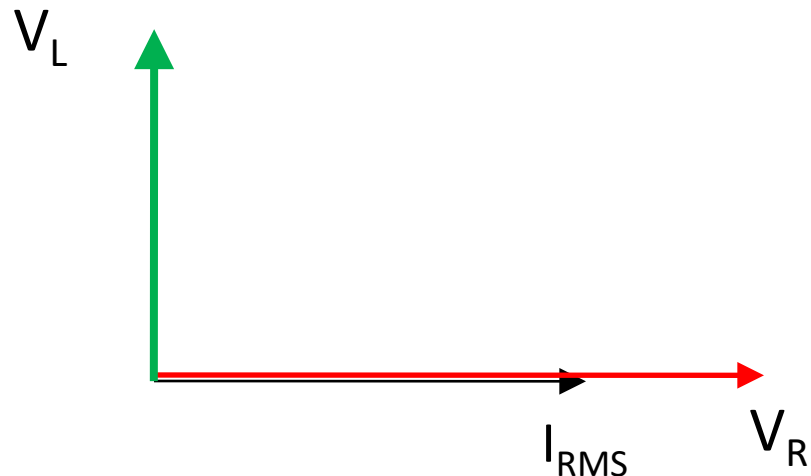
$$\overline{V_{RMS}} = \overline{V_R} + \overline{V_L}$$




AC circuit operation with R + L

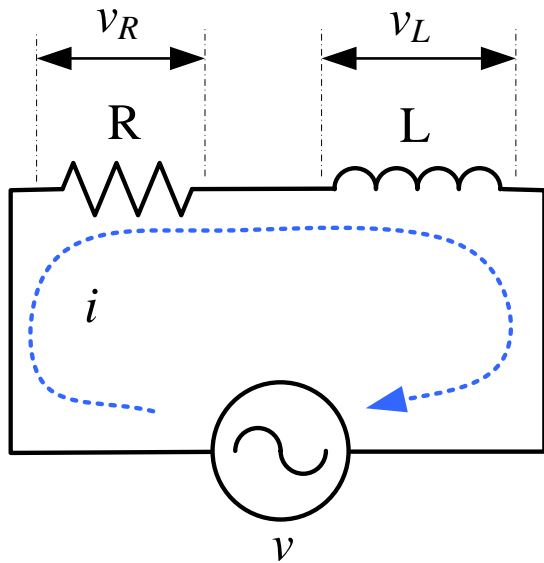


Phasor diagram

$$\overline{V_{RMS}} = \overline{V_R} + \overline{V_L}$$

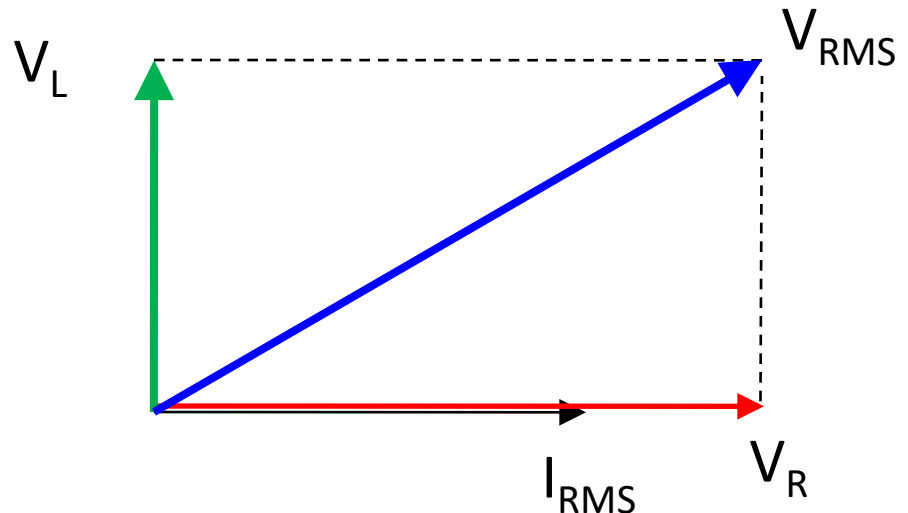- Thus, the supply voltage phasor V_{RMS} is drawn as the vector addition (resultant) of the two phasors V_R and V_L




AC circuit operation with R + L

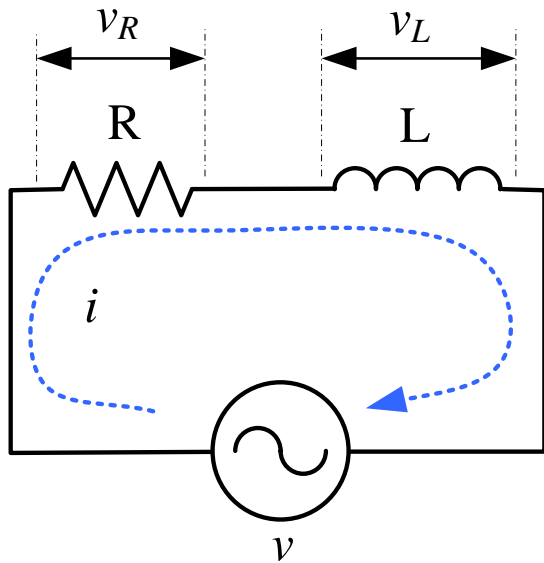


Phasor diagram

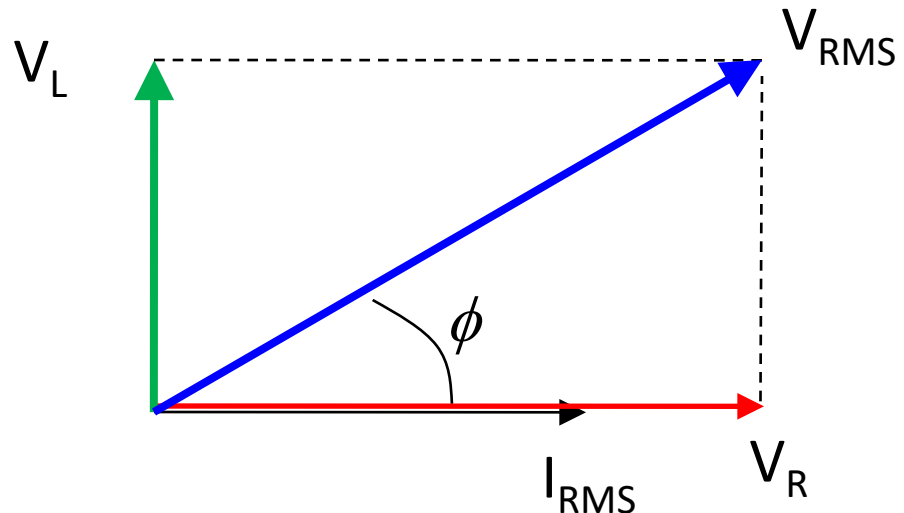- The angle between the supply voltage V_{RMS} phasor and the supply current I_{RMS} phasor is known as the **power factor angle ϕ**



AC circuit operation with R + L

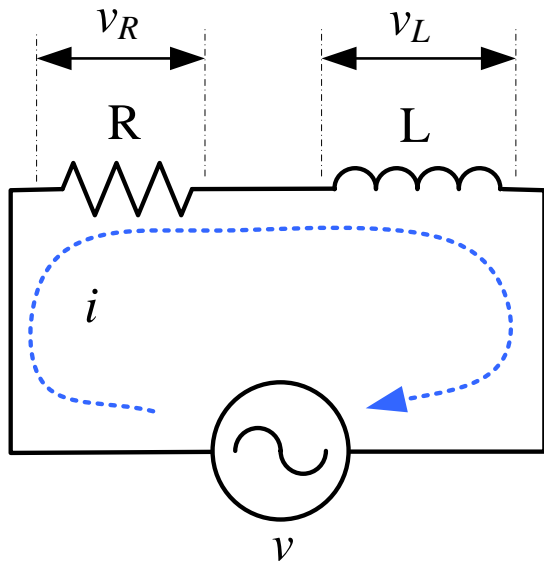


Phasor diagram


Value of the power factor angle can be expressed from the phasor diagram as:

$$\phi = \tan^{-1}\left(\frac{V_L}{V_R}\right) = \tan^{-1}\left(\frac{I_{RMS} \times X_L}{I_{RMS} \times R}\right) = \tan^{-1}\left(\frac{X_L}{R}\right)$$
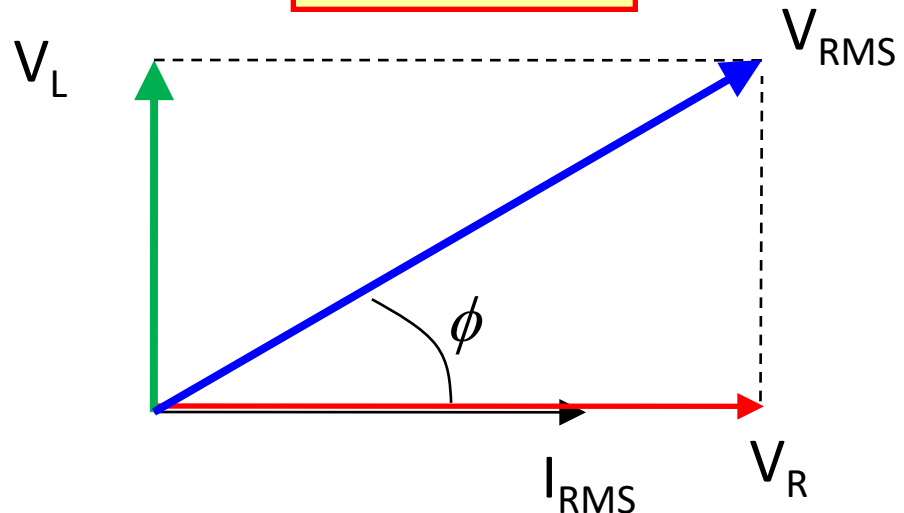
$$\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$




AC circuit operation with R + L

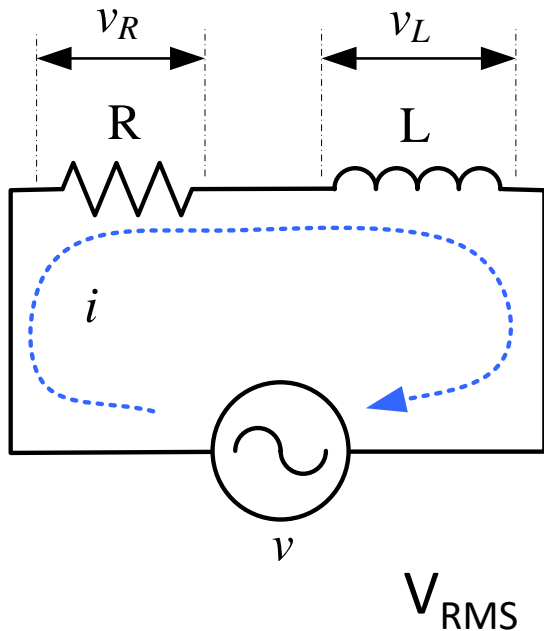



Phasor diagram

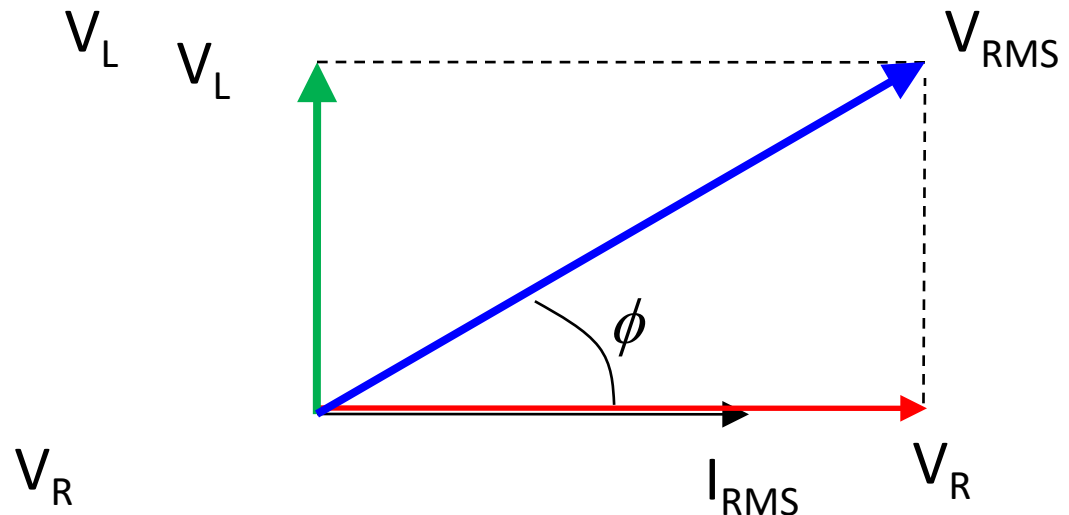Drawing only the voltage phasors from the phasor diagram we obtain the so-called **voltage triangle** of a series R-L circuit:



AC circuit operation with R + L

Voltage triangle

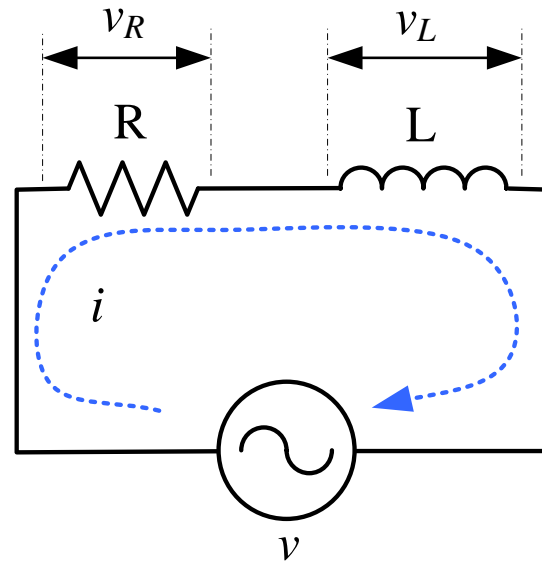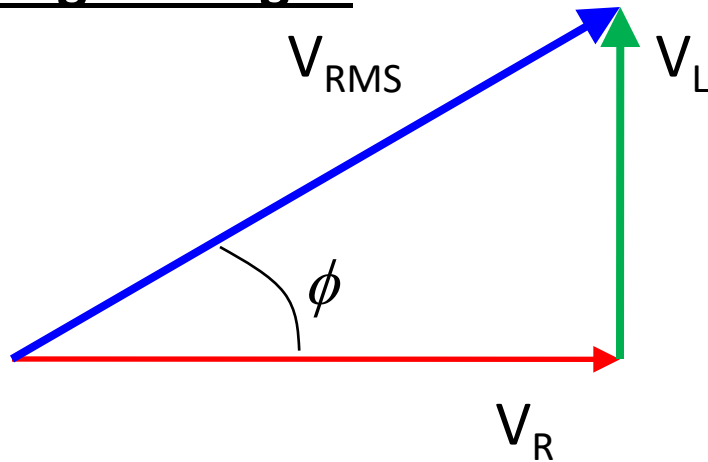

From the voltage triangle we have the relation:

$$V_{RMS} = \sqrt{V_R^2 + V_L^2}$$


$$V_{RMS} = \sqrt{(I_{RMS} R)^2 + (I_{RMS} X_L)^2}$$

$$V_{RMS} = I_{RMS} \sqrt{R^2 + X_L^2}$$


$$\frac{V_{RMS}}{I_{RMS}} = \sqrt{R^2 + X_L^2}$$

AC circuit operation with R + L

Voltage triangle

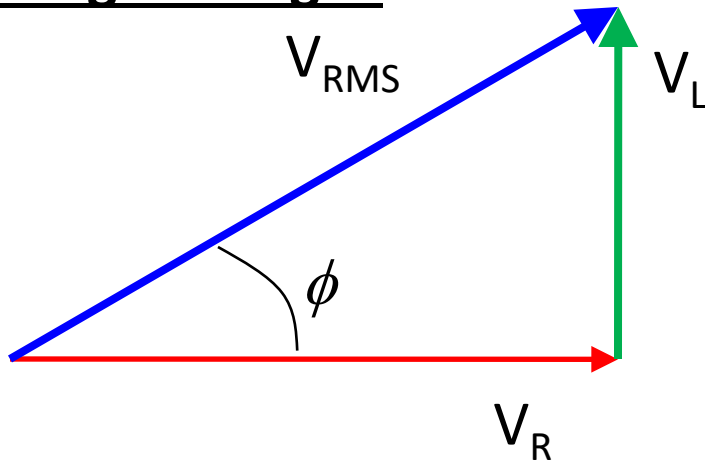
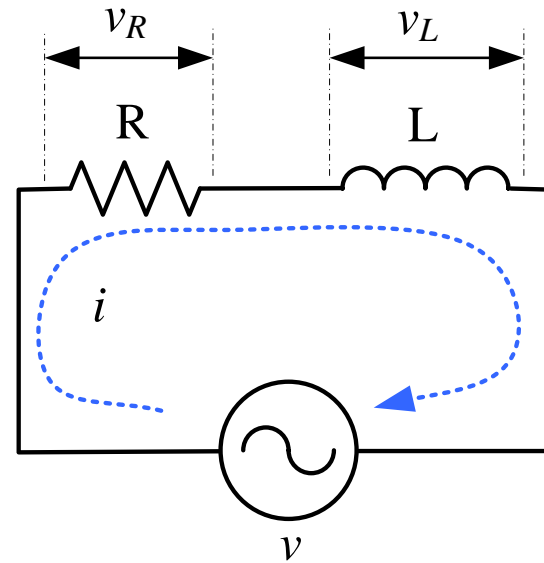
$$\frac{V_{RMS}}{I_{RMS}} = \sqrt{R^2 + X_L^2}$$



$$\frac{V_{RMS}}{I_{RMS}} = \sqrt{R^2 + X_L^2} = Z$$


This ratio of V_{RMS} and I_{RMS} in a series R-L circuit is called **impedance** of the circuit that has a magnitude

$$Z = \sqrt{R^2 + X_L^2}$$

The unit of impedance is also “Ohm” (Ω).

AC circuit operation with R + L

Voltage triangle

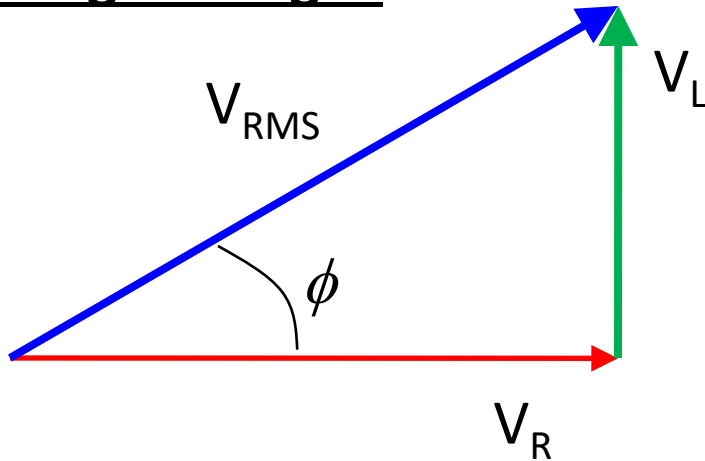


- Redraw the same triangle in terms of the resistance, reactance, and impedance only
- (by eliminating the common quantity I_{RMS})

$$V_R = I_{RMS} \times R$$

$$V_L = I_{RMS} \times X_L$$

$$V_{RMS} = I_{RMS} \times Z$$


Impedance triangle

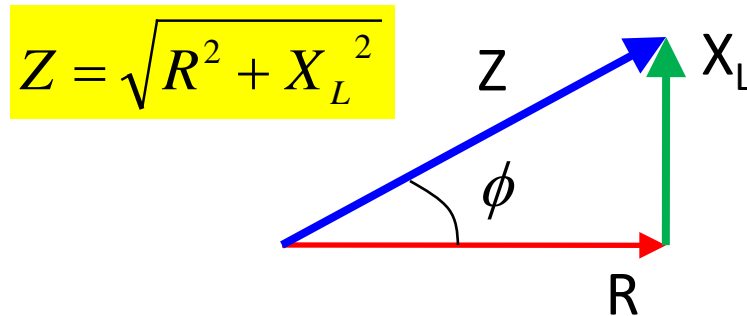

Hypotenuse of the impedance triangle is the impedance Z

AC circuit operation with R + L

More on phase angle

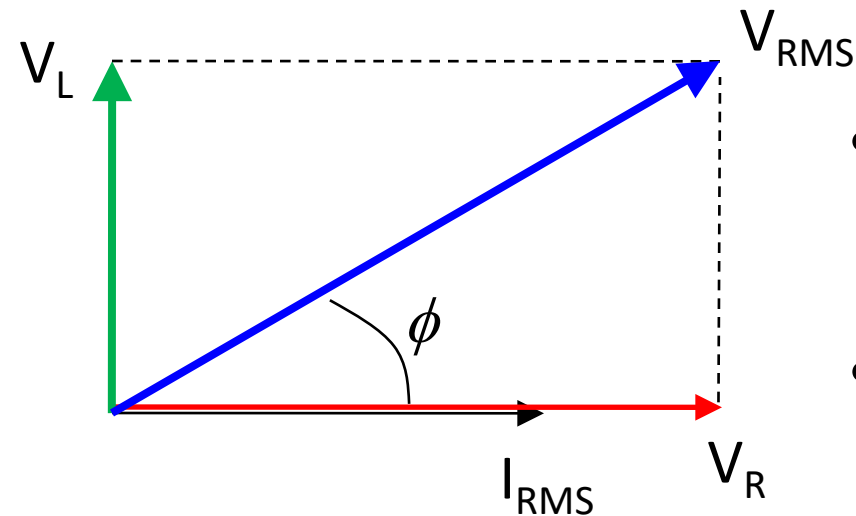


- The supply voltage signal leads the current by a phase angle ϕ which is less than 90°
- This is expected because it is a combination of R and L circuit

- In an R + L circuit, the angle between voltage and current should lie somewhere between 0° (pure resistance) and 90° (pure inductance)
- When $R > X_L$, the phase angle $\phi < 45^\circ$
- When $X_L > R$, then the phase angle $\phi > 45^\circ$
- When $X_L = R$, the phase angle $\phi = 45^\circ$


AC circuit operation with R + L

Instantaneous values

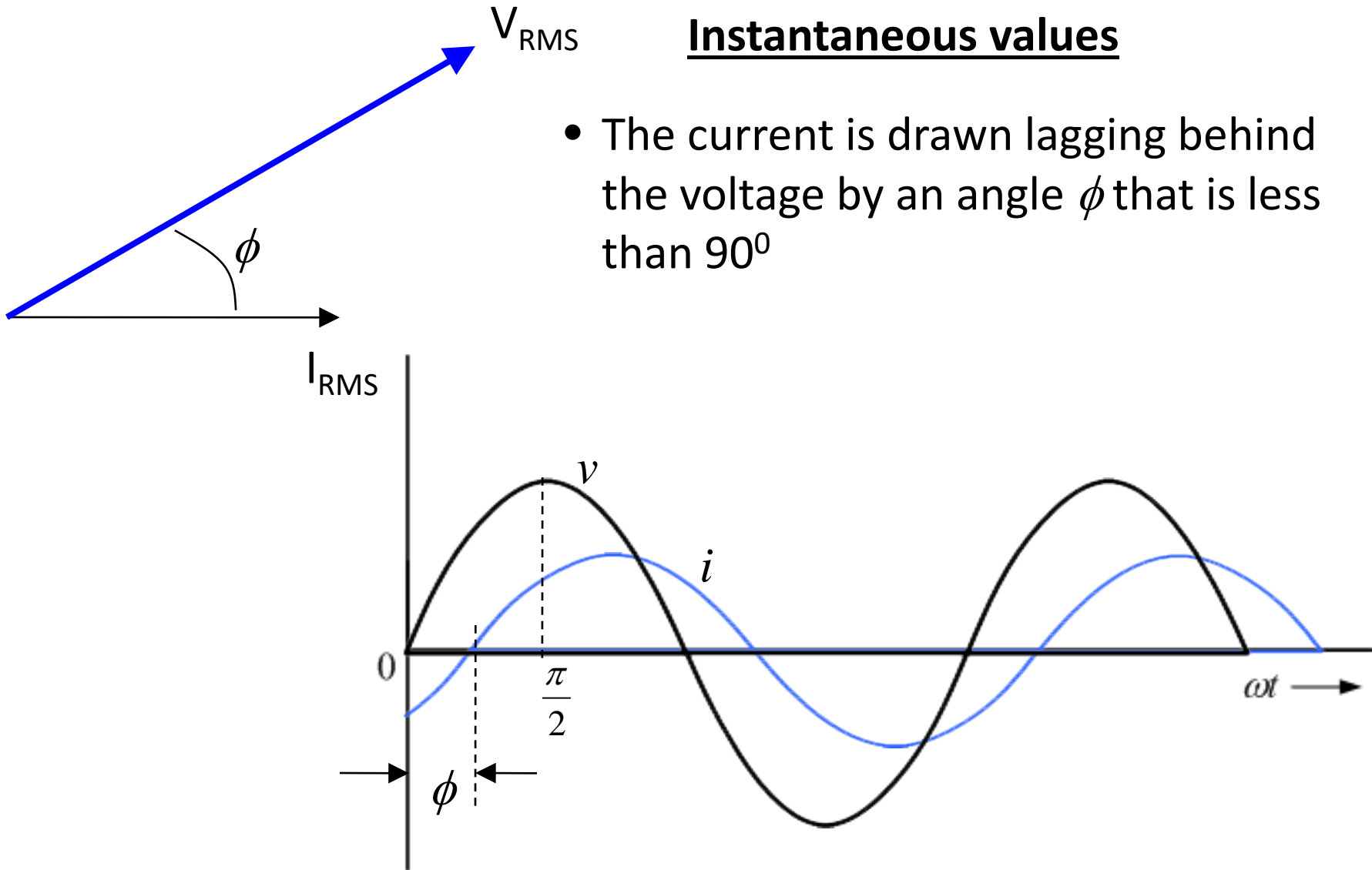- The current is drawn lagging behind the voltage by an angle ϕ that is less than 90°



AC circuit operation with R + L

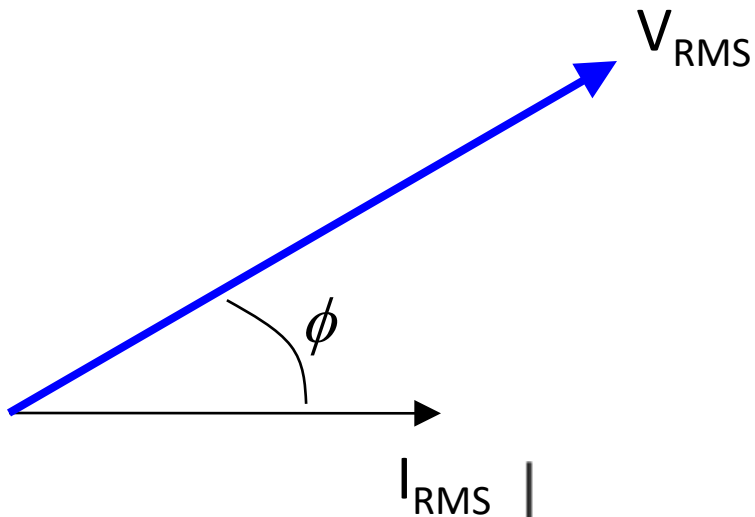


- If the voltage signal is given by the expression

$$v = V_m \sin \omega t$$


- then the current signal that lags behind the voltage by an angle ϕ , will be given by the expression

$$i = I_m \sin(\omega t - \phi)$$

$$I_m = \frac{V_m}{Z}$$

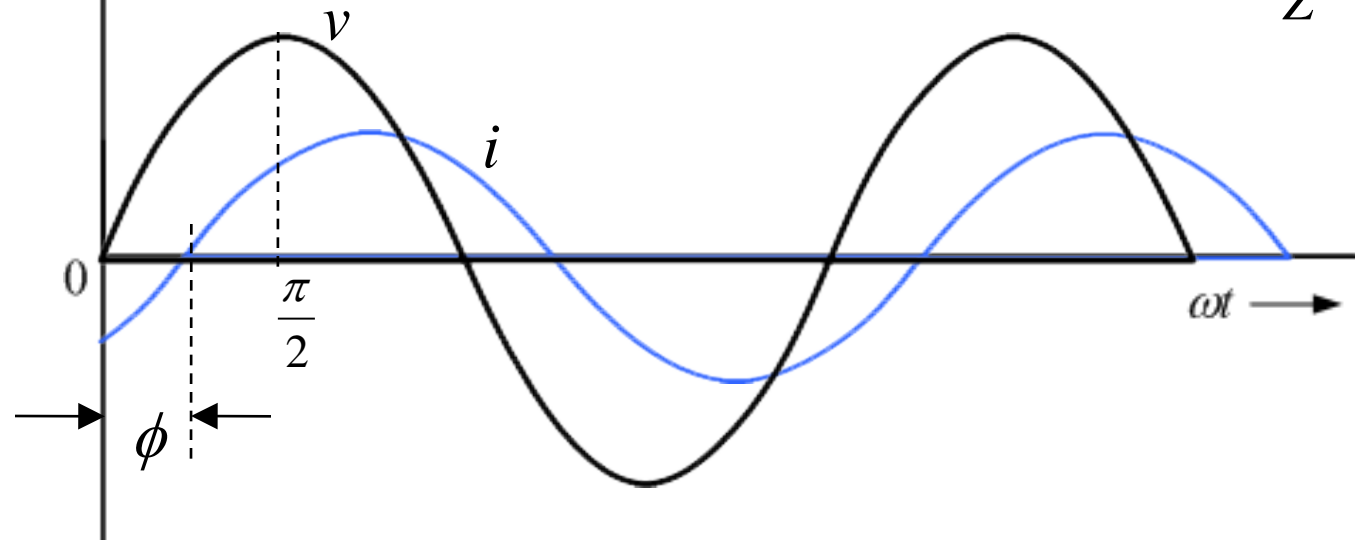

AC circuit operation with R + L

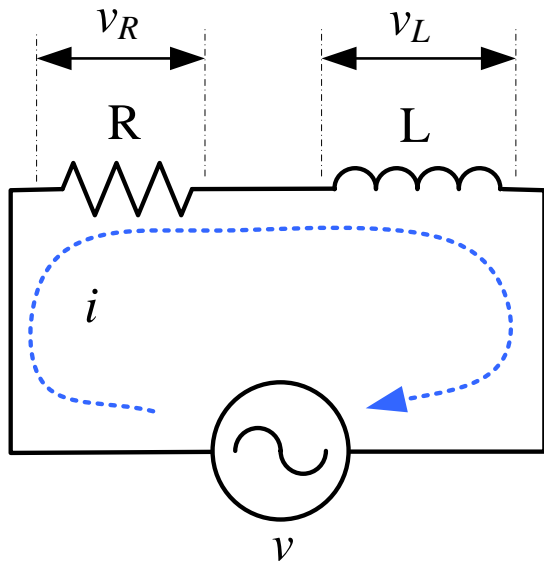

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \phi)$$

Instantaneous power


$$p = v \times i$$

$$p = V_m \sin \omega t \times I_m \sin(\omega t - \phi)$$

$$p = V_m I_m \sin \omega t \sin(\omega t - \phi)$$


$$p = \frac{V_m I_m}{2} [\cos(\omega t - \omega t + \phi) - \cos(\omega t + \omega t - \phi)]$$
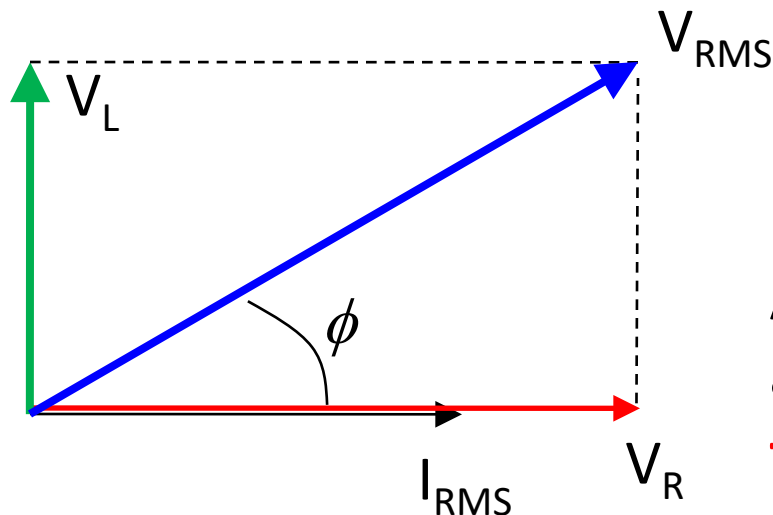
$$p = \frac{V_m I_m}{2} [\cos(\phi) - \cos(2\omega t - \phi)]$$



As earlier, the instantaneous power is an alternating quantity, but it varies at **twice the frequency** of the input voltage signal (note the 2ω term).

AC circuit operation with R + L

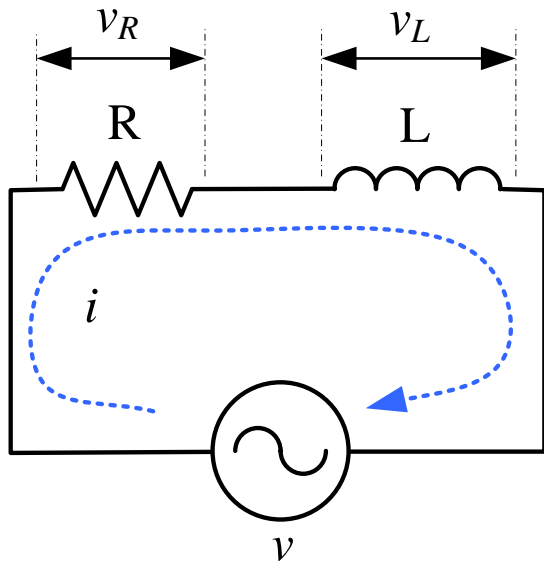

$$p = \frac{V_m I_m}{2} [\cos(\phi) - \cos(2\omega t - \phi)]$$


Average power

$$P = \frac{1}{T} \int_0^T p dt$$

$$P = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} [\cos(\phi) - \cos(2\omega t - \phi)] dt$$

$$P = \frac{V_m I_m}{2T} \int_0^T \left[\cos \phi - \cos \left(2 \frac{2\pi}{T} t - \phi \right) \right] dt$$

$$P = \frac{V_m I_m}{2T} \left[\cos \phi t - \frac{T}{4\pi} \sin \left(\frac{4\pi}{T} t - \phi \right) \right] \Bigg|_0^T$$

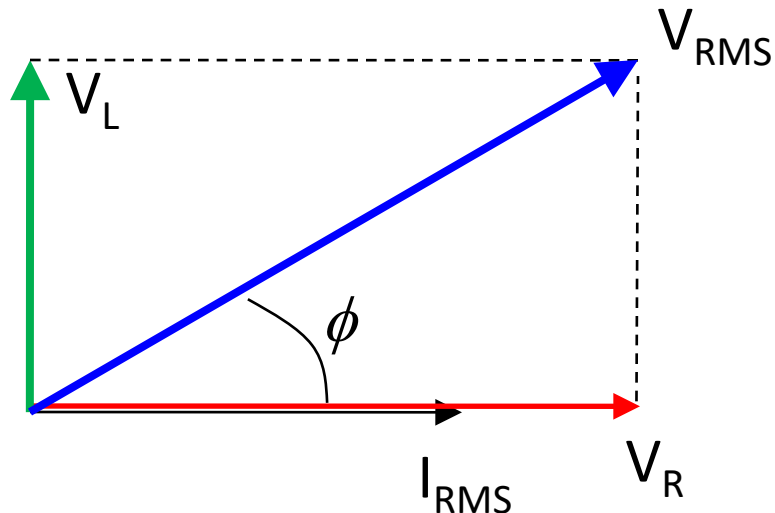


AC circuit operation with R + L

$$P = \frac{V_m I_m}{2T} \left[\cos \phi t - \frac{T}{4\pi} \sin \left(\frac{4\pi}{T} t - \phi \right) \right] \bigg|_0^T$$

$$P = \frac{V_m I_m}{2T} \left[(\cos \phi \times T - \cos \phi \times 0) - \left\{ \frac{T}{4\pi} \sin \left(\frac{4\pi}{T} T - \phi \right) - \frac{T}{4\pi} \sin \left(\frac{4\pi}{T} \times 0 - \phi \right) \right\} \right]$$
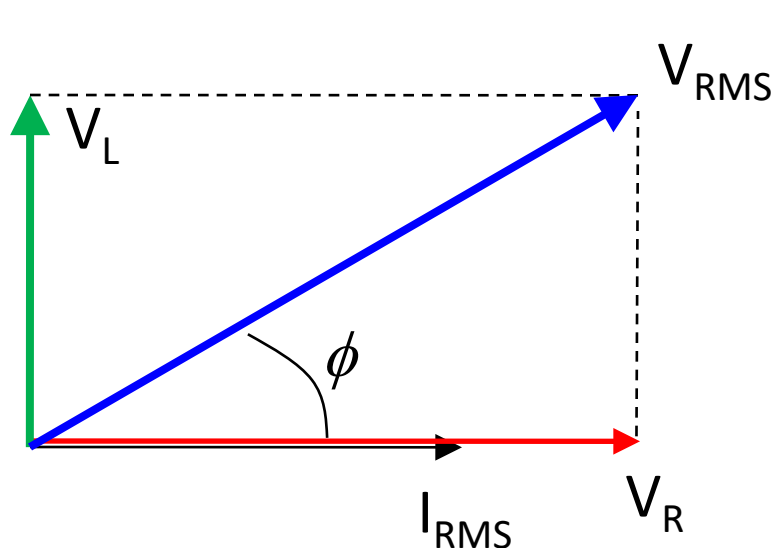
$$P = \frac{V_m I_m}{2T} \left[(T \cos \phi) - \left\{ \frac{T}{4\pi} \sin(4\pi - \phi) - \frac{T}{4\pi} \sin(-\phi) \right\} \right]$$



$$P = \frac{V_m I_m}{2T} \left[(T \cos \phi) - \left\{ \frac{T}{4\pi} \sin(-\phi) - \frac{T}{4\pi} \sin(-\phi) \right\} \right]$$

$$P = \frac{V_m I_m}{2T} (T \cos \phi)$$

$$P = \frac{V_m I_m}{2} \cos \phi$$

AC circuit operation with R + L


$$P = \frac{V_m I_m}{2} \cos \phi$$

$$P = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi$$

$$P = V_{RMS} I_{RMS} \cos \phi$$

Thus, the average active power consumed by a R-L series circuit is the product of RMS values of voltage and current and cosine of the angle between them.

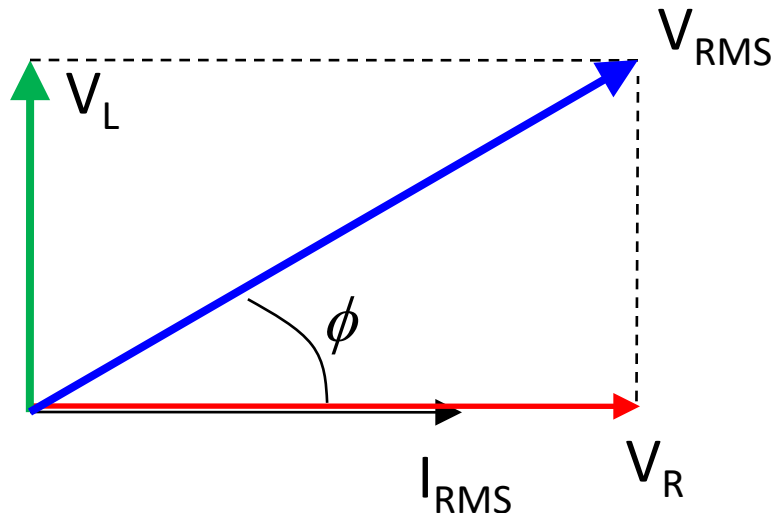The quantity $\cos \phi$ is called **power factor** of the circuit



$$\text{Power factor, } \cos \phi = \frac{P}{V_{RMS} I_{RMS}}$$