

Single Phase AC Circuits

(changes mag. as well as dir. periodically)

Introduction of Single Phase AC



Generation of Single phase AC

Basic Terms used

emf eqn for ϕ AC

① Generation of Single phase AC,

$$e = - \frac{N d\phi}{dt}$$

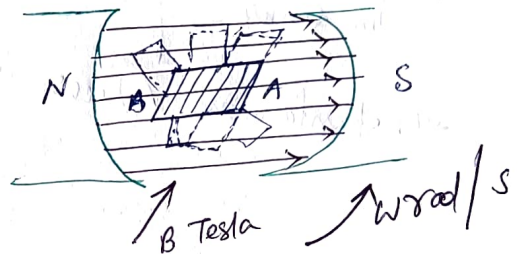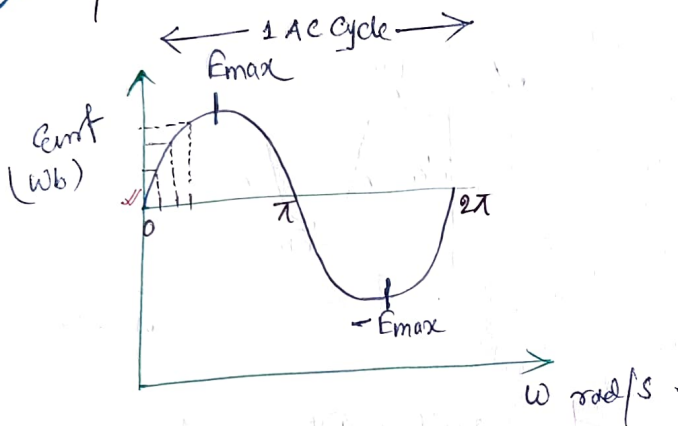

② Basic Terms used:

(i) Circuits

(ii) Alternating Current (AC)

(iii) Cycle

(iv) Frequency for AC = 50 Hz, for DC = 0

(v) phase difference

(vi) Leading Phase

(vii) Lagging Phase

$$* T = \frac{1}{f}$$

$\omega t \rightarrow \theta$


$$* \omega T = 2\pi$$

③ Emf equation for Single Phase AC:-

$$e = -N \cdot \frac{d\phi}{dt} \quad \text{--- (1)}$$

for the given condⁿ

PTO

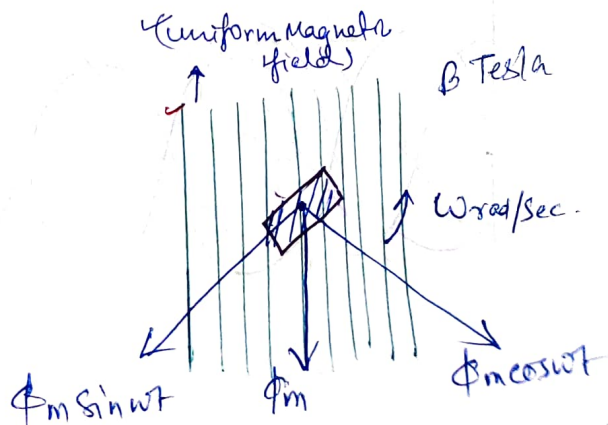

$$\phi = \phi_m \cos \omega t \quad (\perp \text{ component})$$

$$\frac{d\phi}{dt} = -\phi_m \sin \omega t \cdot \omega$$

$$\therefore e = -N \cdot \frac{d\phi}{dt}$$

$$= N\omega \phi_m \sin \omega t$$

$$e = N\omega \phi_m \sin \omega t$$


$$E_m = N\omega \phi_m \quad (\text{maxi. value})$$

$$e = E_m \sin \omega t$$

$$V = V_m \sin \omega t$$

$$i = i_m \sin \omega t$$

Instantaneous Values

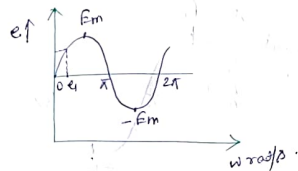



Representation of Single Phase AC

Graphical form

Magnitude form


Mathematical form

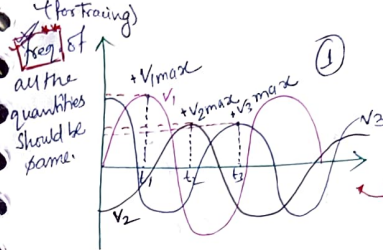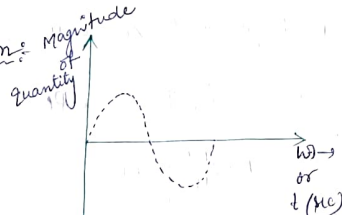① Graphical form: ① Wave form: Magnitude of quantity



Lead/Lag Condⁿ

3 signals are (out of phase)

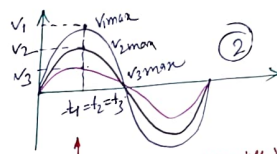

* but have same freq. and T

Between ① & ② Graph, only Graph ① show phase difference and leading & lagging Condⁿ along with different time.

Phasor form: $\sqrt{2}$ (20) (same freq)

$V = 30^\circ$ leading from Current I.

$$V_m = 300V$$

$$I_m = 20A$$

* max. value pata hoi change.

° ϕ , phase diff. and sath main kon lead/lag kar raha hai woh pata hoga change

② Mathematical form of representation of AC.

Rectangular form: $a + jb$


a = Constant part,

b = fluctuating part

$j = \sqrt{-1}$, phase shift of 90°

\rightarrow leading Condⁿ.

\rightarrow lagging Condⁿ.

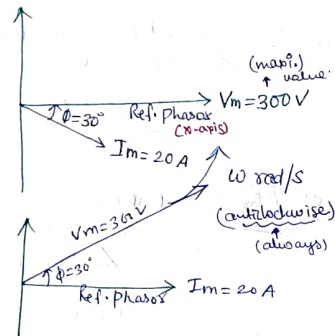

ω rad/s

(maxi.) value

$V_m = 300V$

Ref. Phasor (x-axis)

$I_m = 20A$

ω rad/s

(anticlockwise) (always)

$V_m = 300V$


Ref. Phasor

$I_m = 20A$

$$a = 20, b = 30$$

$$a + jb = 20 + j30$$

$$20 - j30$$

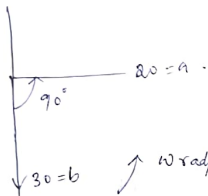

$$\text{Phase angle } (\phi) = \tan^{-1} \frac{b}{a}$$

$$\Rightarrow \tan \phi = b/a$$

(b) Trigonometrical form :- (NOT IMP)
(observation not use)

$$a \cos \theta \pm j b \sin \theta$$

(c) Polar form :- (IMP NUM.)
↓ magnitude

$$V = |V| \angle \pm \theta_{\text{phase angle}}$$

$$V = 20 \angle 30^\circ \text{ V} \quad \text{magnitude } 20 \text{ and lagging by } 30^\circ$$

$$V = 20 \angle \pm 30^\circ \text{ V} \quad \text{magnitude } 20 \text{ and leading by } 30^\circ$$

⑧ Magnitude form :-

① Instantaneous Values

② Peak or Maximum Value / Amplitude

③ Average Value representation


④ RMS Value (Root Mean Square Value) Representation.

⑤ Instantaneous Values :-

$$e = E_m \sin \omega t$$

$$V = V_m \sin \omega t$$

$$i = I_m \sin \omega t$$

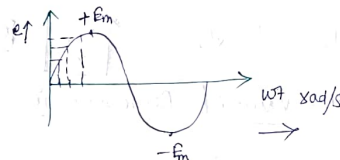

$$V = 200 \sin 35t \text{ V}$$

$$V = V_m \sin \omega t$$

$$V_m = 200 \text{ V}, \quad \omega = 35 \text{ rad/s}$$

⑥ Peak or Max^m Value Representation :-

$$\text{emf} \Rightarrow E_o, E_m, E$$

$$\text{Voltage} \Rightarrow V_o, V_m, V$$

$$\text{Current} \Rightarrow I_o, I_m, I$$


⑦ Average Value Representation :-

$$\text{Avg} = \frac{\text{Sum of all values}}{\text{no. of values}}$$

$$I_{\text{av}} = \frac{I_1 + I_2 + I_3 + \dots + I_n}{n}$$

* only half cycle avg nikala jata hai
(+ve) half
(-ve) half
hikala jata hai
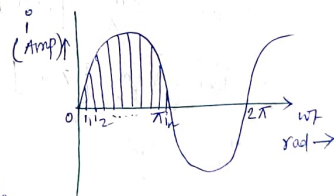
$$* \text{ avg. } \rightarrow \text{ sine wave } 1T \rightarrow 0$$



(half part of cycle) \uparrow
 Taking the area of alternation of $0-\pi$ and dividing it into all possible divisions.

$$I_{av} = \int_0^{\pi} \frac{I_m \sin \omega t}{\pi - 0} d\omega t$$

$$\Rightarrow I_{av} = \frac{I_m}{\pi} \int_0^{\pi} \sin \omega t d\omega t$$

$$\Rightarrow I_{av} = \frac{I_m}{\pi} (-\cos \omega t)_0^{\pi}$$

$$\Rightarrow I_{av} = \frac{I_m}{\pi} \times (1+1) = \frac{2I_m}{\pi} \Rightarrow 0.637 I_m$$

⑩ RMS Value of Representation:-

$$I = I_m \sin \omega t$$

Squaring both sides

$$I^2 = I_m^2 \sin^2 \omega t$$

$$\Rightarrow I^2 = I_m^2 \left(\frac{1 - \cos 2\omega t}{2} \right) \quad \text{(taking avg of given value)}$$

$$\Rightarrow I_{avg}^2 = \frac{I_m^2}{2} \int_0^{\pi} \frac{(1 - \cos 2\omega t)}{\pi - 0} d\omega t$$

$$\Rightarrow I_{av}^2 = \frac{I_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\omega t) d\omega t$$

$$\Rightarrow I_{av}^2 = \frac{I_m^2}{2\pi} \left[(\omega t)_0^{\pi} - \left(\frac{\sin 2\omega t}{2} \right)_0^{\pi} \right]$$

$$\Rightarrow I_{av}^2 = \frac{I_m^2}{2\pi} [\pi - 0]$$

$$\Rightarrow I_{av}^2 = \frac{I_m^2}{2} \quad \text{Squaring both sides.}$$

$$\Rightarrow I_{av} = \frac{I_m}{\sqrt{2}}$$

$$i_{rms} = \sqrt{\frac{I_m^2}{2}}$$

$$\Rightarrow i_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$E_{rms} = \frac{E_m}{\sqrt{2}}$$

* peak factor
 $K_p = \frac{\text{Maximum}}{\text{rms}}$

* form factor
 $ff = \frac{\text{rms}}{\text{avg}}$

Analysis of Single phase AC

Resistive Load
 R


Inductive Load
 L

Capacitive Load
 C

(a) Relation b/w V and I due to that load

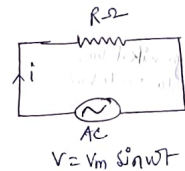(b) Power dissipated

AC Circuit Containing purely Resistive Load:-



Let us assume that a purely Resistive Load $R\Omega$ is Connected across a supply of


$$V = V_m \sin \omega t \quad \text{--- (1)}$$

$$i = \frac{V}{R} \quad \text{[By using Ohm's law]}$$

Putting the value of V from eq (1).

$$i = \frac{V_m \sin \omega t}{R}$$
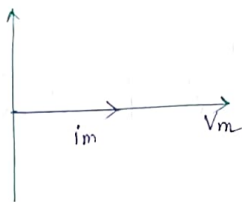
$$\Rightarrow i = I_m \sin \omega t \quad \text{--- (2)}$$



Comparing eq (1) & eq (2)
Voltage and current are in same phase (in phase)

$$\Phi = 0$$

power dissipated in purely resistive load:-

$$P = Vi$$

$$\Rightarrow P = V_m \sin \omega t \times I_m \sin \omega t$$

$$\Rightarrow P = V_m I_m \sin^2 \omega t$$

$$\Rightarrow P = V_m I_m \left(1 - \frac{\cos 2\omega t}{2}\right)$$

$$\Rightarrow P = \frac{V_m I_m}{2} - \frac{V_m I_m \cos 2\omega t}{2}$$

neglecting the fluctuating part or auro nikal kar
ge la sake hai


$$P = \frac{V_m I_m}{2} - 0$$

$$\Rightarrow P = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$\Rightarrow P = V_{rms} \cdot I_{rms}$$

AC Circuit containing purely Inductive Load:-

L (Henry)

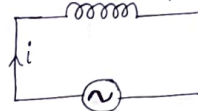

$$V = V_m \sin \omega t$$

(inductor \Rightarrow coil/magnet)

Let us assumed, a purely inductive load to be connected across a supply of

$$V = V_m \sin \omega t \quad \text{--- (1)}$$

emf induced in coil as given as

$$e = -N \frac{d\phi}{dt}$$

$e = (-V)$ (\because emf = equivalent voltage)

$$N = L \quad (\text{no. of turns} = \text{inductance}) \text{ n.t.}$$

$$\frac{d\phi}{dt} = \frac{di}{dt} \quad (\text{rate of change of flow of supply current})$$

(rate of ring flux)

$$-V = -L \frac{di}{dt}$$

$$\Rightarrow V = L \frac{di}{dt}$$

from eq (1)

$$V_m \sin \omega t = L \cdot \frac{di}{dt}$$

$$\Rightarrow di = \frac{V_m}{L} \cdot \sin \omega t \, dt$$

$$\Rightarrow i = \frac{V_m}{L} \cdot \left[-\frac{\cos \omega t}{\omega} \right]$$

$$\Rightarrow i = -\frac{V_m}{\omega L} \cos \omega t$$

$$i = \frac{V_m}{\omega L} \sin(\omega t - \frac{\pi}{2})$$

Comparing it with Ohm's law:-

$$X_L = \omega L \quad \left\{ \text{By Ohm's law} \right\}$$

$$i = \frac{V_m}{X_L} \sin(\omega t - \frac{\pi}{2})$$

$$\Rightarrow i = I_m \sin(\omega t - \frac{\pi}{2}) \quad \left\{ \text{By Ohm's law} \right\}$$

(2)

for purely inductive load, current lags by voltage by 90° .

power in AC circuit for purely

Inductive load:

$$P = Vi$$

$$= V_m \sin \omega t \cdot I_m \sin(\omega t - \frac{\pi}{2})$$


$$\Rightarrow P = -V_m I_m \sin \omega t \cos \omega t$$

Multiplying and dividing with 2.


$$\Rightarrow P = -\frac{V_m I_m}{2} \times 2 \sin \omega t \cos \omega t$$

$$\Rightarrow P = -\frac{V_m I_m}{2} \sin 2\omega t \quad \left\{ \text{neglecting fluctuating part} \right\}$$

$$\Rightarrow \boxed{P = 0}$$

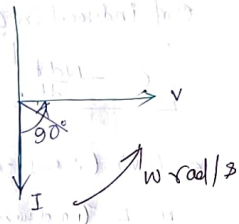

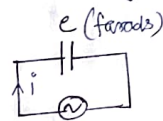AC circuit containing purely capacitive Load:-



$$V = V_m \sin \omega t$$

Let us assume that a purely capacitive load of C farads is connected across a supply of

$$V = V_m \sin \omega t \quad \text{--- (1)}$$

The charge stored by a capacitor is given as

$$q = CV$$

$$i = \frac{dq}{dt}$$

$$\Rightarrow i = \frac{d}{dt} (CV)$$

$$\Rightarrow i = C \cdot \frac{dV}{dt} \Rightarrow i = C \cdot \frac{d}{dt} (V_m \sin \omega t)$$

$$\Rightarrow i = CV_m \cdot \frac{d}{dt} \sin \omega t$$

$$\Rightarrow i = V_m C \cdot \cos \omega t \cdot \omega$$

$$\Rightarrow i = V_m \omega C \cos \omega t$$

$$\Rightarrow i = V_m \omega C \cdot \sin(\omega t + \frac{\pi}{2})$$

$$\Rightarrow i = \frac{V_m \sin(\omega t + \frac{\pi}{2})}{(\frac{1}{\omega C})}$$

$$\Rightarrow i = \frac{V_m \sin(\omega t + \frac{\pi}{2})}{X_C}$$

By comparing it to Ohm's law

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$\Rightarrow i = I_m \sin(\omega t + \pi/2) \quad \left\{ \text{acc. to Ohm's law} \right\}$$

②

By comparing eq (1) & eq (2)

I leads from voltage by 90° for a purely capacitive load.

Power in an AC circuit containing purely capacitive load.


$$p = v i$$

$$\Rightarrow p = V_m \sin \omega t \cdot I_m \sin(\omega t + \pi/2)$$

$$\Rightarrow p = V_m I_m \sin \omega t - \cos \omega t$$

$$\Rightarrow p = \frac{V_m I_m}{2} \times \sin 2\omega t$$
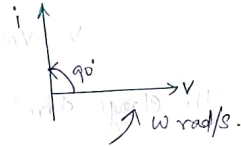
$$\boxed{p = 0} \quad \left\{ \text{By neglecting fluctuating part} \right\}$$



$$\begin{aligned} \sin 2\omega t &= \frac{1}{2} \\ \sin \omega t &= 0 \end{aligned}$$

Components of Single Phase AC:-


① Impedance Triangle:-

② The power Triangle:-

③ Power Factor:-

P.T.O

Impedance Triangle:-

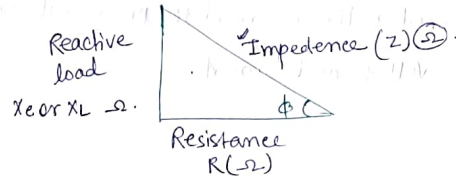

$$R \rightarrow \phi = 0$$

$$X_L \rightarrow I = I_m \sin(\omega t - \pi/2)$$

$$X_C \rightarrow I = I_m \sin(\omega t + \pi/2)$$

$$Z = \sqrt{R^2 + X^2}$$

$$Z = \sqrt{R^2 + (X_C - X_L)^2} \quad \text{if } X_C > X_L$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad \text{if } X_L > X_C$$

$$Z = \sqrt{R^2} = R \quad \text{if } \boxed{X_L = X_C} \quad \text{(Resonance)}$$

$$\sin \phi = \frac{X}{Z}$$

$$\cos \phi = \frac{R}{Z}$$

Power Triangle:-

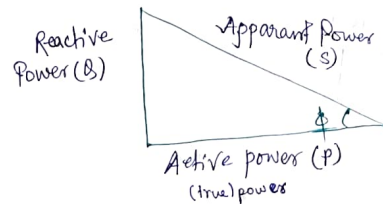

① Active power (P) -

② Reactive Power (Q)

③ Apparent power (S)

$$\begin{aligned} P &= V_{rms} \cdot I_{rms} \cos \phi \quad (\text{watts}) \\ Q &= V_{rms} \cdot I_{rms} \sin \phi \quad (\text{Volt-Amp Reactive}) \\ S &= V_{rms} \cdot I_{rms} \quad (\text{Volt-Amp}) \end{aligned}$$

Power factor: (factor on which true power depend)

A power factor is defined as the cosine of the phase difference angle between Supply Voltage and Current.

- ① $\cos \phi$
- ② $\cos \phi = \frac{R}{Z}$
- ③ $\cos \phi = \frac{\text{Active Power}}{\text{Apparent power}} = \frac{P}{S}$

Numericals on Series AC Circuit

Q Find an expression for current flowing and calculate the power in a series R-L circuit of value $R = 50\Omega$ and $L = 0.159$ H when a voltage of $V = 283 \sin 100t$ is applied.

$$\rightarrow V = 283 \sin 100t$$

$$V_m = 283 \text{ V}, \quad \omega = 100 \text{ rad/s.}$$


$$X_L = \omega L$$

$$= 100 \times 0.159$$

$$= 15.9 \Omega$$

$$I = \frac{V_m}{R} \sin 100t \rightarrow I = \frac{283}{50} \sin 100t$$

$$i = I_m \sin \omega t$$

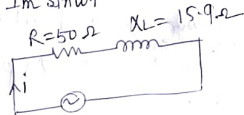

Always find rms values

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{283}{\sqrt{2}} = 200.11 \text{ V}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{(50)^2 + (15.9)^2}$$

$$Z = 52.46 \Omega$$

$$V = IZ$$

$$I_{rms} = \frac{V_{rms}}{Z}$$

$$I_{rms} = \frac{200.11}{52.46}$$

$$I_{rms} = 3.81 \text{ A}$$

$$I_m = I_{rms} \times \sqrt{2}$$

$$= 3.81 \sqrt{2}$$

$$= 5.39 \text{ A}$$

$$\Rightarrow \cos \phi = \frac{R}{Z}$$

$$\Rightarrow \cos \phi = \frac{50}{52.46}$$

$$\Rightarrow \phi = 17.63^\circ$$

$$i = 5.39 \sin(100t - 17.63^\circ) \text{ A}$$


$$P = V_{rms} I_{rms} \cos \phi$$

$$= 200.11 \times 3.81 \times \frac{50}{52.46} \text{ W}$$

$$= 726.6 \text{ W}$$

Q If a resistance of 15Ω and capacitor of $150 \mu\text{F}$ are connected in series across 230 V , 50 Hz supply then calculate

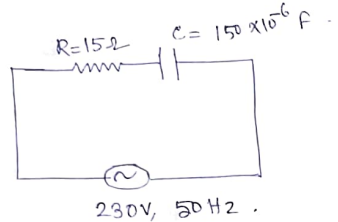- (a) Impedance
- (b) Current
- (c) Power factor
- (d) Phase angle
- (e) power consumed



→ $R = 15\Omega$, $C = 150 \times 10^{-6} F$ $V_{rms} = 230V$

$$\Rightarrow X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{10^6}{2\pi \times 50 \times 150}$$

$$= \frac{7 \times 10^4}{2\pi \times 150} = 21.23\Omega$$

① Impedance (Z) = $\sqrt{(15)^2 + (21.23)^2}$

$$= \sqrt{225 + 454.96}$$

$$= 26.07\Omega$$

② power factor $\cos \phi = \frac{R}{Z} = \frac{15}{26.07} = 0.53^\circ$ (leading)

~~$\phi = 100^\circ$~~

④ phase angle $\phi = 1.01^\circ$

⑤ power consumed = $V_{rms} I_{rms} \cos \phi$ $I_{rms} = \frac{V_{rms}}{Z}$

$$= 230 \times 8.82 \times 0.53$$

$$= 1075.45 W$$


① $I_{rms} = \frac{V_{rms}}{Z} = \frac{230}{26.07} = 8.82 A$

Phasor:

$$V_m = V_{rms} \times \sqrt{2} = 325.269 V$$

$$I_m = I_{rms} \times \sqrt{2} = 12.515 A$$

$$\phi = 51.70^\circ$$

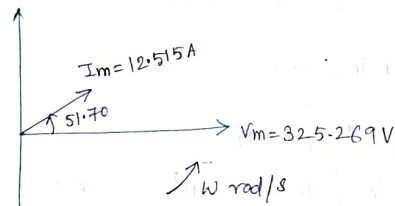

* Agar L, C both ho toh X_L , X_C pe depend karta hai (dominating) jo bhi hoga uske nature ka hoga circuit.

Numericals on Parallel AC Circuits:-

in parallel

8 Two Branches A and B are connected across a supply of 200V, 50Hz, if A consist of a resistance of 10Ω and inductance of $0.12 H$, B consist of a resistance of 20Ω and capacitor of $40\mu F$, then calculate —

- ① Total Impedance
- ② Total Current
- ③ Current in each Branch
- ④ power factor
- ⑤ phase.

→ Branch A, $R = 10\Omega$, $L = 0.12 H$, $X_L = \omega L = 2\pi f L$


Where $f = 50 Hz$, $X_L = 2\pi \times 50 \times 0.12 = 37.699\Omega$

$$V_{rms} = 200 V$$

Branch B, $R = 20\Omega$

$$C = 40 \times 10^{-6} F$$
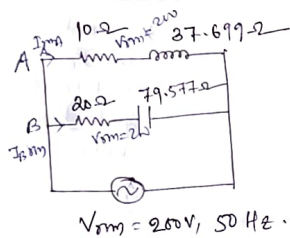
$$X_C = \frac{1}{\omega C} = 79.577\Omega$$



i) Total impedance

Branch wise, (series) $Z = \sqrt{R^2 + X_L^2}$

$$Z_A = \sqrt{(10)^2 + (37.699)^2} = 39.002 \Omega$$

parallel $Z_B = \sqrt{R^2 + X_C^2} = \sqrt{(20)^2 + (79.577)^2}$

$$= 82.051 \Omega$$

$Z_T = \frac{Z_A \times Z_B}{Z_A + Z_B} = 26.435 \Omega$

ii) Total supply current

$$I_{rms} = \frac{V_{rms}}{Z_T} = \frac{200}{26.435} = 7.565 A$$

iii) $I_{rmsA} = \frac{V_{rms}}{Z_A} = \frac{200}{39.002} = 5.127 A$

$$I_{rmsB} = \frac{200}{82.051} = 2.437 A$$

iv) Power factor $\cos \phi = \frac{R}{Z} = \frac{6.67}{26.435}$

$$= 0.252$$

$$\# \phi = \cos^{-1}(0.252) = 75.404^\circ$$

v) Phasor:

Branch A

$$V_{mA} = 282.842 V$$

$$I_{mA} = 5.250 A$$


$$\phi_A = \frac{10}{39.002} = 75.167^\circ$$

Branch B


$$V_{mB} = 282.842 V$$

$$I_{mB} = 3.446 A$$

$$\phi_B = 75.936^\circ$$

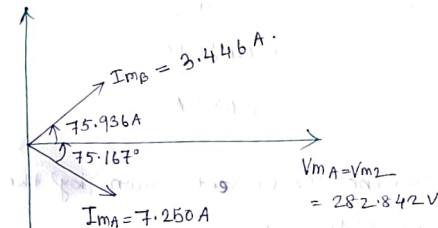

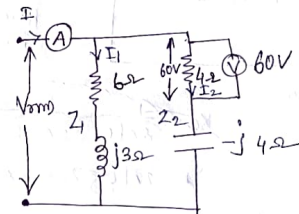8 In the given circuit, if a voltmeter reads 60V, then find the reading of Ammeter.



$$Z_1 = \sqrt{6^2 + 3^2} = 6.708 \Omega$$

$$Z_2 = \sqrt{4^2 + 4^2} = 5.656 \Omega$$

$$I_{rms2} = \frac{60}{4} = 15 A$$

$$Z_2 = 5.656 \Omega$$

$$V_{rms2} = 15 \times 5.656 = 84.84 V$$

$$V_{rms1} = V_{rms2} = 84.84 \text{ V}$$

$$Z_1 = 6.708 \Omega$$


$$I_{rms1} = \frac{84.84}{6.708} = 12.647 \text{ A}$$

$$I_{rmsT} = I_{rms1} + I_{rms2}$$

$$= 12.647 + 15$$

$$= 27.647 \text{ A}$$

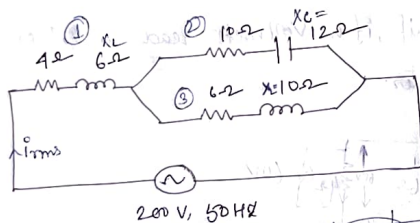8. Determine the Current drawn by the given network at a Supply Voltage of 200V.



If Capacitive, then unit will be in farad. Here unit is Ω so it is X_L & X_C .

$$\rightarrow V_{rms} = 200 \text{ V}$$

$$Z_1 = \sqrt{(4)^2 + (6)^2} = 7.211 \Omega$$

$$Z_2 = \sqrt{(10)^2 + (12)^2} = 15.620 \Omega$$

$$Z_3 = \sqrt{(6)^2 + (10)^2} = 11.661 \Omega$$


$$Z_T = Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3} = 13.887 \Omega$$

$$I_{rms} = \frac{200}{13.887} = 14.401 \text{ A}$$

9. With reference to the Network given below find:

(i) Z_T (ii) Branch Currents (iii) power factor (iv) power dissipated

(v) phasor

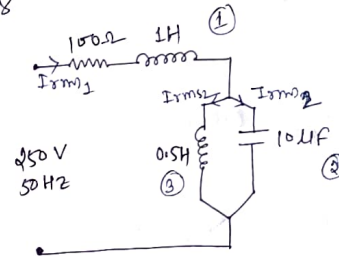

$$\rightarrow L_1 = 1 \text{ H}, \quad X_{L1} = 2\pi fL = 2\pi \times 50 \times 1 = 314.15 \Omega$$

$$C = 10 \mu\text{F} = X_C = \frac{1}{2\pi fC} = \frac{10^6}{2\pi \times 50 \times 10} = 3183.098 \Omega$$

$$X_{L2} = 2\pi f \times 0.5 = 157.079 \Omega$$

$$Z_1 = \sqrt{(100)^2 + (314.15)^2} = 3145.739 \Omega$$

$$Z_2 = \sqrt{(3183.098)^2} = 3183.098 \Omega \times 318.3098 \Omega$$

$$Z_3 = \sqrt{(157.079)^2} = 157.079 \Omega$$

$$(i) \cdot Z_T = Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3} = 3295.399 \Omega$$

$$(ii) \cdot I_{rms} = \frac{250}{3295.399} = 0.075 \text{ A} \quad I_{rms1} = I_{rmsT}$$

$$Z_{parallel} = 149.660 \Omega$$

$$V_{parallel} = 149.660 \times 0.075 \text{ V}$$

$$I_{parallel} = I_{rms1} = 0.075$$

$$= 11.224 \text{ V}$$

$$V_{m2} = V_{m3} = 11.224 \text{ V}$$

$$\therefore I_{m2} = \frac{11.224}{3183.098} = 0.0035 \text{ A}$$

$$I_{m3} = \frac{11.224}{157.079} = 0.071 \text{ A}$$

$$\textcircled{III} \quad \cos \phi = \frac{R}{Z} = \frac{100}{3295.899} = 0.030$$

$$\textcircled{IV} \quad P = V_{m0} I_{m0} \cos \phi$$

$$\Rightarrow P = 250 \times 0.075 \times 0.030 = 0.562 \text{ W}$$

$$\textcircled{V} \quad \text{Branch (1)}$$

$$V_{m0} = I_{m0} \times Z$$

$$\Rightarrow V_{m1} = 0.075 \times 3145.729 = 235.930 \text{ V}$$

$$V_{m1} = 333.655 \text{ V}$$

$$I_{m1} = 0.106 \text{ A}$$

$$\cos \phi_1 = \frac{100}{3145.739} = 0.031$$

$$\phi_1 = \cos^{-1}(0.031) = 88.223^\circ$$

Branch (2)

$$V_{m2} = 15.873 \text{ V}$$

$$I_{m2} = 0.100 \text{ A}$$

$$\phi_2 = \cos^{-1} R/Z$$

$$\phi_2 = 90^\circ$$

Branch (2)

$$V_{m2} = 15.873 \text{ V}$$

$$I_{m2} = 0.004 \text{ A}$$

$$\cos \phi_2 = R/Z$$

$$\phi_2 = \cos^{-1}(R/Z) = 90^\circ$$

