

# AC Fundamentals

---

Day 10

Phasor diagram

# ILOs – Day 10

---

- Understand the basic concept of phasor diagram for AC circuits
- For a purely resistive circuit with AC supply:
  - Derive the expression for current and power
  - Draw phasor diagram
- For a purely inductive circuit with AC supply:
  - Derive the expression for current and power
  - Draw phasor diagram
- For a purely capacitive circuit with AC supply:
  - Derive the expressions for current and power
  - Draw phasor diagram


# Phasor diagram

---

- AC signals are popularly represented by the use of phasor diagrams
- In AC circuits, different signals that are of the same frequency can be represented by phasor diagrams
- A phasor is a two-dimensional vector:
  - whose length is proportional to the RMS value of the signal
  - and angle is equal to the phase angle difference between that signal and a reference phasor
- The reference phasor is normally drawn along the X-axis
- If the signal leads the reference signals, then its phasor is drawn in the anticlockwise direction
- If the signal lags the reference signal, its phasor is drawn in the clockwise direction
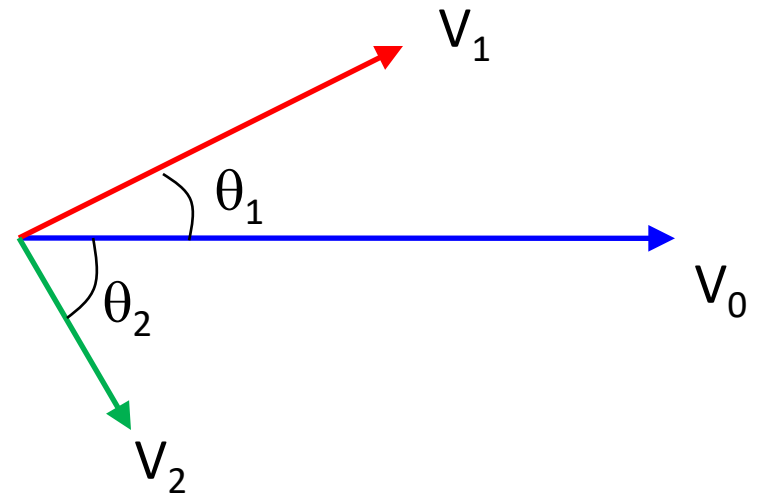
# Phasor diagram


- Phasor diagram of three voltages with RMS values  
 $V_0 > V_1 > V_2$



- Lengths of the phasors are proportional to their RMS values
- $V_0$  is the reference phasor, drawn along the X-axis
- Say, the phasor  $V_1$  leads the reference phasor  $V_0$  by  $\theta_1$
- Say, the phasor  $V_2$  lags the reference phasor  $V_0$  by  $\theta_2$
- The phasor  $V_1$  leads the phasor  $V_2$  by  $(\theta_1 + \theta_2)$
- The phasor  $V_2$  lags the phasor  $V_1$  by  $(\theta_1 + \theta_2)$

# AC circuit operation with resistance

# AC circuit operation with R

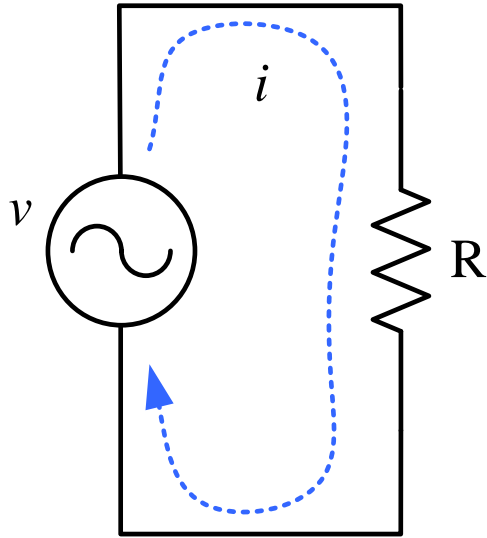


$$v = V_m \sin \omega t$$

$$i = \frac{v}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t = I_m \sin \omega t$$

Where  $I_m = \frac{V_m}{R}$  is peak value of the current


- Thus current flowing through the circuit is also sinusoidal
- Current has the same frequency ( $\omega$ ) as the input voltage signal
- Magnitude of current depends on value of  $R$

# AC circuit operation with R

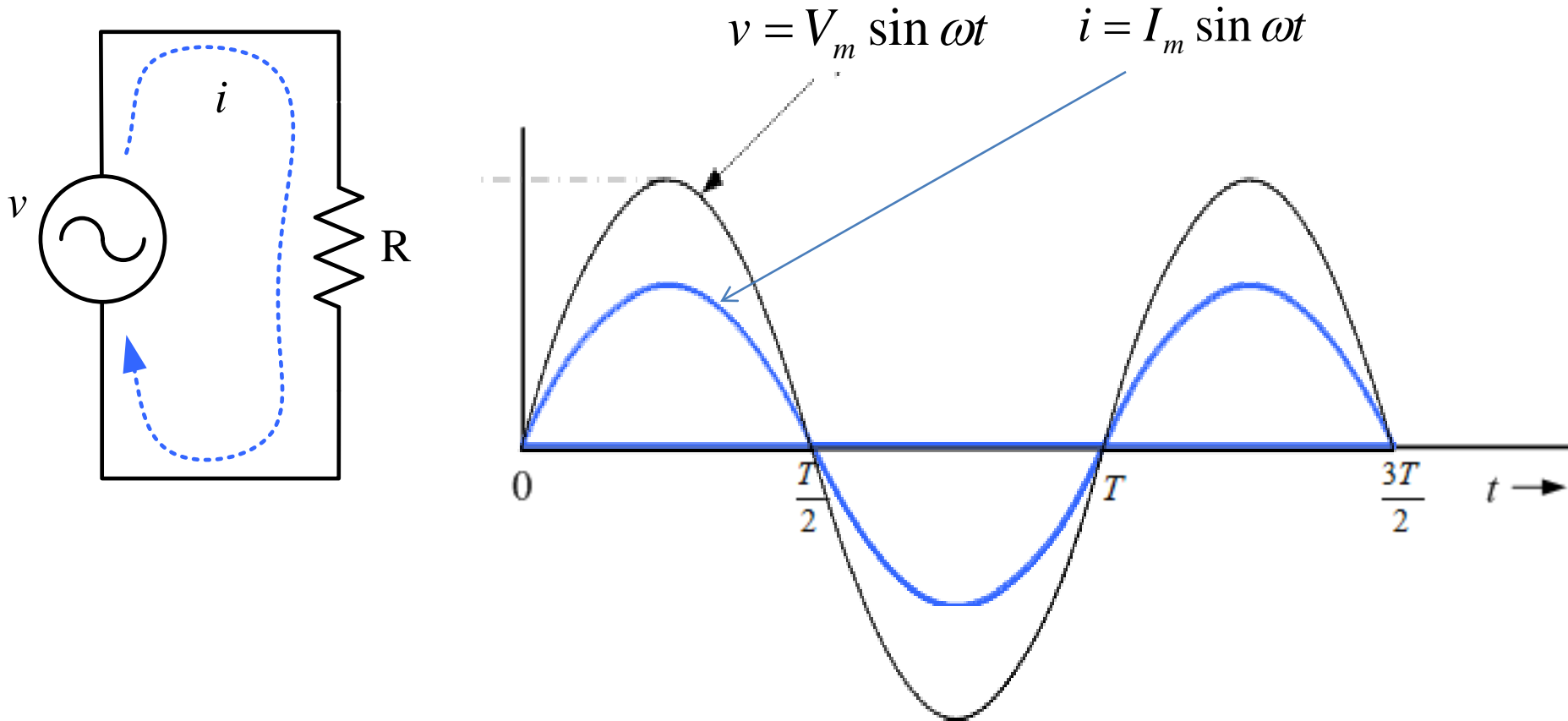

- Voltage and current signals are in the same phase
- They do not have any phase angle difference
- They have same frequency

# AC circuit operation with R

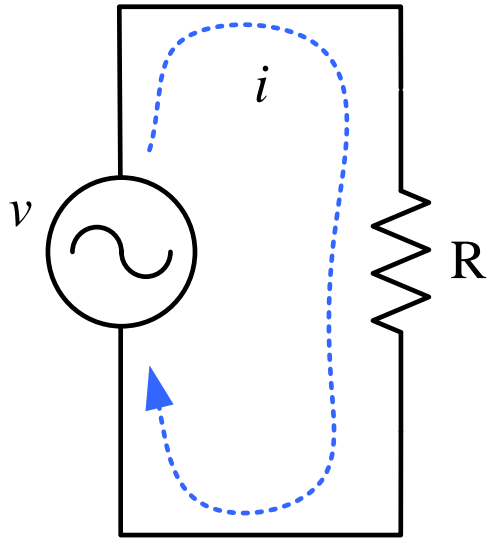

$$v = V_m \sin \omega t \quad i = I_m \sin \omega t$$

- Voltage and current signals are in the same phase
- They do not have any phase angle difference
- They have same frequency

## Phasor diagram

Reference phasor  $V_{\text{RMS}}$

Current phasor  $I_{\text{RMS}}$



**Thus, in a resistive circuit, the voltage and current are always in the same phase.**



# AC circuit operation with R

---

$$v = V_m \sin \omega t \quad i = I_m \sin \omega t$$

## Instantaneous power

$$p = v \times i$$

$$p = V_m \sin \omega t \times I_m \sin \omega t$$

$$p = V_m I_m \sin^2 \omega t$$

$$p = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

Thus, in a resistive circuit, the **instantaneous power is also an alternating quantity**, but it varies at **twice the frequency** of the input voltage signal (*note the  $2\omega$  term*).

# AC circuit operation with R

## Average power

$$P = \frac{1}{T} \int_0^T p dt$$

$$P = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} (1 - \cos 2\omega t) dt$$

$$P = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \left( 1 - \cos 2 \frac{2\pi}{T} t \right) dt$$

$$P = \frac{V_m I_m}{2T} \int_0^T \left( 1 - \cos \frac{4\pi}{T} t \right) dt$$

$$P = \frac{V_m I_m}{2T} \left( t - \frac{T}{4\pi} \sin \frac{4\pi}{T} t \right) \Bigg|_0^T$$

$$p = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

$$P = \frac{V_m I_m}{2T} \left[ \left( T - \frac{T}{4\pi} \sin \frac{4\pi}{T} T \right) - \left( 0 - \frac{T}{4\pi} \sin \frac{4\pi}{T} 0 \right) \right]$$

$$P = \frac{V_m I_m}{2T} \left[ \left( T - \frac{T}{4\pi} \sin 4\pi \right) - (0 - 0) \right]$$

Express  $\omega$  as  $\omega = 2\pi/T$

$$P = \frac{V_m I_m}{2}$$


$$P = \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}}$$

$$P = V_{RMS} \times I_{RMS}$$

Thus, average power in a purely resistive circuit is equal to the product of the RMS values of voltage and current

# AC circuit operation with inductance

# AC circuit operation with L

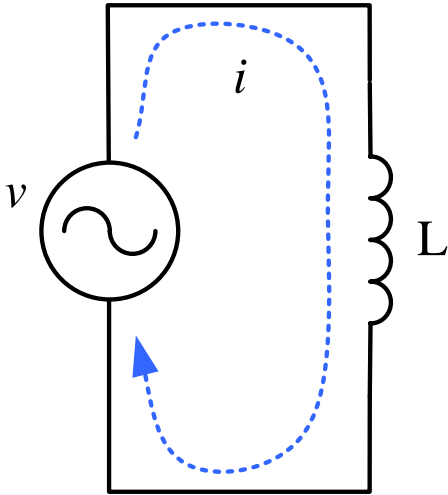

$$v = L \frac{di}{dt} \rightarrow di = \frac{v}{L} dt$$

$$v = V_m \sin \omega t$$

$$i = \int di = \int \frac{v}{L} dt$$

$$i = \frac{1}{L} \int V_m \sin \omega t dt$$


$$i = \frac{V_m}{\omega L} (-\cos \omega t)$$

$$i = \frac{V_m}{\omega L} \sin \left( \omega t - \frac{\pi}{2} \right)$$

$$i = I_m \sin \left( \omega t - \frac{\pi}{2} \right)$$

$I_m = \frac{V_m}{\omega L}$  is peak value of the current

# AC circuit operation with L

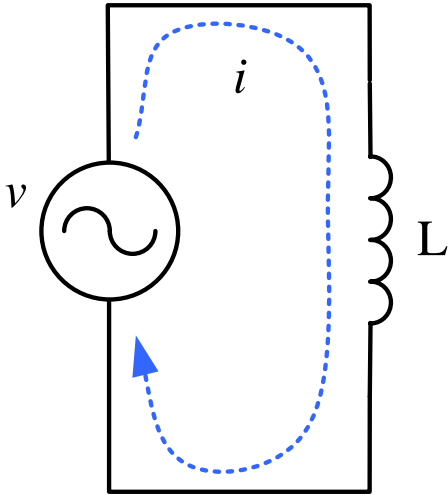

$$v = V_m \sin \omega t$$

$$i = I_m \sin \left( \omega t - \frac{\pi}{2} \right)$$

$$I_m = \frac{V_m}{\omega L}$$

- Thus, the current signal is also a sinusoidal quantity
- Current signal has the same frequency ( $\omega$ ) as the voltage signal
- But as compared to voltage signal, the **current signal is lagging behind** by a phase angle of  $\pi/2$
- Magnitude of the current is determined by the quantity  $\omega L$

# AC circuit operation with L

---

$$v = V_m \sin \omega t$$


$$i = I_m \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$I_m = \frac{V_m}{\omega L} \quad \longrightarrow \quad \omega L = \frac{V_m}{I_m} = \frac{V_m / \sqrt{2}}{I_m / \sqrt{2}} = \frac{V_{RMS}}{I_{RMS}}$$

- The quantity  $\omega L$  in an inductive circuit is the ratio of the RMS values of voltage and current
- It is called **inductive reactance** of the circuit
- Inductive reactance is denoted by the symbol  $X_L$
- Its unit is as usual 'ohm' ( $\Omega$ )


$$X_L = \omega L = 2\pi fL$$

# AC circuit operation with L

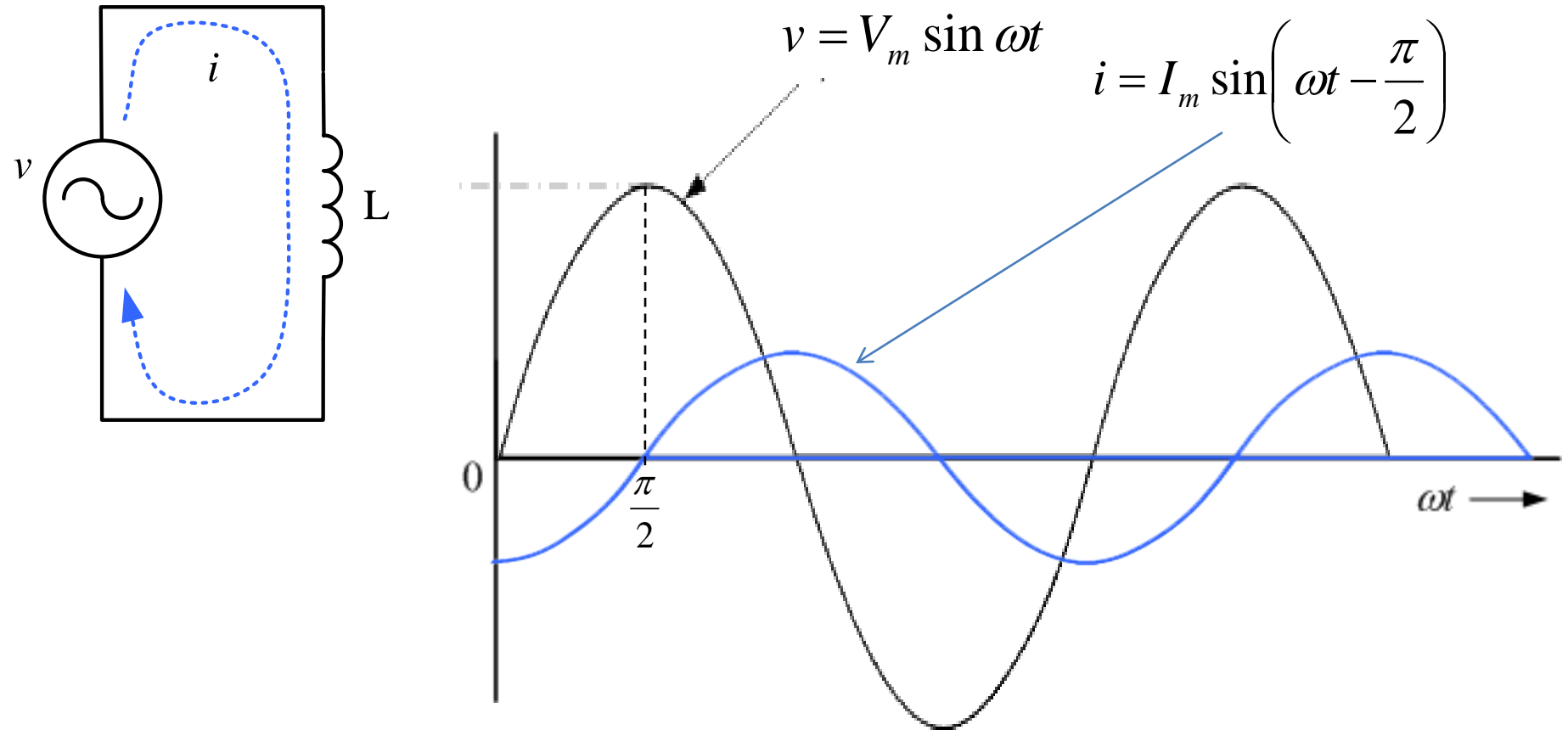

- The current lags behind the voltage by a phase angle of  $90^\circ$
- They have same frequency

# AC circuit operation with L

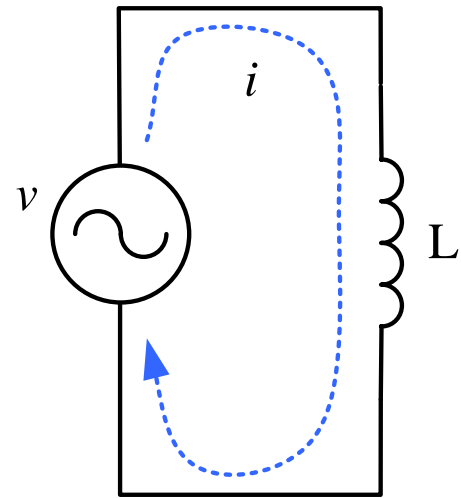

$$v = V_m \sin \omega t \quad i = I_m \sin \left( \omega t - \frac{\pi}{2} \right)$$

- The current lags behind the voltage by a phase angle of  $90^\circ$

## Phasor diagram

Reference phasor  $V_{\text{RMS}}$

Current phasor  $I_{\text{RMS}}$



Thus, in a purely inductive circuit, the current lags behind the voltage by a phase angle of  $90^\circ$ , or in other words, the voltage leads ahead of the current by a phase angle of  $90^\circ$ .



# AC circuit operation with L

---

$$v = V_m \sin \omega t \quad i = I_m \sin \left( \omega t - \frac{\pi}{2} \right)$$

## Instantaneous power

$$p = v \times i$$

$$p = V_m \sin \omega t \times I_m \sin \left( \omega t - \frac{\pi}{2} \right)$$

$$p = -V_m I_m \sin \omega t \cos \omega t$$

$$p = -\frac{V_m I_m}{2} \sin 2\omega t$$

Thus, in an inductive circuit also the **instantaneous power is an alternating quantity**, but it varies at **twice the frequency** of the input voltage signal (*note the  $2\omega$  term*).

# AC circuit operation with L

## Average power

$$P = \frac{1}{T} \int_0^T p dt$$

$$P = \frac{1}{T} \int_0^T -\frac{V_m I_m}{2} \sin 2\omega t dt$$

$$P = -\frac{V_m I_m}{2T} \int_0^T \sin 2 \frac{2\pi}{T} t dt$$

$$P = -\frac{V_m I_m}{2T} \times (-) \frac{T}{4\pi} \times \left( \cos \frac{4\pi}{T} t \right) \Bigg|_0^T$$

$$p = -\frac{V_m I_m}{2} \sin 2\omega t$$

$$P = \frac{V_m I_m}{8\pi} \times \left( \cos \frac{4\pi}{T} T - \cos \frac{4\pi}{T} 0 \right)$$

$$P = \frac{V_m I_m}{8\pi} \times (\cos 4\pi - \cos 0)$$

Express  $\omega$  as  $\omega = 2\pi/T$

$$P = \frac{V_m I_m}{8\pi} \times (\cos 4\pi - \cos 0)$$

$$P = \frac{V_m I_m}{8\pi} \times 0$$


$$P = 0$$

Thus, **average active power consumed by a purely inductive circuit is zero**, i.e. a **purely inductive circuit does not take any active power**.

# AC circuit operation with capacitance

# AC circuit operation with C

---

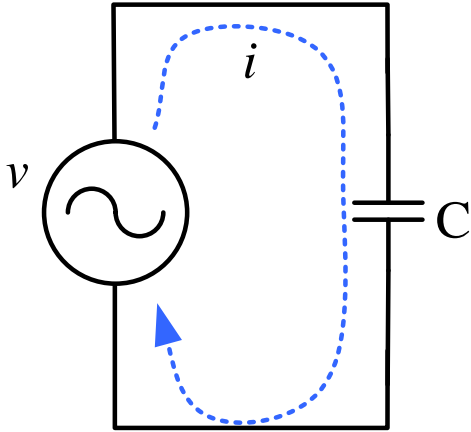

$$i = C \frac{dv}{dt}$$

$$v = V_m \sin \omega t$$

$$i = C \frac{d}{dt} (V_m \sin \omega t)$$


$$i = V_m \omega C \cos \omega t$$

$$i = V_m \omega C \sin \left( \omega t + \frac{\pi}{2} \right)$$

$$i = I_m \sin \left( \omega t + \frac{\pi}{2} \right)$$

$I_m = V_m \omega C$  is peak value of the current

# AC circuit operation with C

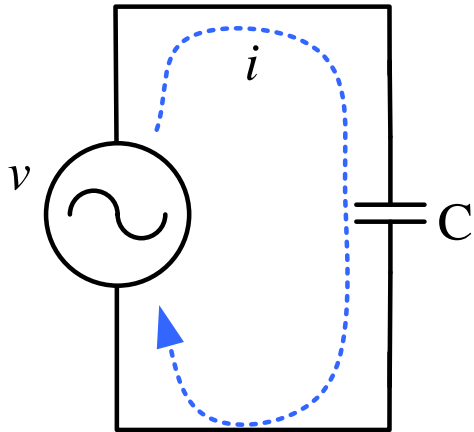

$$v = V_m \sin \omega t$$

$$i = I_m \sin \left( \omega t + \frac{\pi}{2} \right)$$

$$I_m = V_m \omega C$$

- Thus, the current signal is also a sinusoidal quantity
- Current signal has the same frequency ( $\omega$ ) as the voltage signal
- But as compared to voltage signal, the **current signal is leading ahead** by a phase angle of  $\pi/2$
- Magnitude of the current is determined by the quantity  $\omega C$

# AC circuit operation with C

$$v = V_m \sin \omega t$$


$$i = I_m \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$I_m = V_m \omega C \quad \longrightarrow \quad \frac{1}{\omega C} = \frac{V_m}{I_m} = \frac{V_m / \sqrt{2}}{I_m / \sqrt{2}} = \frac{V_{RMS}}{I_{RMS}}$$

- The quantity  $(1/\omega C)$  in a capacitive circuit is the ratio of the RMS values of voltage and current
- It is called **Capacitive reactance** of the circuit
- Capacitive reactance is denoted by the symbol  $X_c$
- Its unit is as usual 'ohm' ( $\Omega$ )


$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

# AC circuit operation with C

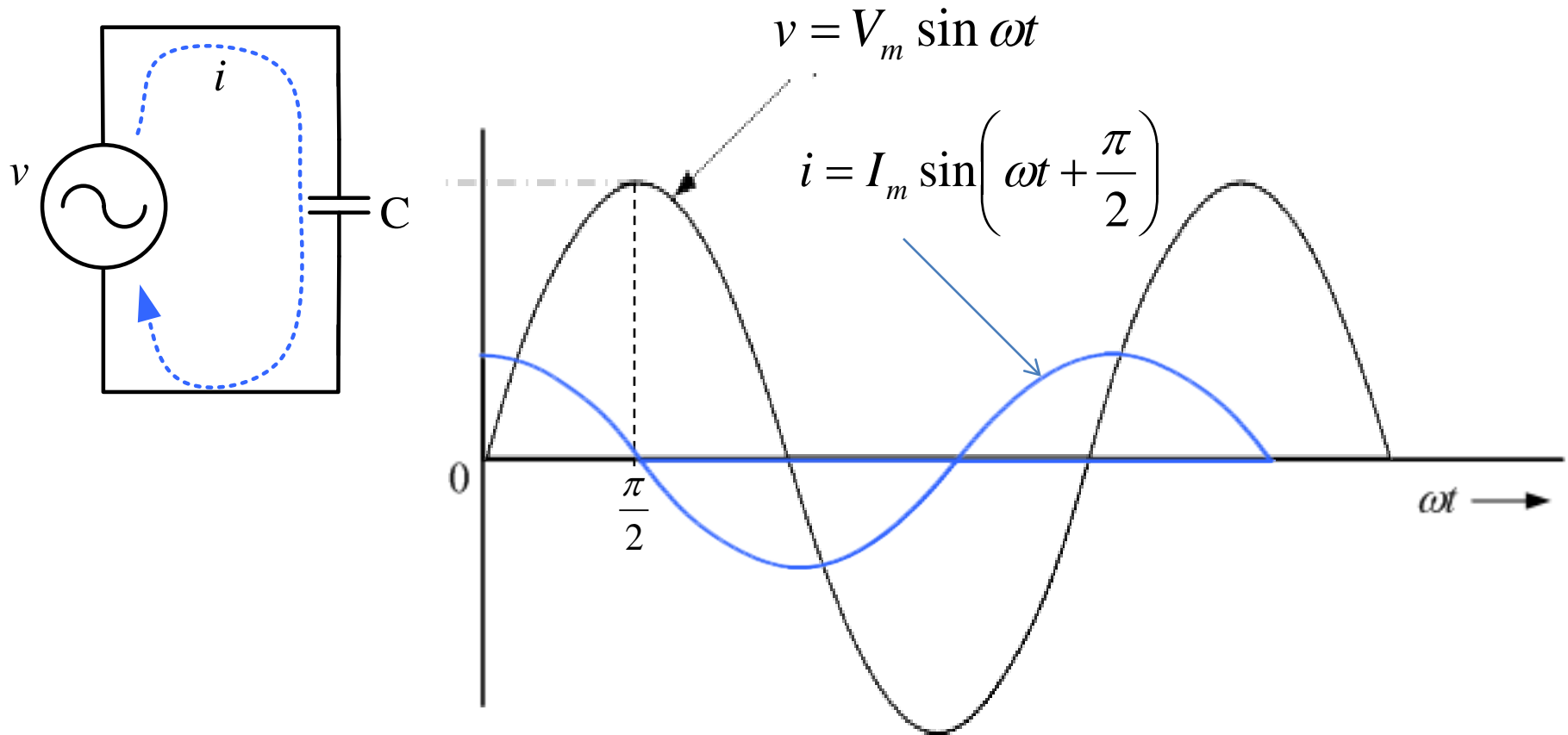

- The current leads ahead of the voltage by a phase angle of  $90^\circ$
- They have same frequency

# AC circuit operation with C

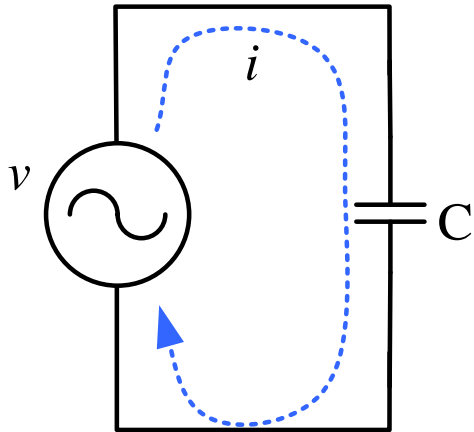

$$v = V_m \sin \omega t \quad i = I_m \sin \left( \omega t + \frac{\pi}{2} \right)$$

- The current leads ahead of the voltage by a phase angle of  $90^\circ$

## Phasor diagram

Reference phasor  $V_{\text{RMS}}$

Current phasor  $I_{\text{RMS}}$



**Thus, in a purely capacitive circuit, the current leads ahead of the voltage by a phase angle of  $90^\circ$ , or in other words, the voltage lags behind the current by a phase angle of  $90^\circ$ .**



# AC circuit operation with C

---

$$v = V_m \sin \omega t \quad i = I_m \sin \left( \omega t + \frac{\pi}{2} \right)$$

## Instantaneous power

$$p = v \times i$$

$$p = V_m \sin \omega t \times I_m \sin \left( \omega t + \frac{\pi}{2} \right)$$

$$p = \frac{V_m I_m}{2} \sin 2\omega t$$

$$p = V_m I_m \sin \omega t \cos \omega t$$

Thus, in a capacitive circuit also the **instantaneous power is an alternating quantity**, but it varies at **twice the frequency** of the input voltage signal (*note the  $2\omega$  term*).

# AC circuit operation with C

## Average power

$$P = \frac{1}{T} \int_0^T p dt$$

$$P = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \sin 2\omega t dt$$

$$P = \frac{V_m I_m}{2T} \int_0^T \sin 2 \frac{2\pi}{T} t dt$$

$$P = \frac{V_m I_m}{2T} \times (-) \frac{T}{4\pi} \times \left( \cos \frac{4\pi}{T} t \right) \Big|_0^T$$

$$p = \frac{V_m I_m}{2} \sin 2\omega t$$

$$P = -\frac{V_m I_m}{8\pi} \times \left( \cos \frac{4\pi}{T} T - \cos \frac{4\pi}{T} 0 \right)$$

$$P = -\frac{V_m I_m}{8\pi} \times (\cos 4\pi - \cos 0)$$

$$P = -\frac{V_m I_m}{8\pi} \times (1 - 1)$$

$$P = -\frac{V_m I_m}{8\pi} \times 0$$

$$P = 0$$

Thus, like in a purely inductive circuit, the **average active power consumed by a purely capacitive circuit is also zero**, i.e. a **purely capacitive circuit does not take any active power**.