

# AC Fundamentals

---

Day 15

## Parallel Resonance

# ILOs – Day 15

---

- Investigate resonance condition in parallel RLC circuit
  - Determine the condition for parallel resonance
  - Identify the circuit conditions under parallel resonance
  - Plot the impedance and current variation profile under parallel resonance
  - Obtain expression for Quality factor of a parallel resonating circuit


# Resonance

---

- Resonance in electrical circuits is a particular condition of the circuit when
  - The circuit impedance become maximum or minimum
  - The current in the circuit is minimum or maximum
  - The effective power factor of the circuit becomes unity
- The phenomenon of resonance is observed in both series and parallel AC circuits comprising of R, L, and C
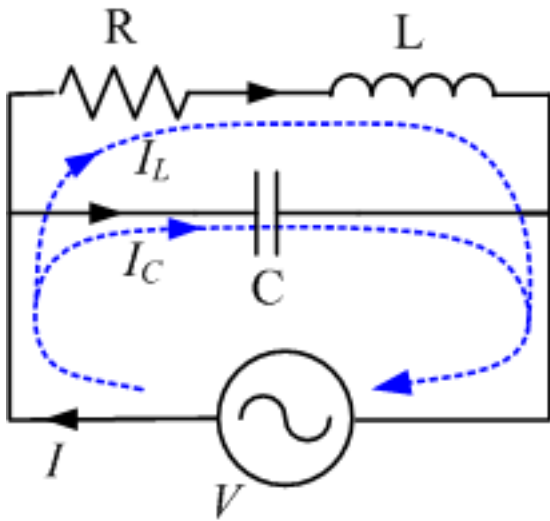
# Parallel Resonance

- Parallel resonance condition can occur in an AC circuit containing a practical coil ( $L$  in series with its inherent  $R$ ), in parallel with a  $C$  and connected across an AC source




According to KCL

$$\bar{I} = \bar{I}_L + \bar{I}_C$$


Phasor diagram

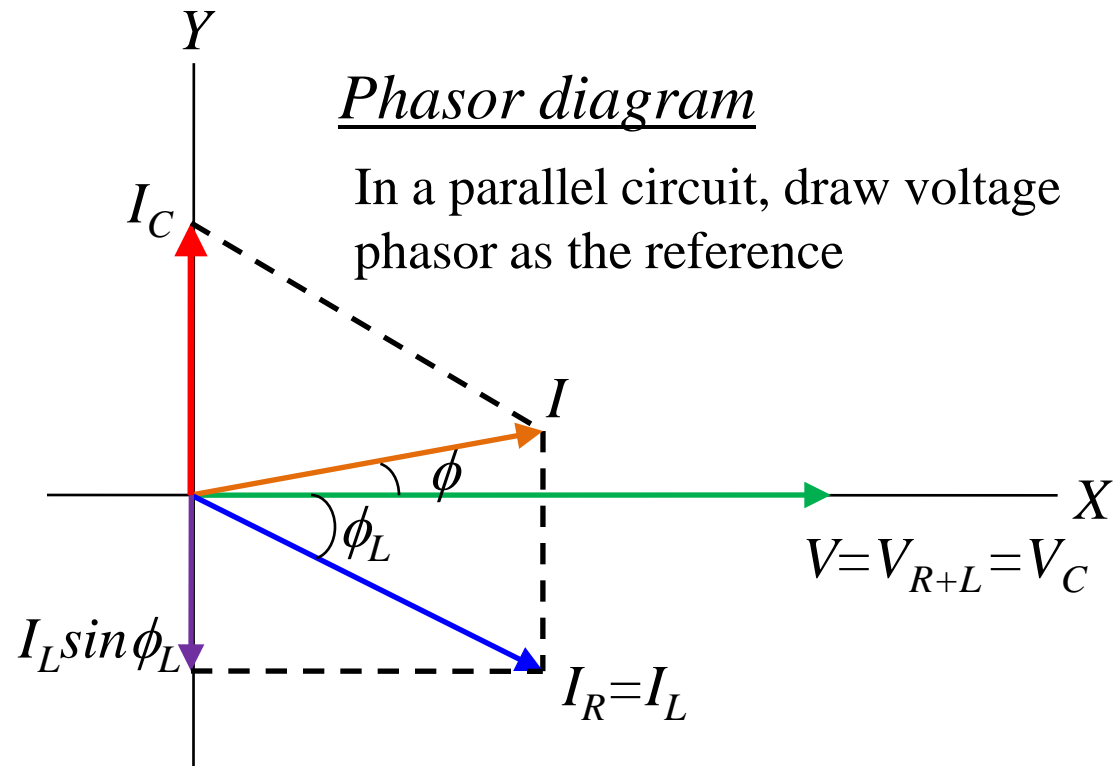In a parallel circuit, draw voltage phasor as the reference


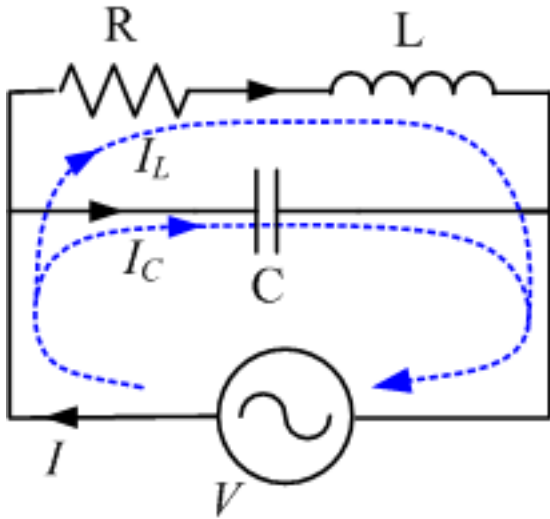
# Parallel Resonance


- Parallel resonance condition can occur in an AC circuit containing a practical coil ( $L$  in series with its inherent  $R$ ), in parallel with a  $C$  and connected across an AC source



In this case  $I_C > I_L \sin \phi_L$


The circuit is predominantly capacitive

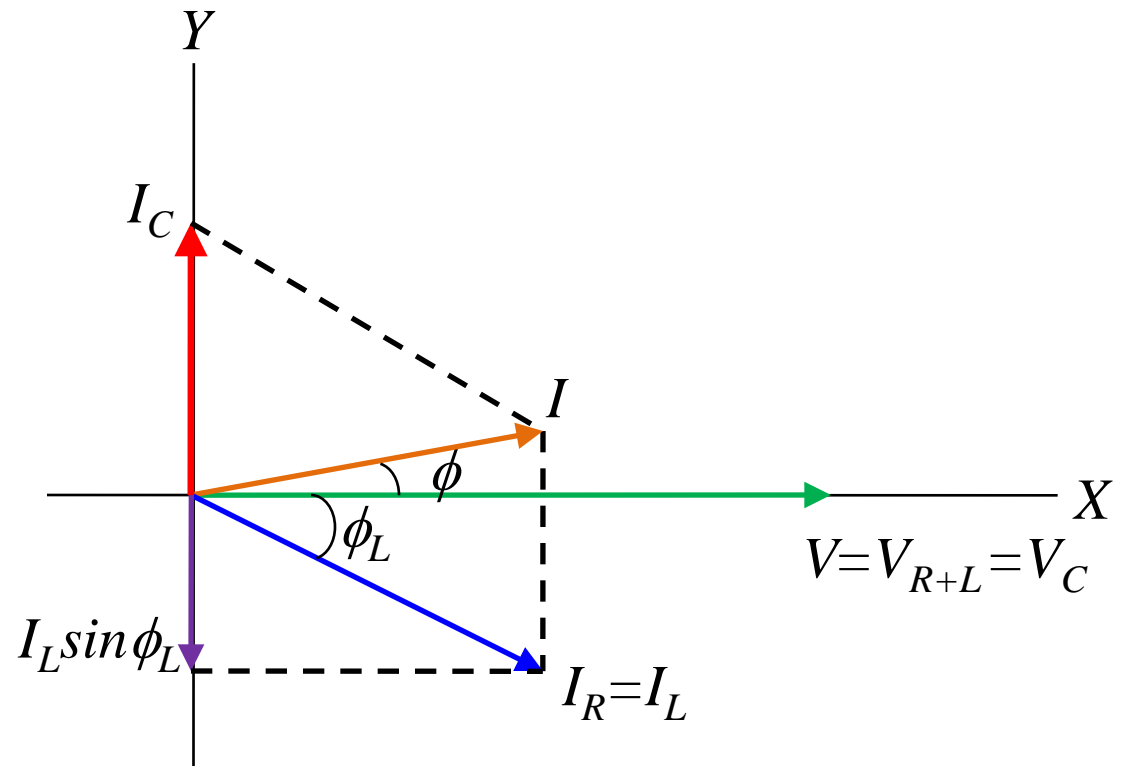Supply current  $I$  leads supply voltage  $V$


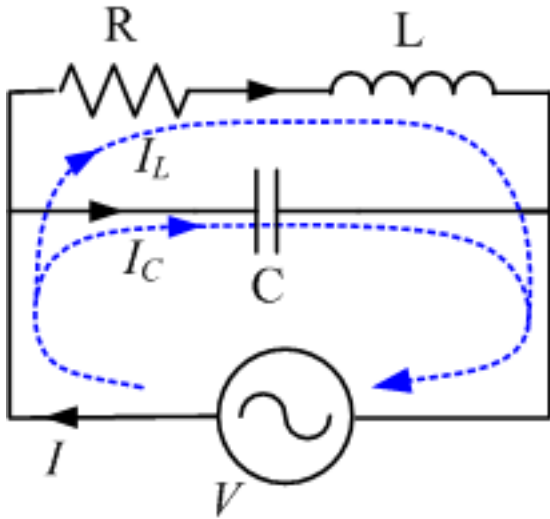
# Parallel Resonance


- Parallel resonance condition can occur in an AC circuit containing a practical coil ( $L$  in series with its inherent  $R$ ), in parallel with a  $C$  and connected across an AC source



In the case when  $I_C < I_L \sin \phi_L$


The circuit is predominantly inductive

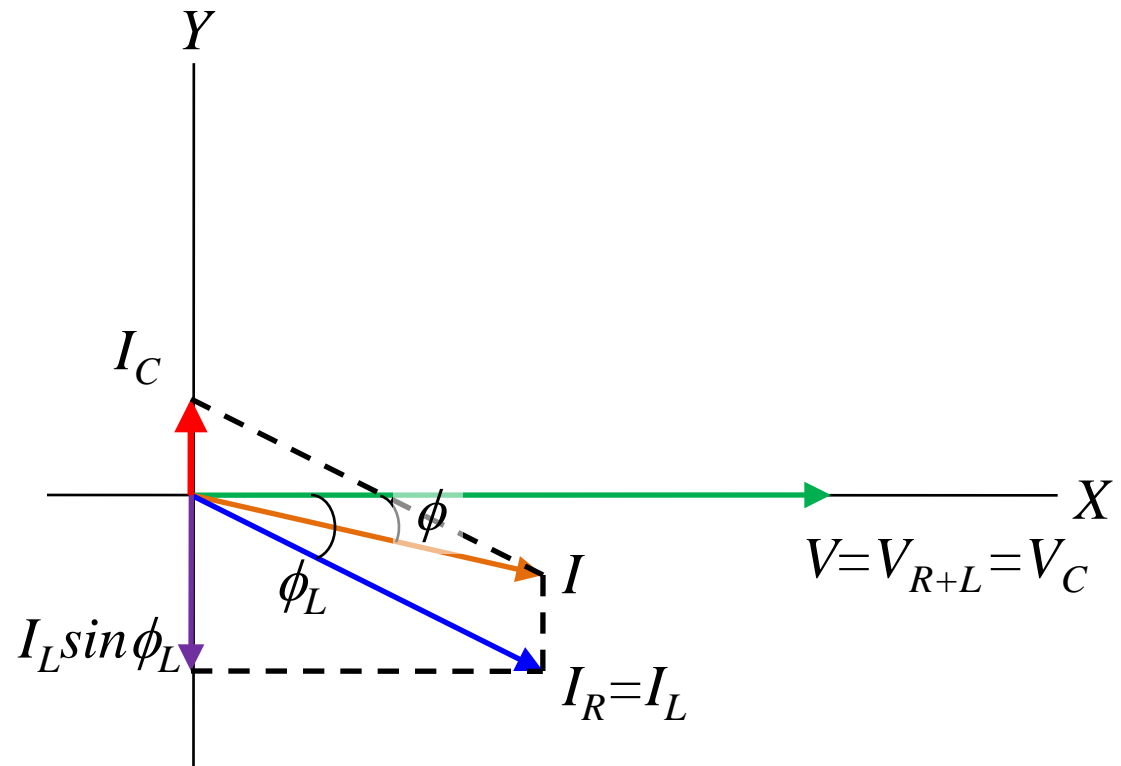Supply current  $I$  lags supply voltage  $V$



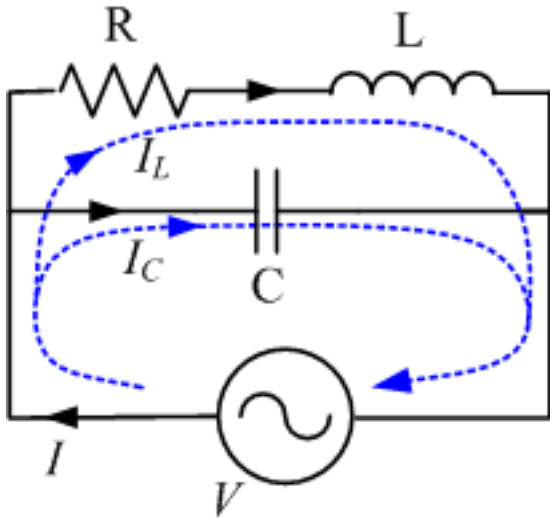
# Parallel Resonance

- Parallel resonance condition can occur in an AC circuit containing a practical coil ( $L$  in series with its inherent  $R$ ), in parallel with a  $C$  and connected across an AC source




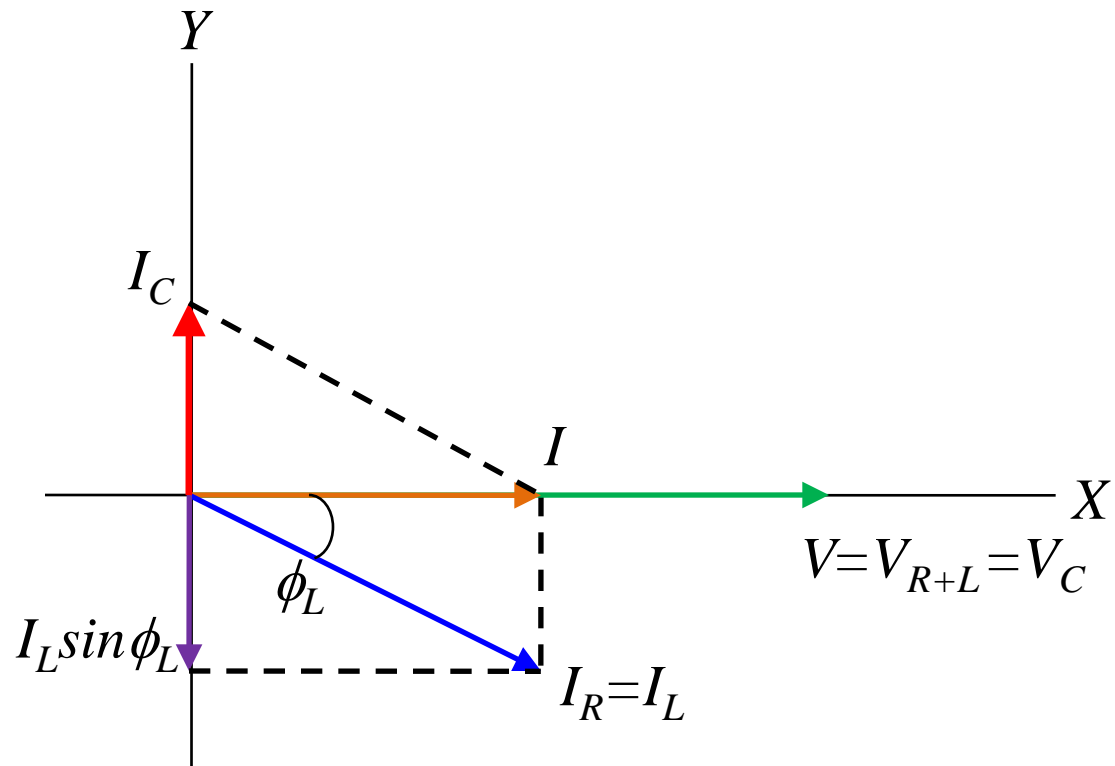In the case when  $I_C = I_L \sin \phi_L$   
Supply current  $I$  is in the same phase as the supply voltage  $V$


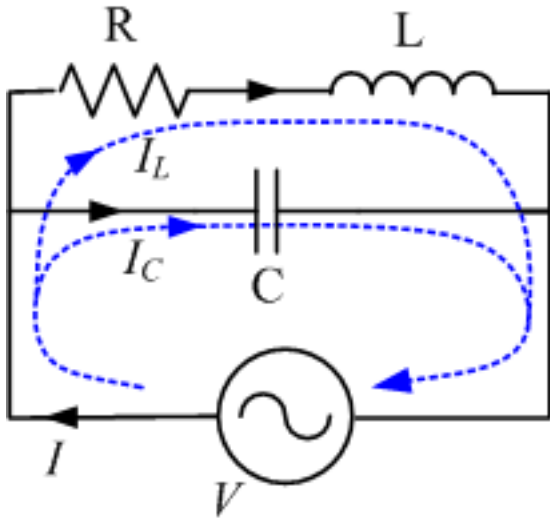
# Parallel Resonance

- Parallel resonance condition can occur in an AC circuit containing a practical coil ( $L$  in series with its inherent  $R$ ), in parallel with a  $C$  and connected across an AC source




In the case when  $I_C = I_L \sin \phi_L$

Supply current  $I$  is in the same phase as the supply voltage  $V$

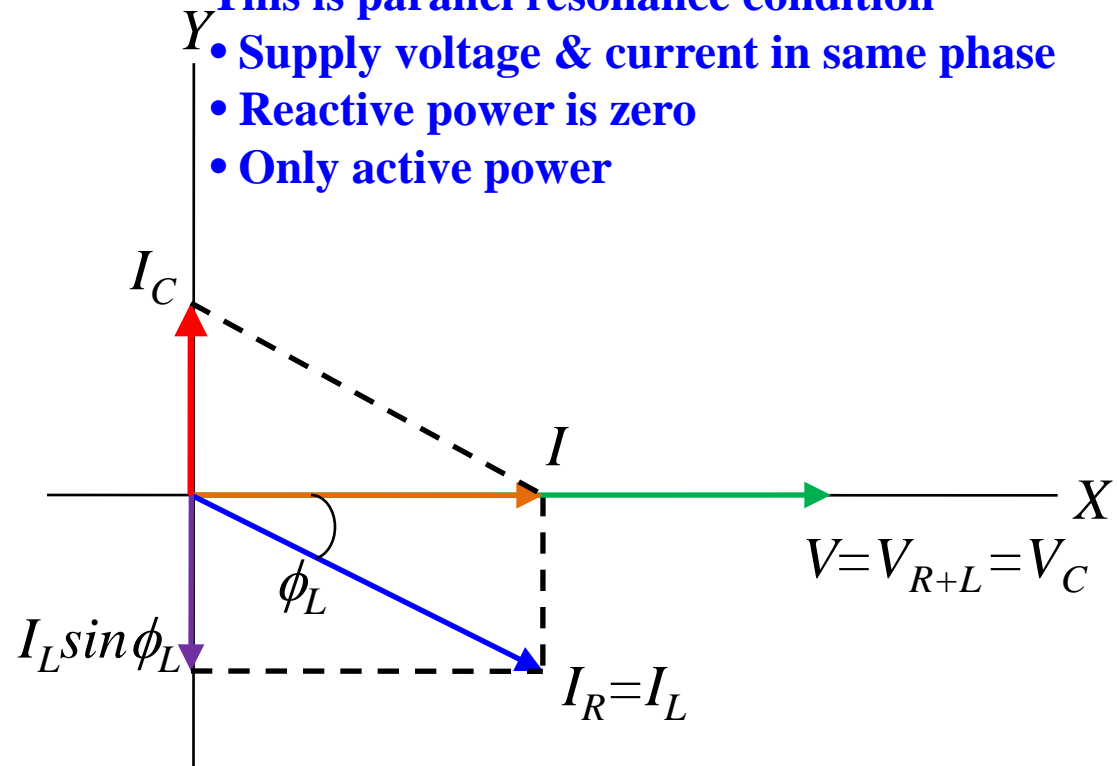**This is parallel resonance condition**


- Supply voltage & current in same phase**
- Reactive power is zero**
- Only active power**





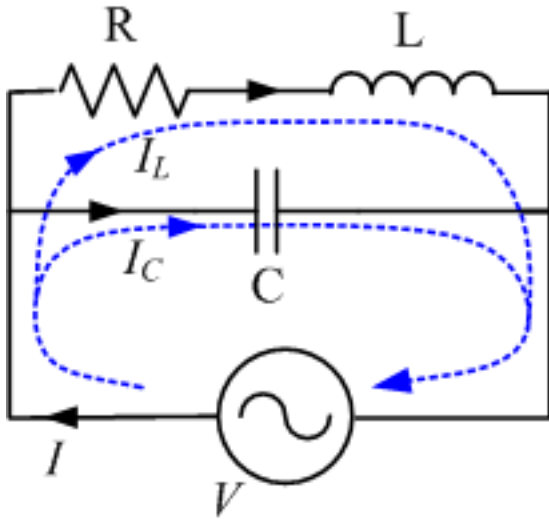
# Parallel Resonance

- Parallel resonance condition  $I_C = I_L \sin \phi_L$
- Draw the impedance triangle of the R-L branch



$$Z_{RL} = \sqrt{R^2 + X_L^2}$$

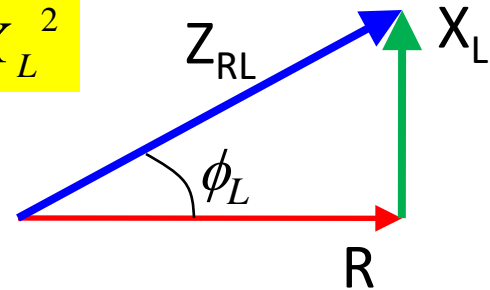

$$I_L = \frac{V}{Z_{RL}}$$

$$\sin \phi_L = \frac{X_L}{Z_{RL}}$$

$$I_C = \frac{V}{X_C}$$

Hence, condition for resonance becomes

$$\frac{V}{X_C} = \frac{V}{Z_{RL}} \times \frac{X_L}{Z_{RL}} \Rightarrow Z_{RL}^2 = X_L \times X_C$$

$$\text{Now, } X_L = \omega L \quad X_C = \frac{1}{\omega C} \quad \Rightarrow Z_{RL}^2 = \omega L \times \frac{1}{\omega C} \quad \Rightarrow Z_{RL}^2 = \frac{L}{C}$$

# Parallel Resonance – resonant Frequency

$$Z_{RL}^2 = \frac{L}{C}$$

$$\Rightarrow R^2 + X_L^2 = \frac{L}{C} \quad \Rightarrow R^2 + (\omega_0 L)^2 = \frac{L}{C}$$

$$\Rightarrow (\omega_0 L)^2 = \frac{L}{C} - R^2 \quad \Rightarrow \omega_0^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\Rightarrow \omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

If the resistance R is negligible, then the resonant frequency becomes:

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad / s}$$


$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

**Note that this expression is same as that for series resonance**
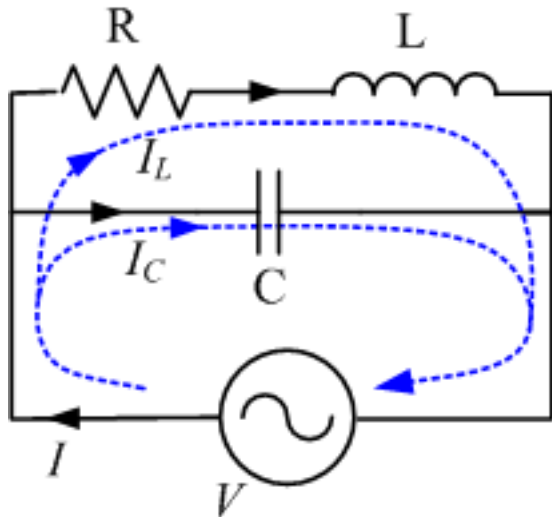
# Parallel Resonance - Mathematically

It is convenient to express admittances in a parallel circuit:

$$\bar{Y}_{RL} = \frac{1}{\bar{Z}_{RL}} = \frac{1}{R + jX_L} = \frac{1}{R + jX_L} \times \frac{R - jX_L}{R - jX_L} = \frac{R}{R^2 + X_L^2} - j \frac{X_L}{R^2 + X_L^2}$$



$$\bar{Y}_C = \frac{1}{\bar{Z}_C} = \frac{1}{-jX_C} = \frac{j}{X_C}$$

$$\begin{aligned} \bar{Y} &= \bar{Y}_{RL} + \bar{Y}_C = \frac{R}{R^2 + X_L^2} - j \frac{X_L}{R^2 + X_L^2} + \frac{j}{X_C} \\ &= \frac{R}{R^2 + X_L^2} + j \left( \frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} \right) \end{aligned}$$

Now, the circuit would be in resonance when the effective total impedance is purely resistive, i.e. *j-component of the complex admittance is zero i.e.:*


$$j \left( \frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} \right) = 0 \Rightarrow \frac{1}{X_C} = \frac{X_L}{R^2 + X_L^2} \Rightarrow X_L \times X_C = R^2 + X_L^2 = Z_{RL}^2$$

**Note that by this method also we are getting the same condition.**
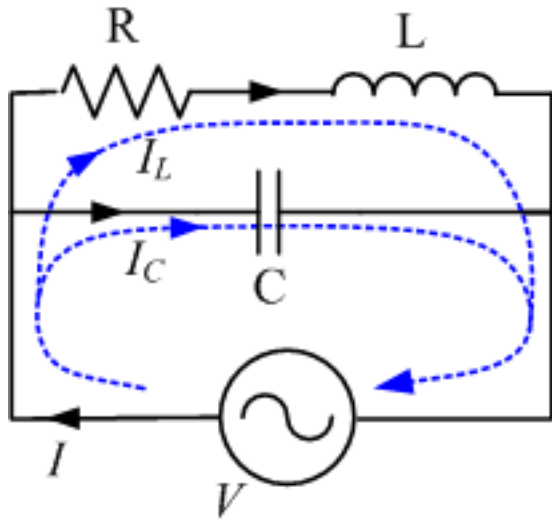
# Parallel Resonance - Mathematically

In terms of susceptance:

$$\bar{Y}_{RL} = \frac{1}{\bar{Z}_{RL}} = \frac{1}{R + jX_L} = \frac{1}{R + jX_L} \times \frac{R - jX_L}{R - jX_L} = \frac{R}{R^2 + X_L^2} - j \frac{X_L}{R^2 + X_L^2} = G_{RL} - jB_{RL}$$



$$\bar{Y}_C = \frac{1}{\bar{Z}_C} = \frac{1}{-jX_C} = \frac{j}{X_C} = G_C + jB_C$$

$$\text{Inductive susceptance: } B_{RL} = \frac{X_L}{R^2 + X_L^2}$$

$$\text{Capacitive susceptance: } B_C = \frac{1}{X_C}$$

Total admittance:

$$\bar{Y} = \bar{Y}_{RL} + \bar{Y}_C = \frac{R}{R^2 + X_L^2} + j \left( \frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} \right) = G_{RL} + j(B_C - B_{RL}) = G + jB$$

The parallel circuit is said to be in resonance when imaginary part of total admittance is zero, i.e.  $B = 0$


**i.e. inductive susceptance = capacitive susceptance**

# Characteristics of Parallel Resonance

Inductive susceptance:  $B_{RL} = -\frac{X_L}{R^2 + X_L^2}$

Neglecting resistance:  $B_{RL} = -\frac{1}{X_L} = -\frac{1}{2\pi fL}$

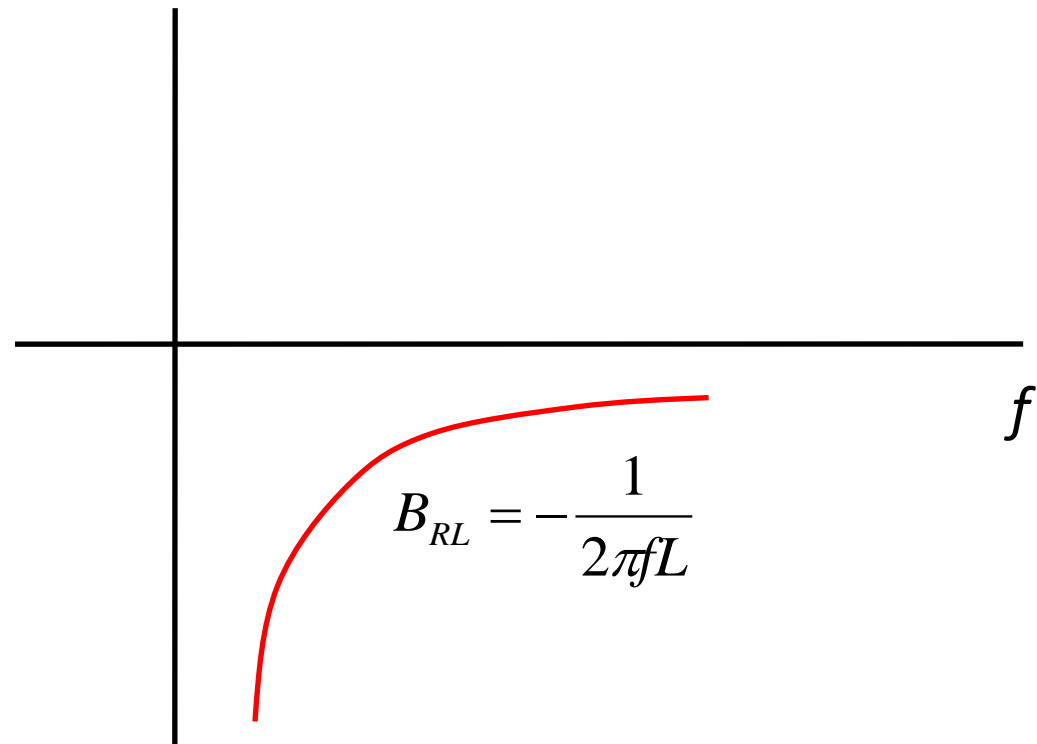
- Thus, it is inversely proportional to the frequency of the applied voltage
- Hence, it is represented by a rectangular hyperbola drawn in the fourth quadrant (it is assumed negative)


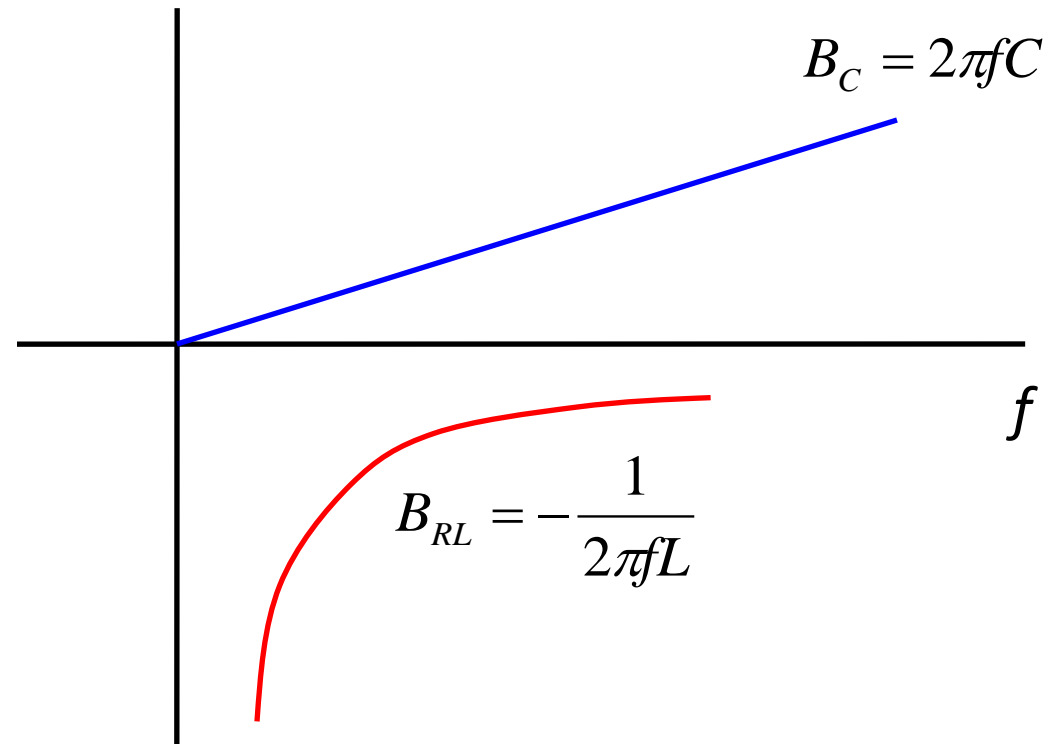
# Characteristics of Parallel Resonance

Capacitive susceptance:  $B_C = \frac{1}{X_C} = \frac{1}{\frac{1}{2\pi fC}} = 2\pi fC$

- Thus, it is directly proportional to the frequency of the applied voltage
- Hence, it is represented by a straight line drawn in the first quadrant passing through the origin



# Characteristics of Parallel Resonance


Total susceptance:  $B = B_C + B_{RL} = 2\pi fC - \frac{1}{2\pi fL}$

- Total susceptance plot will thus be simple addition of the two individual susceptance plots
- It is represented by the dotted hyperbola
- At point A, where  $B_C = B_{RL}$ , the net susceptance  $B$  is zero
- Hence at A, the total admittance is minimum (and equal to the conductance  $G$  only:  $Y = G + B = G + 0 = G$ )
- In other words, impedance is maximum
- **So at point A, line current  $I$  is minimum**
- **This is the resonant frequency  $f_0$**

Current magnitude at resonance:

$$I = \frac{V}{Z} = V \times Y = V \times G = V \times \frac{R}{R^2 + X_L^2} = V \times \frac{R}{Z_{RL}^2}$$

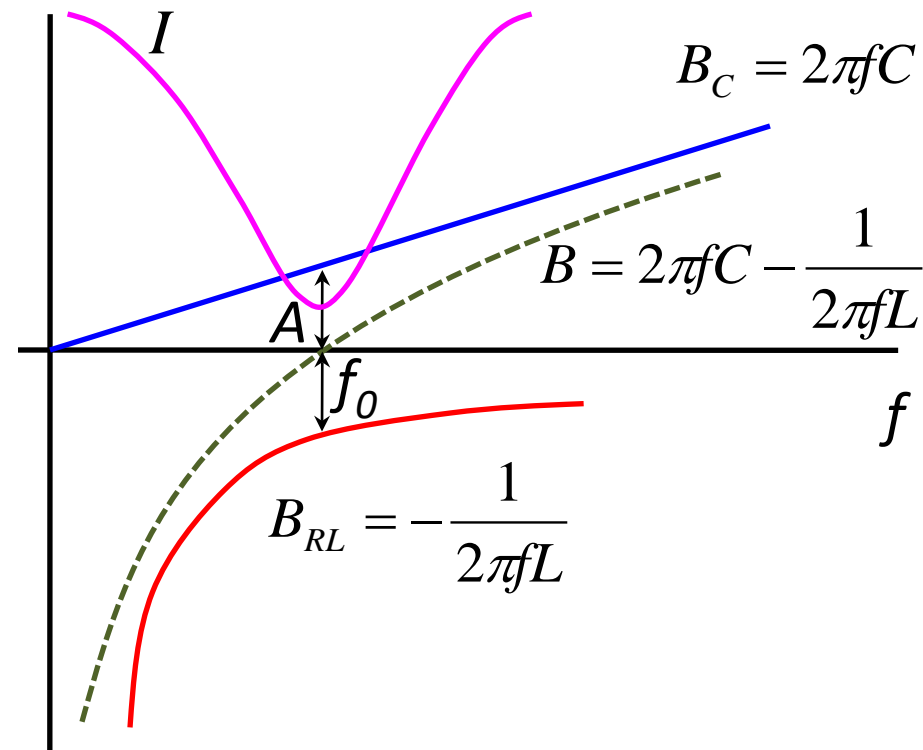Since,  $Z_{RL}^2 = \frac{L}{C} \Rightarrow I = V \times \frac{R}{\frac{L}{C}} = \frac{V}{\frac{L}{CR}}$




# Characteristics of Parallel Resonance

Current magnitude at resonance:

$$I = \frac{V}{L/CR}$$

- The denominator  $L/CR$  is known as the **dynamic impedance of the parallel circuit** at resonance
- It should be noted that impedance is 'resistive' only
- Since current is minimum at resonance,  $L/CR$  must, therefore, represent the *maximum impedance of the circuit*
- In fact, parallel resonance is a condition of maximum impedance or minimum admittance
- At resonant frequency, impedance is maximum and equals  $L/CR$
- Consequently, current at resonance is minimum and is  $I = V / (L/CR)$

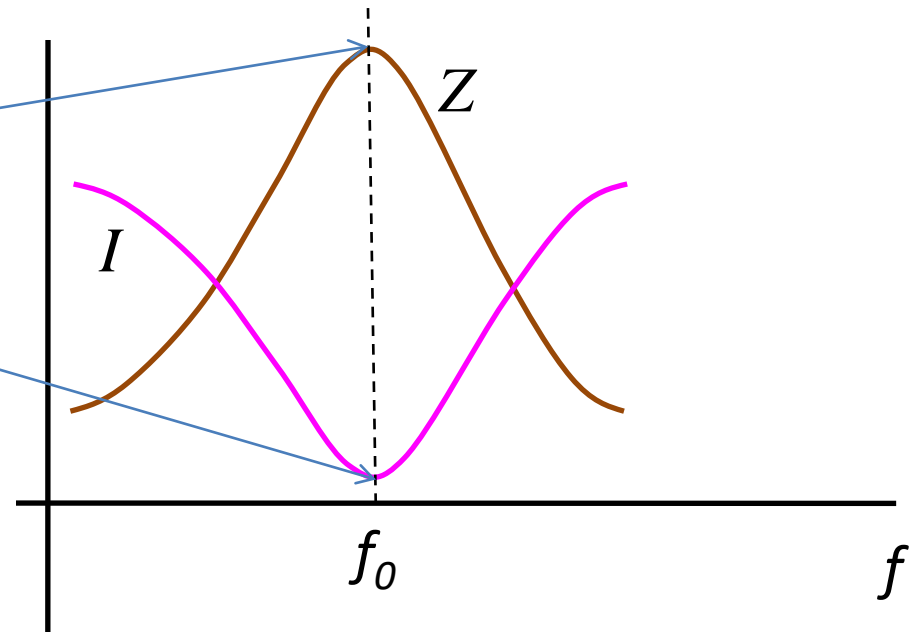



# Resonance in parallel RLC circuit

---

Relation	Remarks
$B_{RL} = B_C$	Inductive susceptance equals capacitive susceptance
$B = B_C - B_{RL} = 0$	Net susceptance is zero
$Y = G + jB = G$	Total admittance equals total conductance
$\begin{aligned} Y  &= \sqrt{G^2 + (B_C - B_{RL})^2} \\ &= \sqrt{G^2 + 0^2} \\ &= G\end{aligned}$	The circuit behaves as a purely resistive circuit with no imaginary part of admittance (or impedance) being present at resonance

# Resonance in parallel RLC circuit

Relation	Remarks
$Z_0 = L/RC$	Dynamic impedance at resonance. The impedance value is maximum at resonance
$I = \frac{V}{L/CR}$	Line current at resonance is minimum and it is purely resistive current, no imaginary part
$\begin{aligned}\phi_0 &= \angle Z_0 = \tan^{-1} \frac{\text{Imag}(Z_0)}{\text{Real}(Z_0)} \\ &= \tan^{-1} \frac{0}{L/RC} \\ &= 0^0\end{aligned}$	The phase angle between supply current and voltage is zero, i.e. current and voltage are in the same phase
$\cos \phi = \cos 0^0 = 1$	The overall circuit power factor is unity

# Q factor (Quality factor)

- In a parallel resonating circuit, the Q-factor is defined the current in any of the two parallel branches to the line current drawn from the supply
- Thus we have the expression for Q-factor as:


$$Q = \frac{I_c}{I}$$

$$\text{Now, } I_c = \frac{V}{X_c} = \frac{V}{1/\omega_0 C} = V\omega_0 C$$

$$\text{And, } I = \frac{V}{Z_0} = \frac{V}{L/RC} = \frac{VRC}{L}$$

$$\therefore \text{Q factor} = Q = \frac{I_c}{I} = \frac{V\omega_0 C}{\frac{VRC}{L}} = \frac{\omega_0 L}{R} = \frac{2\pi f_0 L}{R}$$

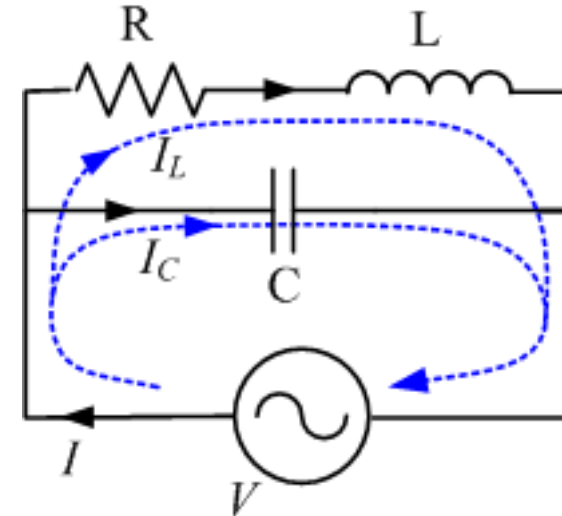This expression is exactly same as in series resonating circuit



Remember the expression for resonating frequency with negligible resistance:

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow Q = \frac{2\pi \frac{1}{2\pi\sqrt{LC}} L}{R} \Rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$