

AC Fundamentals

Day 12


RC circuit

ILOs – Day 12

- For a resistive + capacitive circuit with AC supply:
 - Derive the expression for current and power
 - Draw phasor diagram
- Define active, reactive, and apparent power in AC circuits and obtain their expressions

AC circuit operation
with resistance and
capacitance together

AC circuit operation with R + C

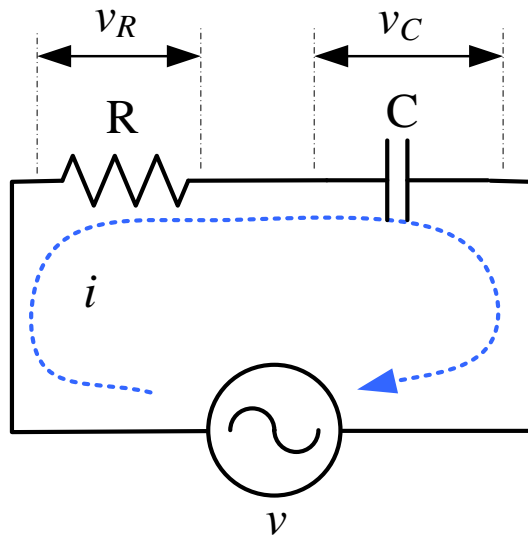


$$v = V_m \sin \omega t$$

Phasor diagram

- To draw the phasor diagram, we take the signals V_{RMS} , I_{RMS} , V_R , V_C
- The RMS value of current I_{RMS} is considered as the reference phasor and it is thus drawn along the X-axis
- *In series circuit, current is common to all the elements, so take current as reference*


AC circuit operation with R + C

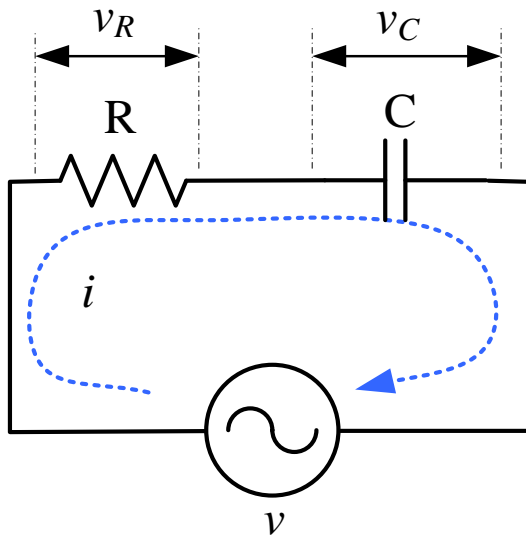


$$v = V_m \sin \omega t$$

Phasor diagram

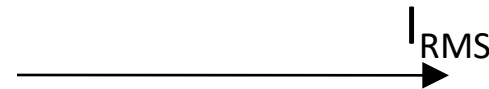- The RMS value of current I_{RMS} is drawn along the X-axis



AC circuit operation with R + C

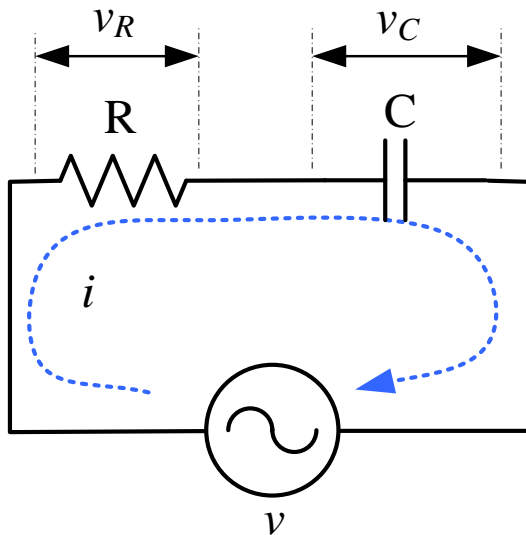


$$v = V_m \sin \omega t$$

Phasor diagram

- Voltage drop across the resistance is
$$V_R = I_{RMS} R$$
- V_R phasor is drawn in the same direction as the current phasor




AC circuit operation with R + C

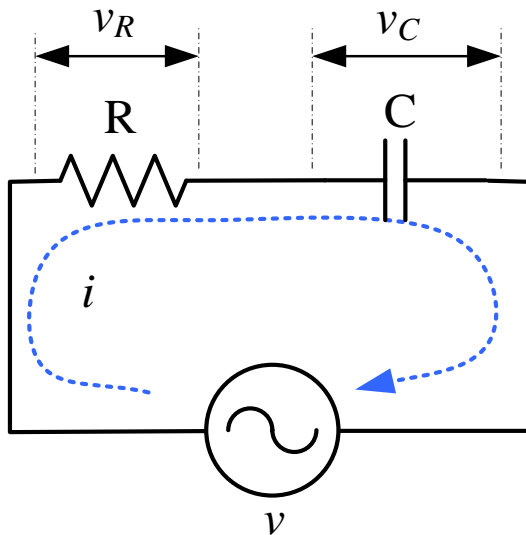


$$v = V_m \sin \omega t$$

Phasor diagram

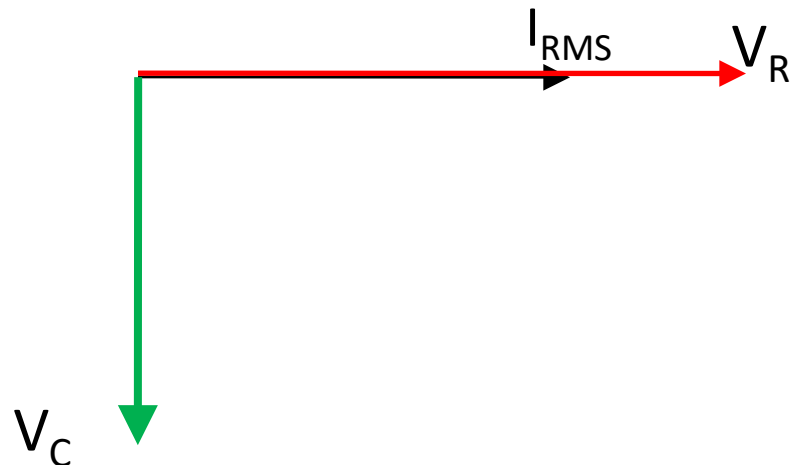- Voltage drop across the capacitor is
$$V_C = I_{RMS} X_C$$
- V_C phasor is drawn 90° lagging to the current phasor
- (*remember, voltage across a capacitor lags the current through it by 90°*)



AC circuit operation with R + C

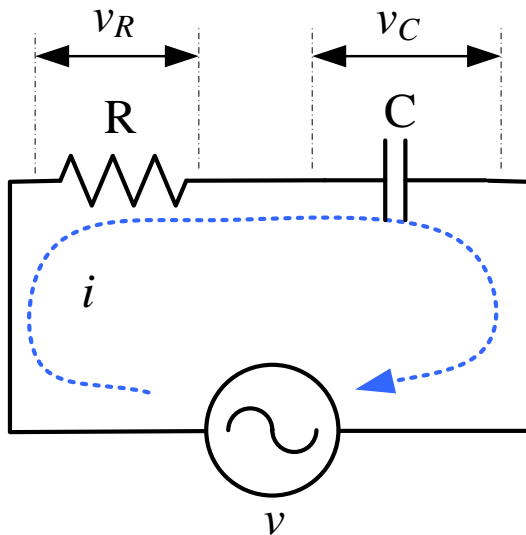


$$v = V_m \sin \omega t$$


Phasor diagram

- According to KVL, the supply voltage must equal summation of the two voltage drops, one across the resistance and the other across the capacitance
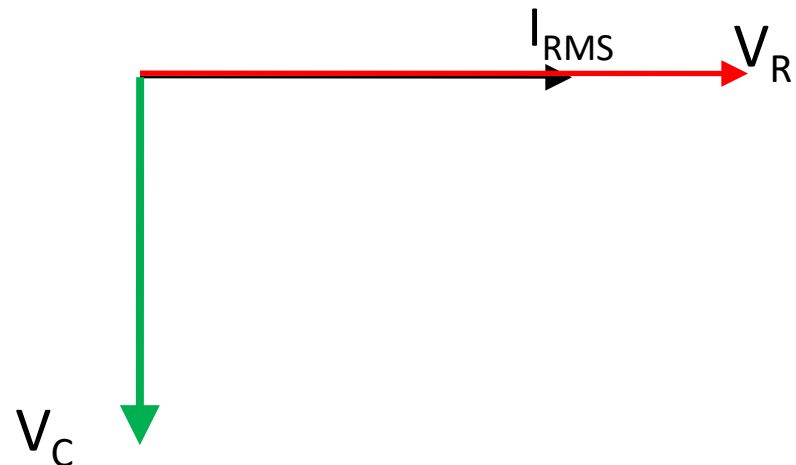
$$\overline{V_{RMS}} = \overline{V_R} + \overline{V_C}$$



AC circuit operation with R + C

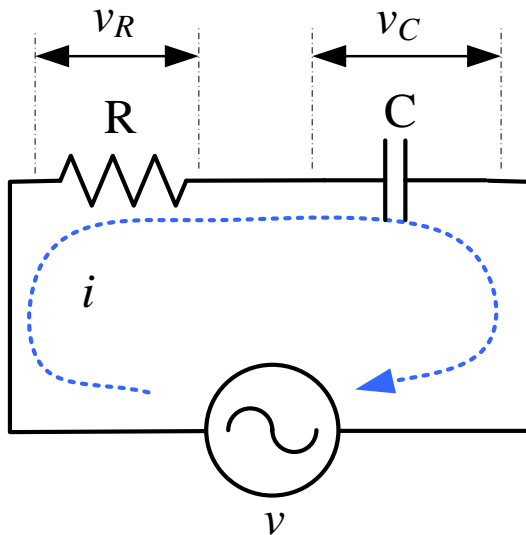


$$v = V_m \sin \omega t$$


Phasor diagram

$$\overline{V_{RMS}} = \overline{V_R} + \overline{V_C}$$

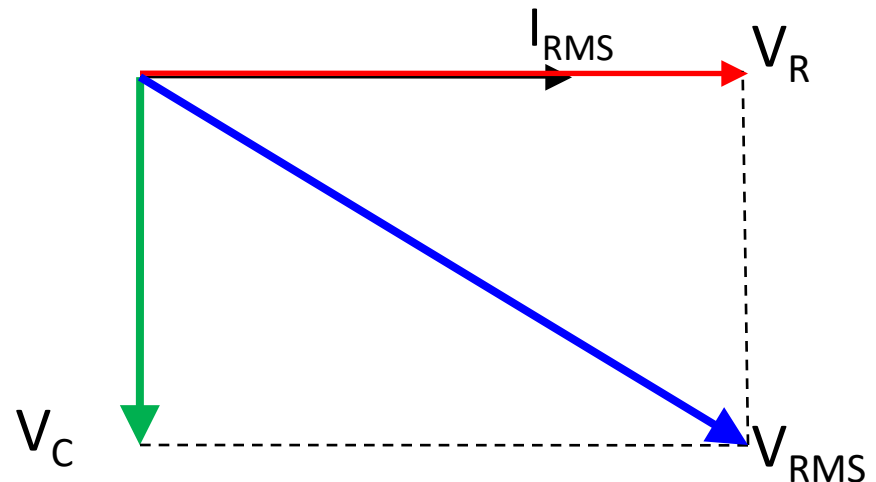- Thus, the supply voltage phasor V_{RMS} is drawn as the vector addition (resultant) of the two phasors V_R and V_C




AC circuit operation with R + C

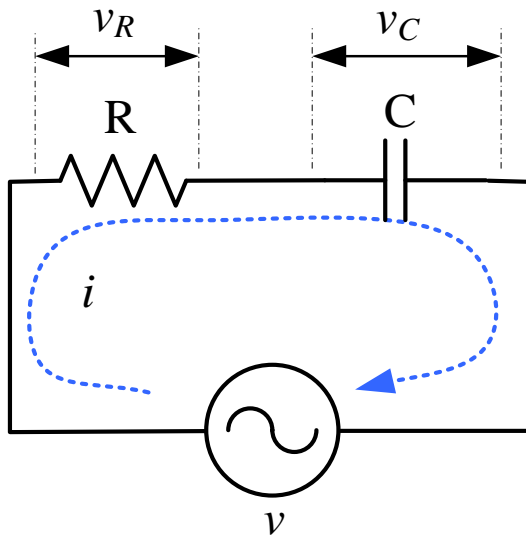


$$v = V_m \sin \omega t$$

Phasor diagram

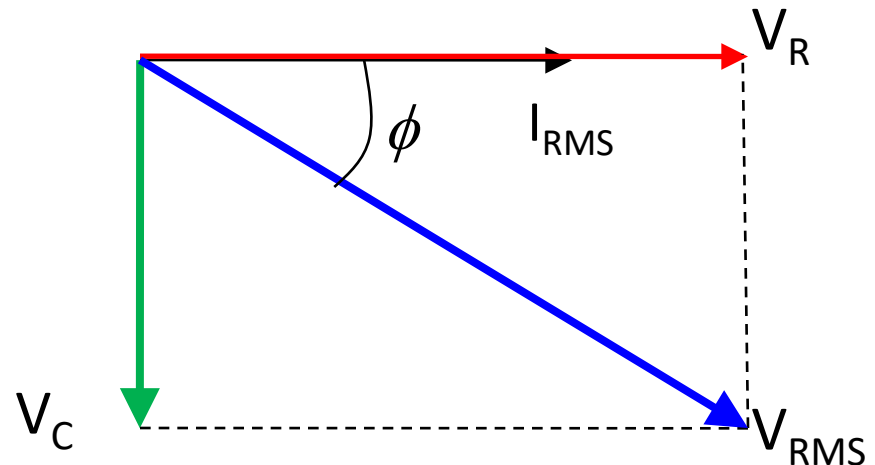- The angle between the supply voltage V_{RMS} phasor and the supply current I_{RMS} phasor is known as the **power factor angle** ϕ



AC circuit operation with R + C

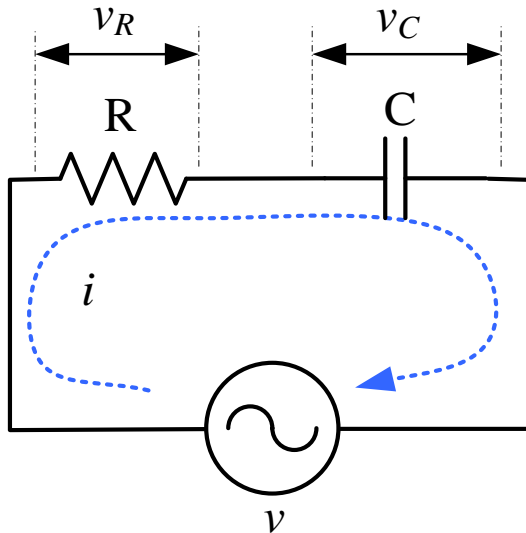


$$v = V_m \sin \omega t$$

Phasor diagram


Value of the power factor angle can be expressed from the phasor diagram as:

$$\phi = \tan^{-1} \left(\frac{V_C}{V_R} \right) = \tan^{-1} \left(\frac{I_{RMS} \times X_C}{I_{RMS} \times R} \right) = \tan^{-1} \left(\frac{X_C}{R} \right)$$
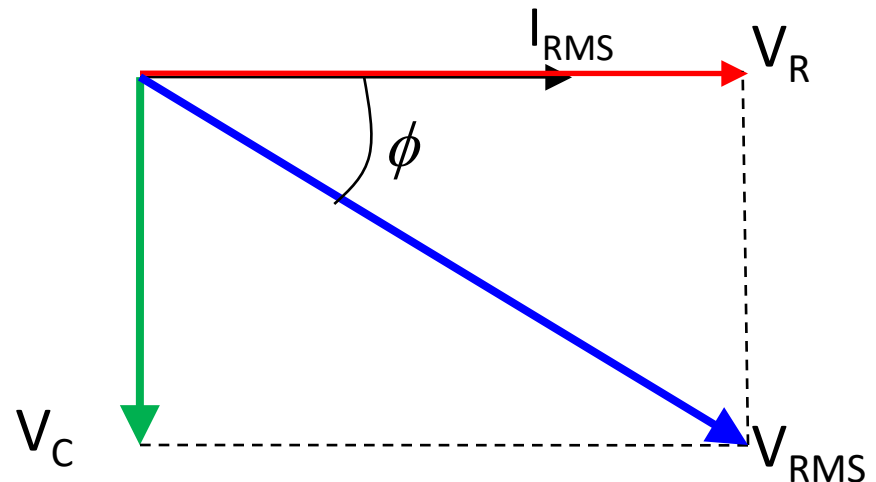
$$\phi = \tan^{-1} \left(\frac{1}{\omega CR} \right)$$




AC circuit operation with R + C

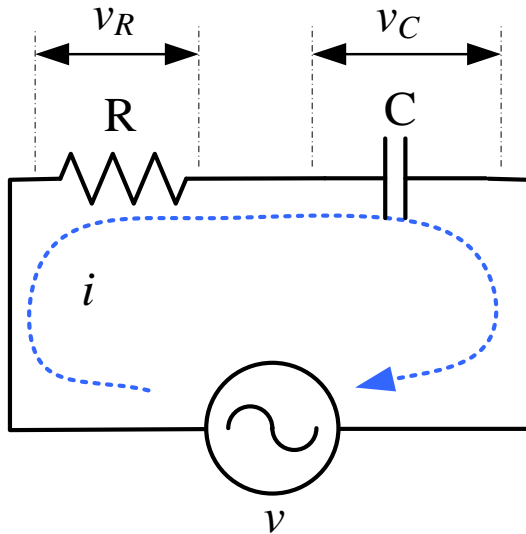



Phasor diagram

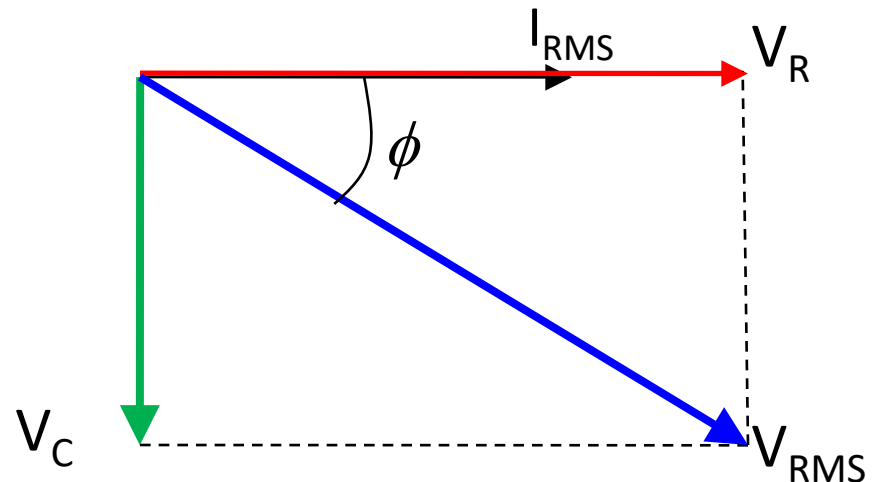Drawing only the voltage phasors from the phasor diagram we obtain the so-called **voltage triangle** of a series R-C circuit:



AC circuit operation with R + C

Voltage triangle

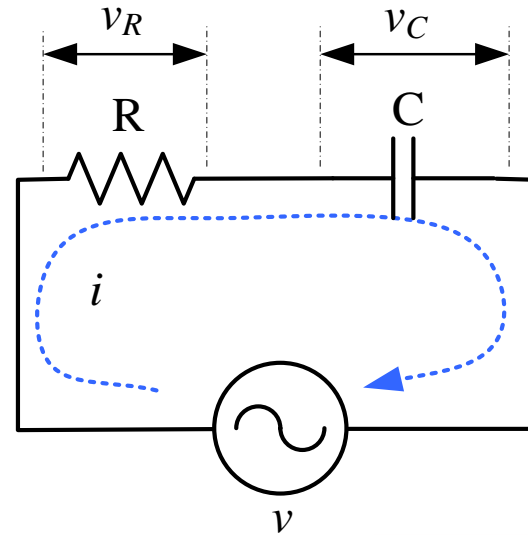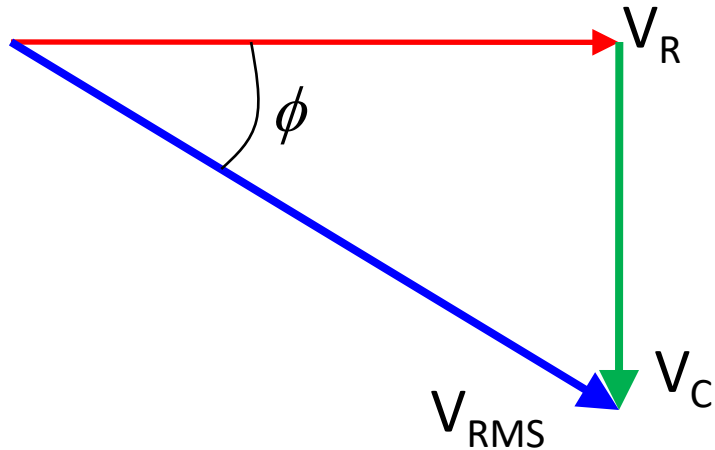

From the voltage triangle we have the relation:

$$V_{RMS} = \sqrt{V_R^2 + V_C^2}$$


$$V_{RMS} = \sqrt{(I_{RMS} R)^2 + (I_{RMS} X_C)^2}$$

$$V_{RMS} = I_{RMS} \sqrt{R^2 + X_C^2}$$


$$\frac{V_{RMS}}{I_{RMS}} = \sqrt{R^2 + X_C^2}$$

AC circuit operation with R + C

Voltage triangle

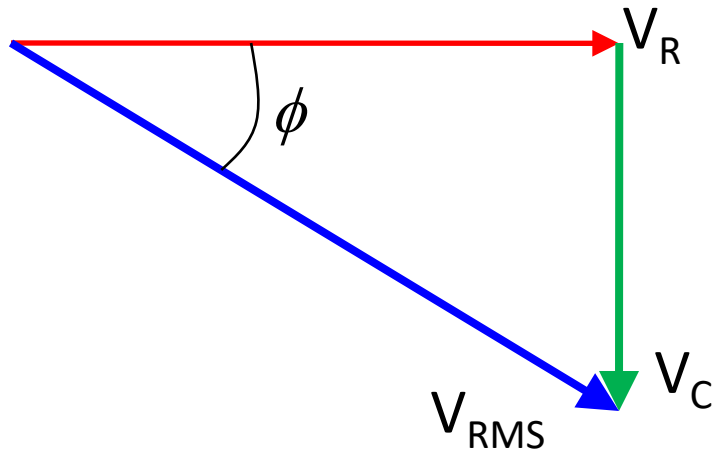
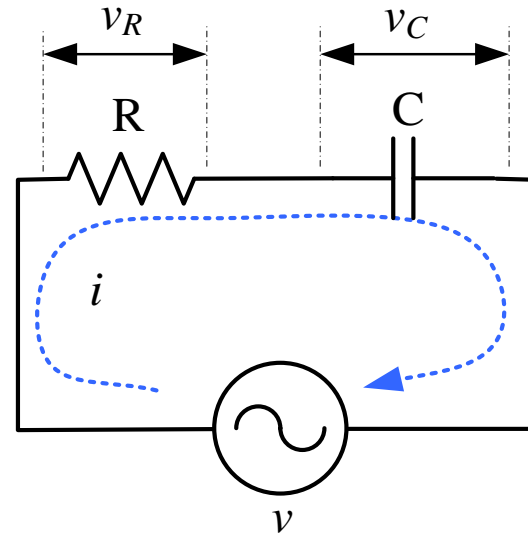
$$\frac{V_{RMS}}{I_{RMS}} = \sqrt{R^2 + X_C^2}$$



$$\frac{V_{RMS}}{I_{RMS}} = \sqrt{R^2 + X_C^2} = Z$$


This ratio of V_{RMS} and I_{RMS} in a series R-C circuit is called **impedance** of the circuit that has a magnitude

$$Z = \sqrt{R^2 + X_C^2}$$

The unit of impedance is “Ohm” (Ω).

AC circuit operation with R + C

Voltage triangle

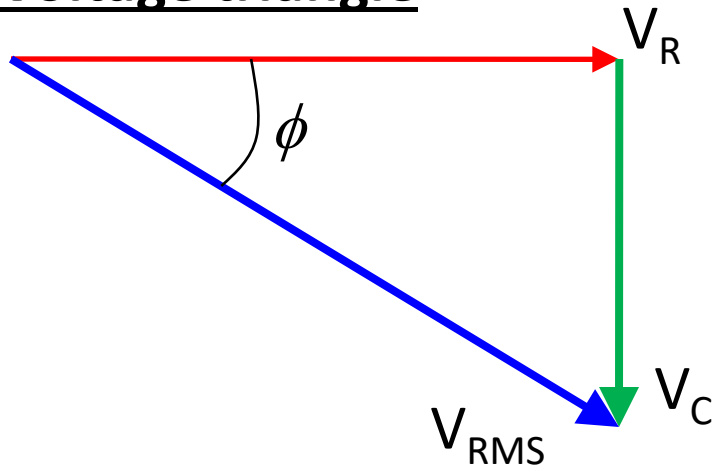


$$V_R = I_{RMS} \times R$$

$$V_L = I_{RMS} \times X_C$$

$$V_{RMS} = I_{RMS} \times Z$$

- Redraw the same triangle in terms of the resistance, reactance, and impedance only
- (by eliminating the common quantity I_{RMS})

Impedance triangle

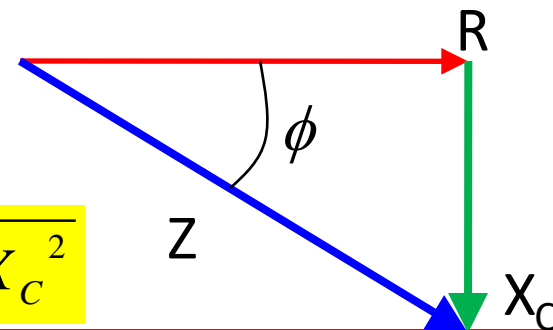


$$Z = \sqrt{R^2 + X_C^2}$$

Hypotenuse of the impedance triangle is the impedance Z

The angle between Z and R is the power factor angle ϕ

AC circuit operation with R + C


More on phase angle

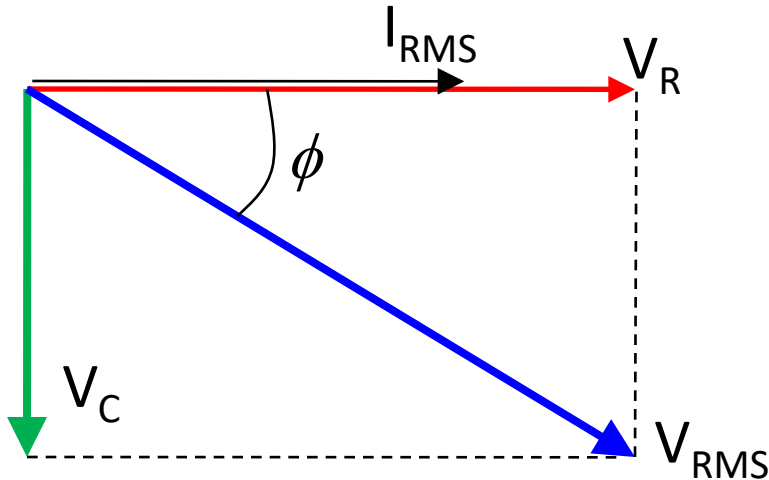

- The supply voltage signal lags the current by a phase angle ϕ which is less than 90°
- This is expected because it is a combination of R and C circuit


- In an R + C circuit, the angle between voltage and current should lie somewhere between 0° (pure resistance) and 90° (pure capacitance)
- When $X_C = R$, the phase angle $\phi = 45^\circ$
- When $R > X_C$, the phase angle $\phi < 45^\circ$
- When $X_C > R$, then the phase angle $\phi > 45^\circ$

AC circuit operation with R + C

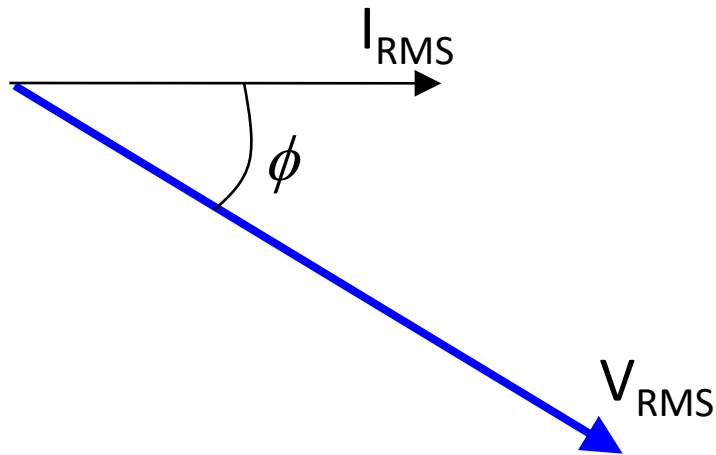


Instantaneous values

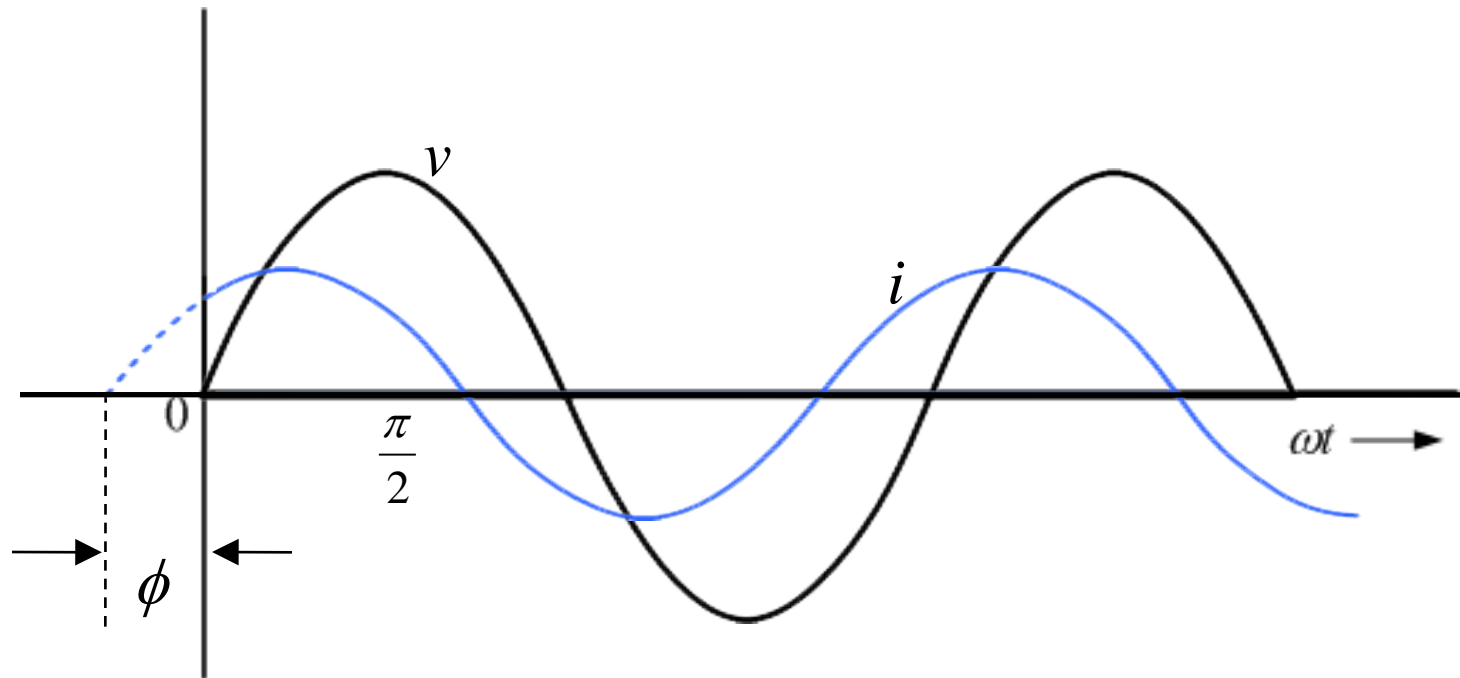- The current is drawn leading ahead of the voltage by an angle ϕ that is less than 90°



AC circuit operation with R + C

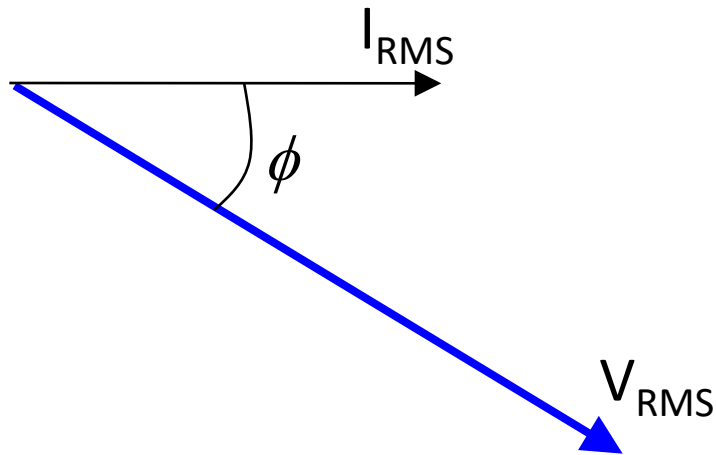


- If the voltage signal is given by the expression

$$v = V_m \sin \omega t$$


- then the current signal that leads the voltage by an angle ϕ , will be given by the expression

$$i = I_m \sin(\omega t + \phi)$$

$$I_m = \frac{V_m}{Z}$$

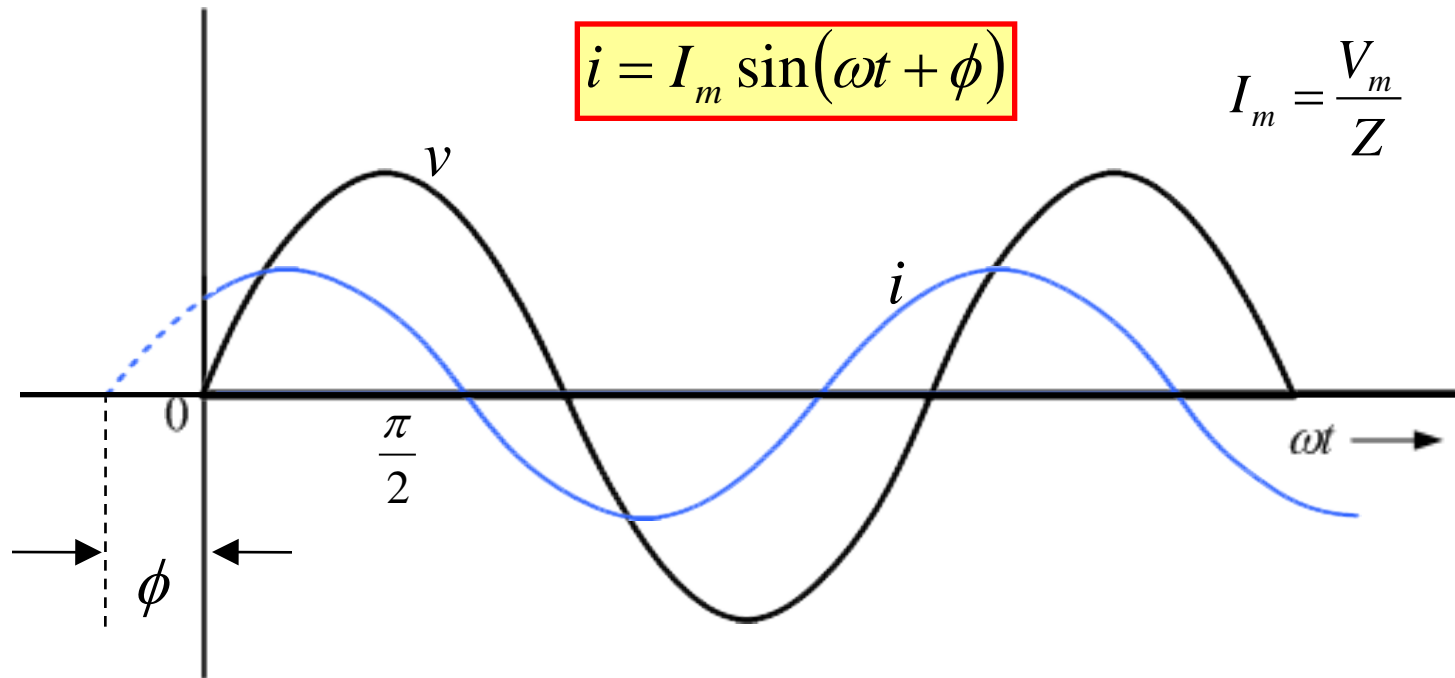

AC circuit operation with R + C

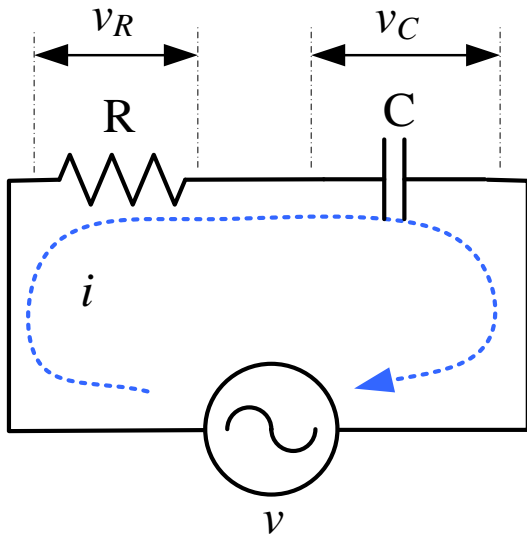

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t + \phi)$$

Instantaneous power

$$p = v \times i$$

$$p = V_m \sin \omega t \times I_m \sin(\omega t + \phi)$$


$$p = V_m I_m \sin \omega t \sin(\omega t + \phi)$$

$$p = \frac{V_m I_m}{2} [\cos(\omega t - \omega t - \phi) - \cos(\omega t + \omega t + \phi)]$$


$$p = \frac{V_m I_m}{2} [\cos(-\phi) - \cos(2\omega t + \phi)]$$

$$p = \frac{V_m I_m}{2} [\cos(\phi) - \cos(2\omega t + \phi)]$$

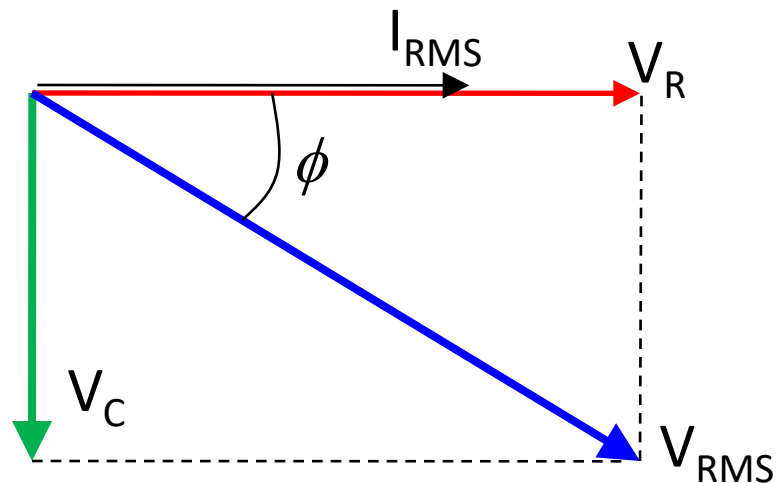As earlier, the instantaneous power varies at **twice the frequency** of the input voltage signal.



AC circuit operation with R + C

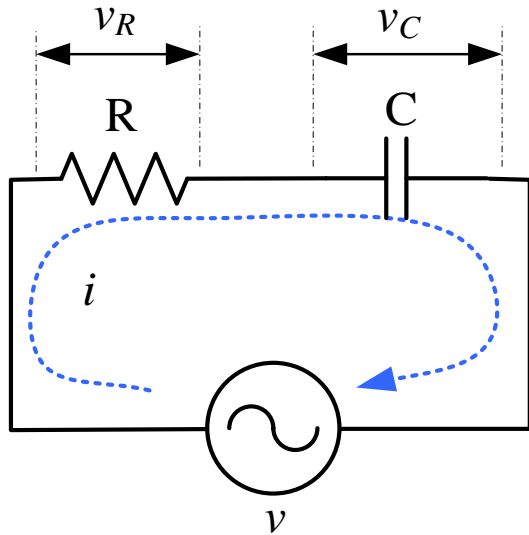

Average power

$$p = \frac{V_m I_m}{2} [\cos(\phi) - \cos(2\omega t + \phi)]$$

$$P = \frac{1}{T} \int_0^T p dt$$


$$P = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} [\cos(\phi) - \cos(2\omega t + \phi)] dt$$

.....

$$P = V_{RMS} I_{RMS} \cos \phi$$

Same expression as for R+L circuit

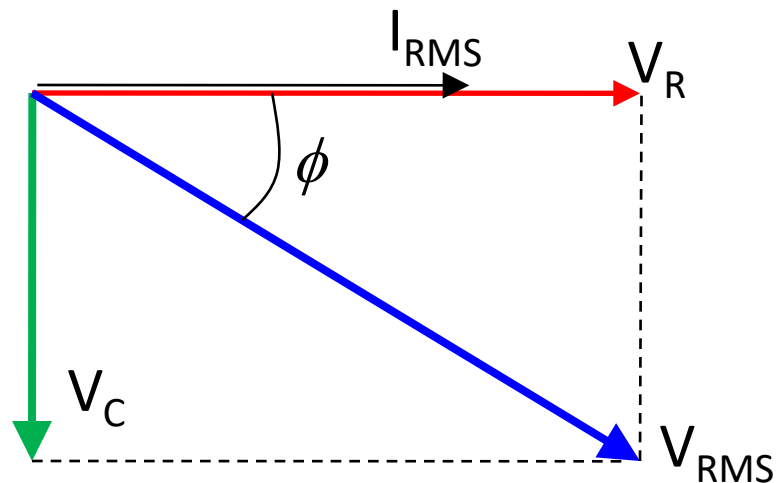Active power is the product of RMS values of voltage and current, and the power factor



Summary




Type of circuit	Effective impedance $Z (\Omega)$	Current I_{RMS}	Phase angle (ϕ) between V & I	Power factor ($\cos\phi$)	Active power
R	R	$\frac{V_{RMS}}{R}$	0^0	1	$V_{RMS} I_{RMS}$
L	$X_L = \omega L$	$\frac{V_{RMS}}{X_L}$	I_{RMS} lags V_{RMS} by 90^0	0	0
R-L	$Z = \sqrt{R^2 + X_L^2}$	$\frac{V_{RMS}}{Z}$	I_{RMS} lags V_{RMS} by ϕ $\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$	(Lag) $\cos\phi$	$V_{RMS} I_{RMS} \cos\phi$
C	$X_C = \frac{1}{\omega C}$	$\frac{V_{RMS}}{X_C}$	I_{RMS} leads V_{RMS} by 90^0	0	0
R-C	$Z = \sqrt{R^2 + X_C^2}$	$\frac{V_{RMS}}{Z}$	I_{RMS} leads V_{RMS} by ϕ $\phi = \tan^{-1}\left(\frac{1}{\omega CR}\right)$	(Lead) $\cos\phi$	$V_{RMS} I_{RMS} \cos\phi$

Power in AC circuits


Voltage triangle of RL circuit

$$V_R = V_{RMS} \cos \phi \quad V_L = V_{RMS} \sin \phi$$

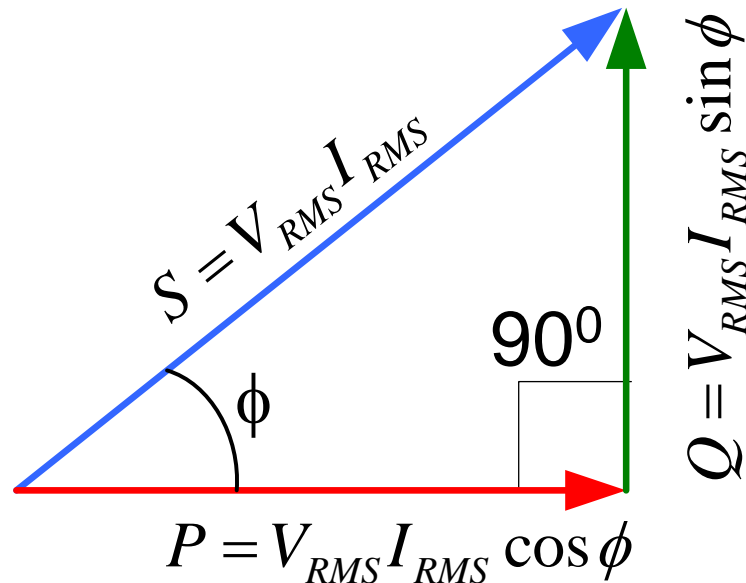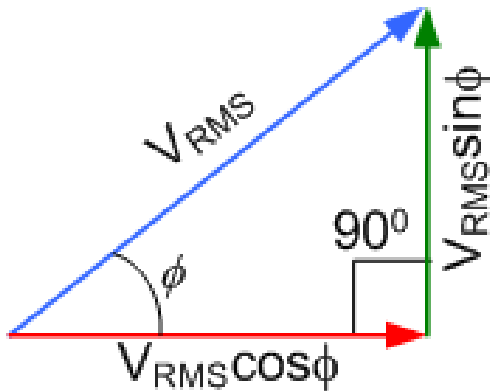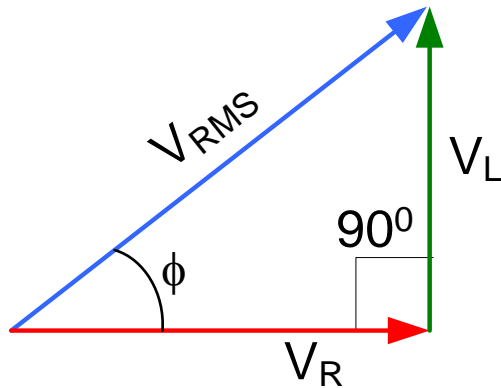Multiplying all three arms of the voltage triangle by the current I_{RMS} , we have the so called **power triangle**:




Power in AC circuits

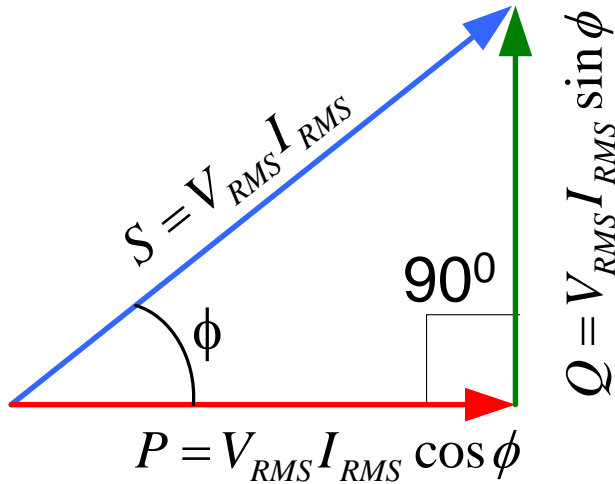

- The quantity $P = V_{RMS} I_{RMS} \cos \phi$ is called the **active power**
- It is expressed in the unit of Watt (W)
- The quantity $Q = V_{RMS} I_{RMS} \sin \phi$ is called the **reactive power**
- It is expressed in the unit of Volt-Ampere-Reactive (VA_R)
- The quantity $S = V_{RMS} I_{RMS}$ is called the **apparent power (Total power)**
- It is expressed in the unit of Volt-Ampere (VA)

Power in AC circuits

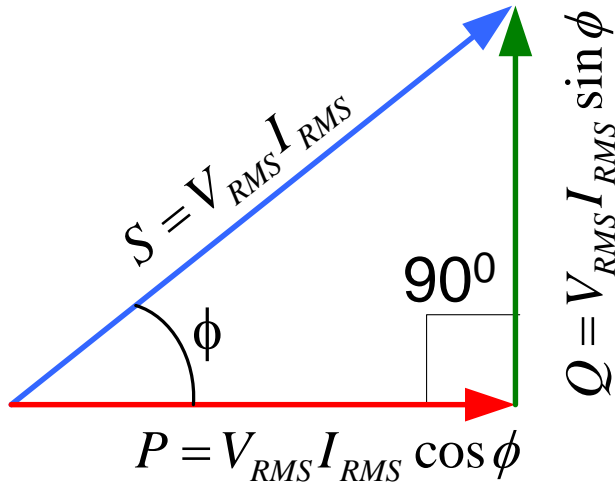

- The relation among the three powers are:


$$S = \sqrt{P^2 + Q^2}$$

- These mathematical relations are equally valid for R-C circuits also

- The practical definition of **power factor** can now be derived from the power triangle as:

$$\cos \phi = \frac{P}{S} = \frac{\text{Active power}}{\text{Apparent power}}$$

Power in AC circuits

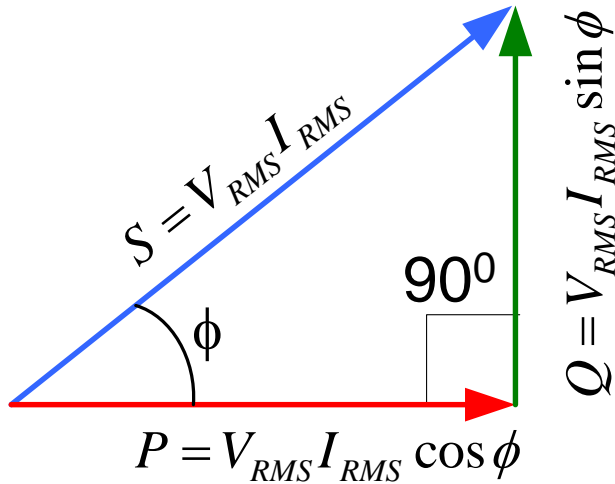

$$\cos \phi = \frac{P}{S} = \frac{\text{Active power}}{\text{Apparent power}}$$

Thus, power factor can be defined as the fraction of total apparent power that is being used as active power

- The power factor is lagging when the current lags the applied voltage (inductive circuit, i.e. R-L circuit)
- The power factor is leading when the current leads the applied voltage (capacitive circuit, i.e. R-C circuit)
- For purely inductive or purely capacitive circuit, the power factor is $\cos 90^\circ = 0$
- For purely resistive circuit, the power factor is $\cos 0^\circ = 1$