

Chapter 5

3-Phase systems

Day 26

Configurations

ILOs – Day 26

- Understand the utility of 3-phase system in electric power supply
- Visualize how 3-phase signal is generated
- Draw delta connected 3-phase system and derive it voltage and current relations
- Draw star connected 3-phase systems and derive it voltage and current relations


3-phase system

- Household electricity supply is single phase
 - One live conductor
 - One neutral conductor
 - (One optional earth conductor)
- But, larger power supply systems are 3-phase
 - Generating stations
 - Power transmission & distribution
 - Industries
 - Large buildings, large motors

3 phase system

- Why three-phase?
 - Large power transfer
 - Current very high at a given voltage
 - If single phase, then conductor too thick
 - Difficult to handle
- Divide power in three lines (3-phase)
 - One third power shared by each phase
 - Conductor size less
 - Easy to handle
 - Increased reliability


Three phase power transfer scheme

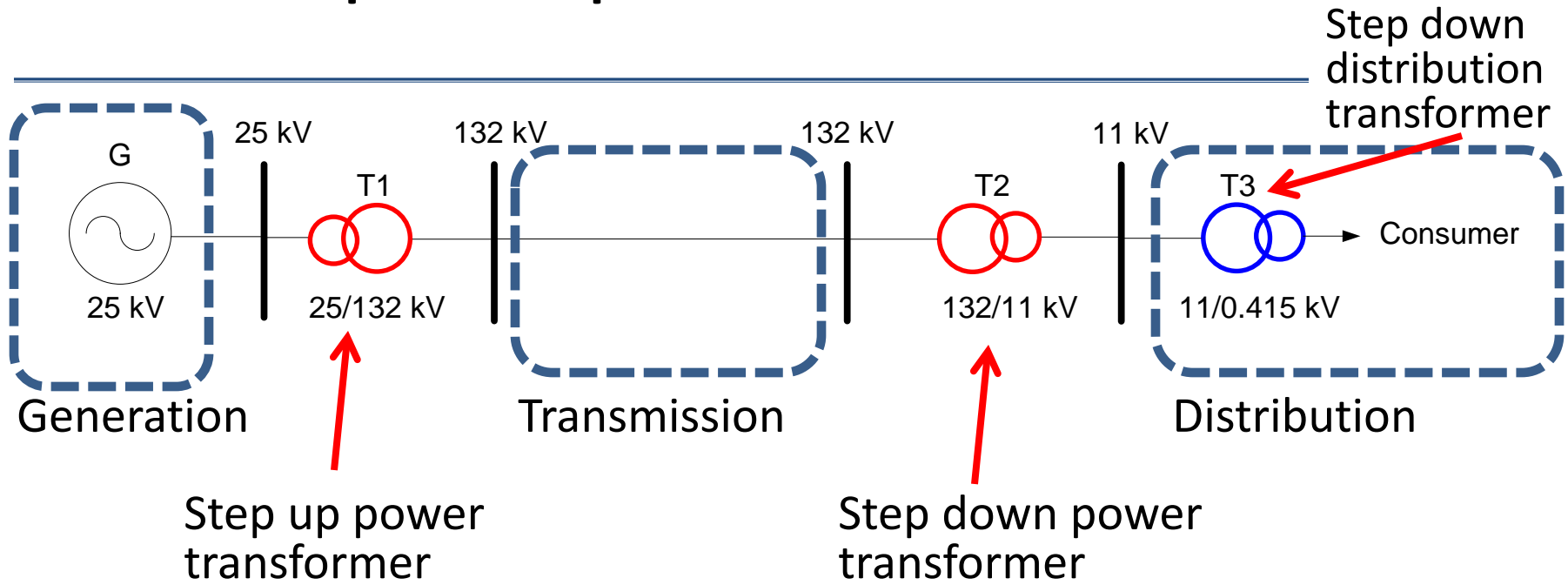

- Transmission at high voltage to reduce power loss during transmission
 - Higher voltage means lower current for a given power
 - Thus, I^2R losses are less in transmission line
 - Also, voltage drop (IZ) is less in transmission line


Generation of 3-phase signal

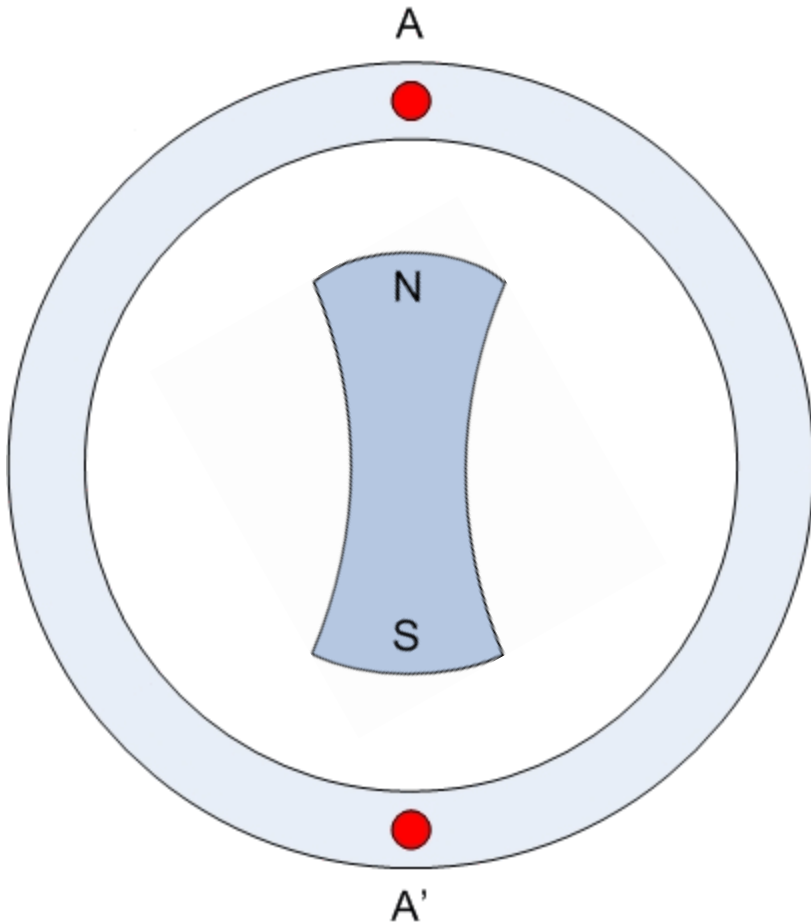- One coil in the stator A-A'
- Pair of permanent magnets in rotor
- Rotor rotated by external mechanical force (prime mover)




Generation of 3-phase signal

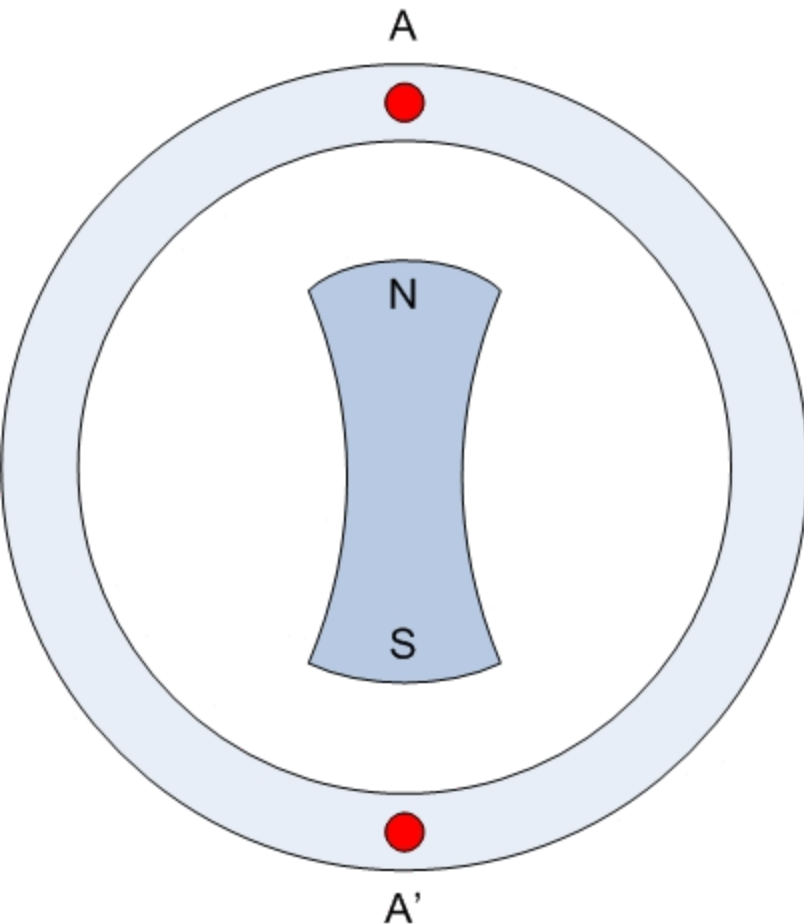- EMF is induced in stator coil ($d\phi/dt$)




Generation of 3-phase signal

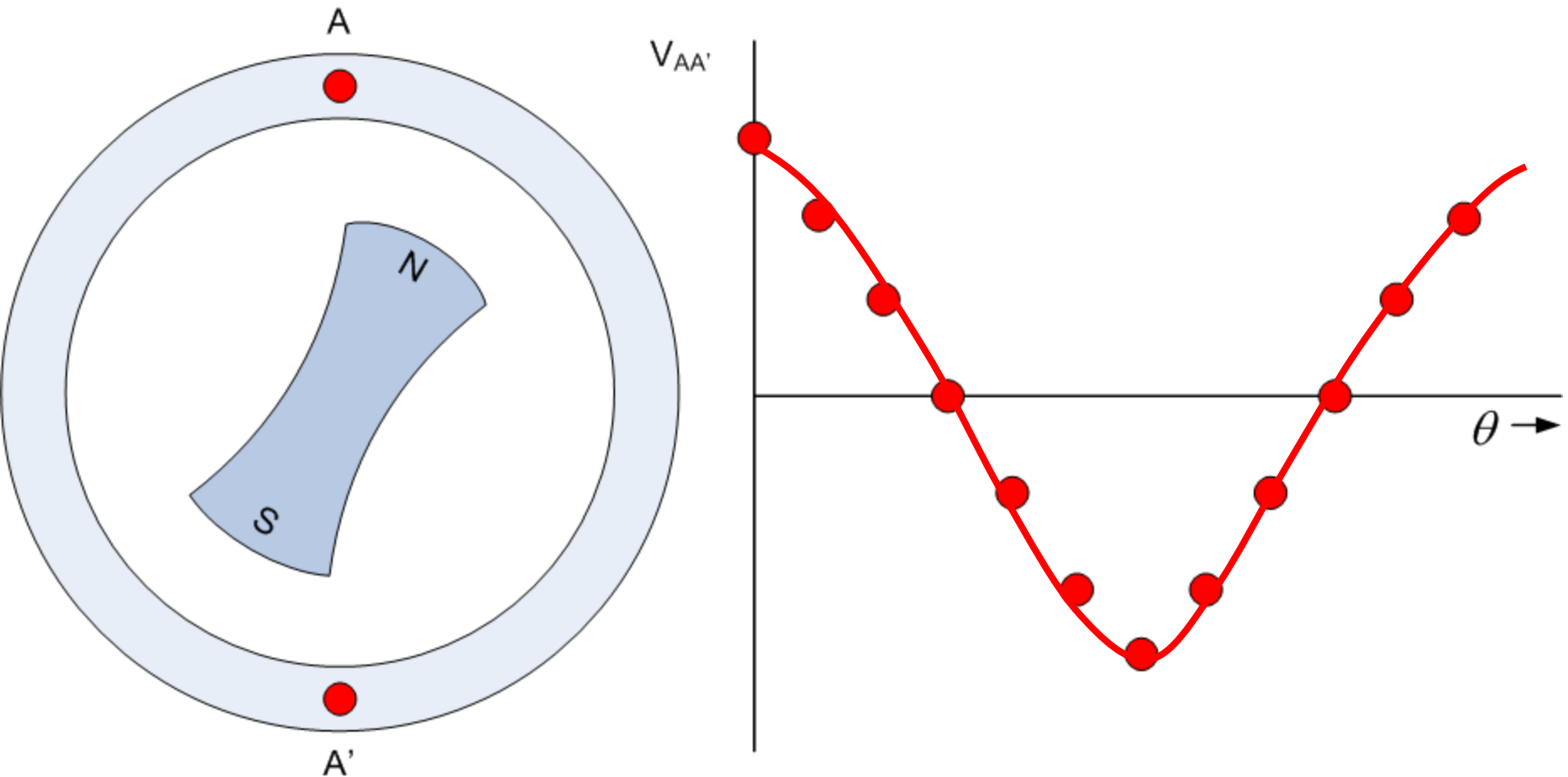- EMF is sinusoidal $e_A = E_m \sin \theta = E_m \sin \omega t$





Generation of 3-phase signal

- Put a second coil B-B' after 120°

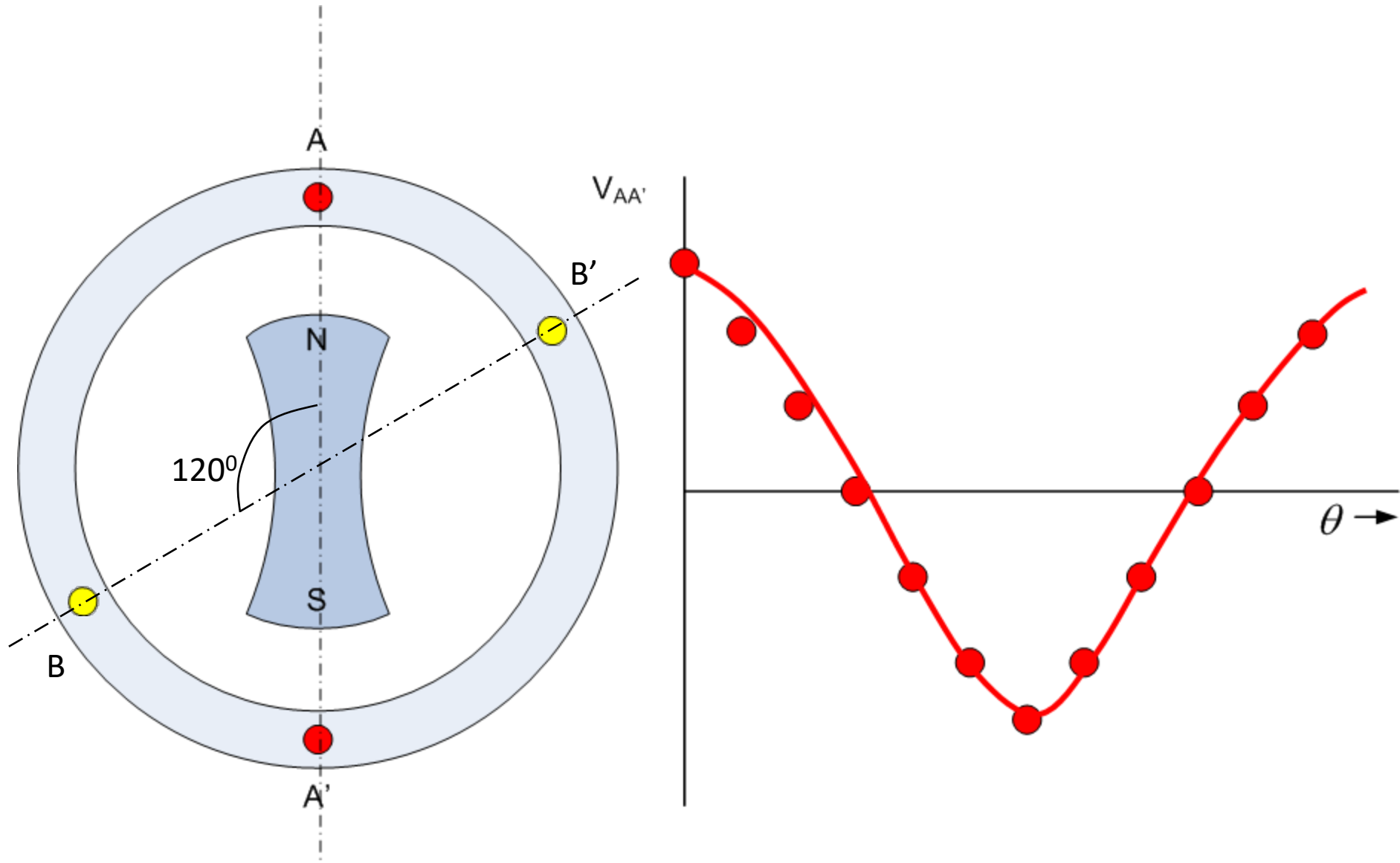



Generation of 3-phase signal

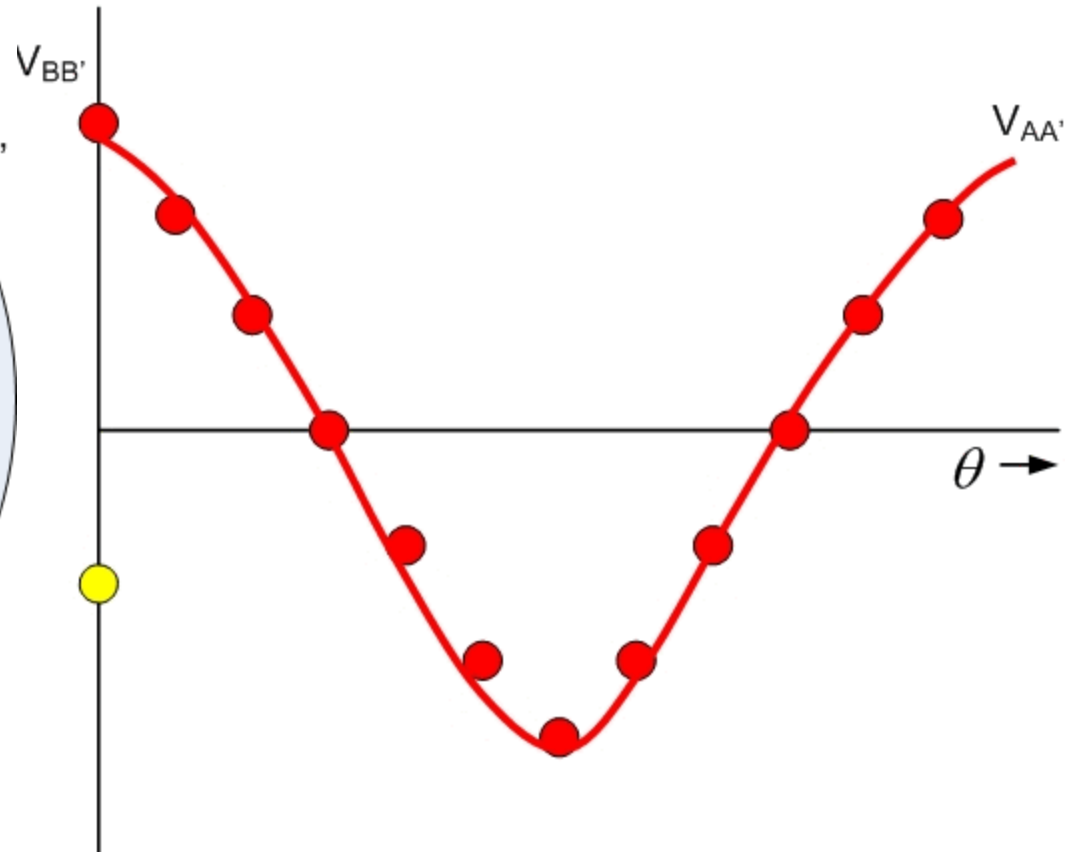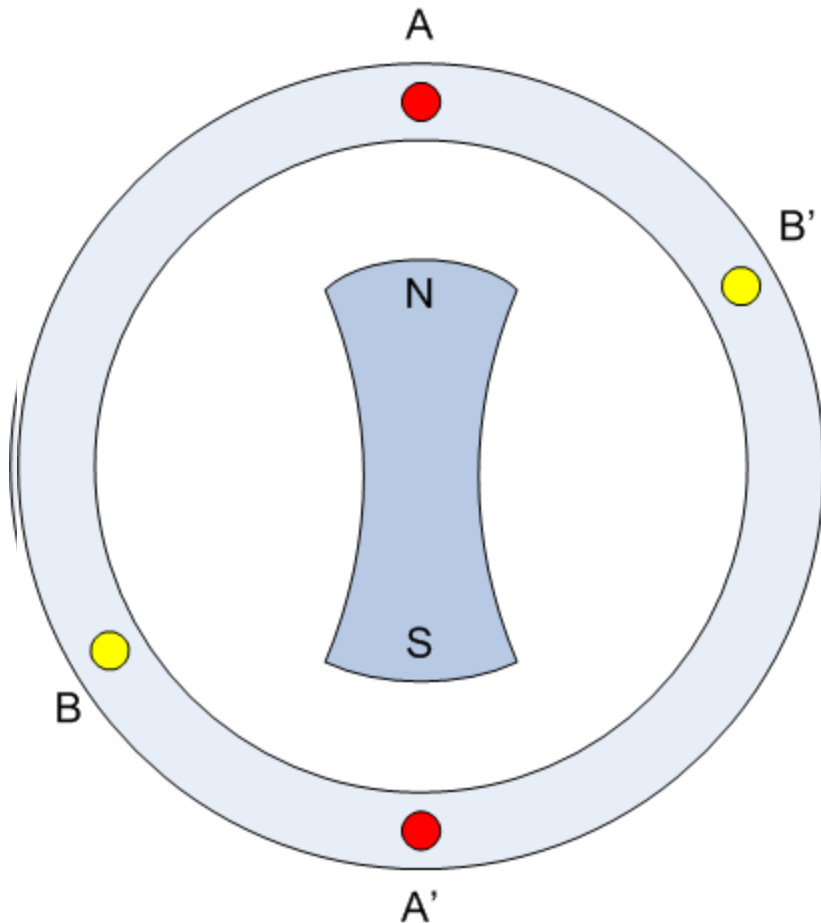- B-B' will also have induced EMF $V_{BB'}$
- But $V_{BB'}$ will come after 120° of $V_{AA'}$ (phase difference of 120° from $V_{AA'}$)




Generation of 3-phase signal

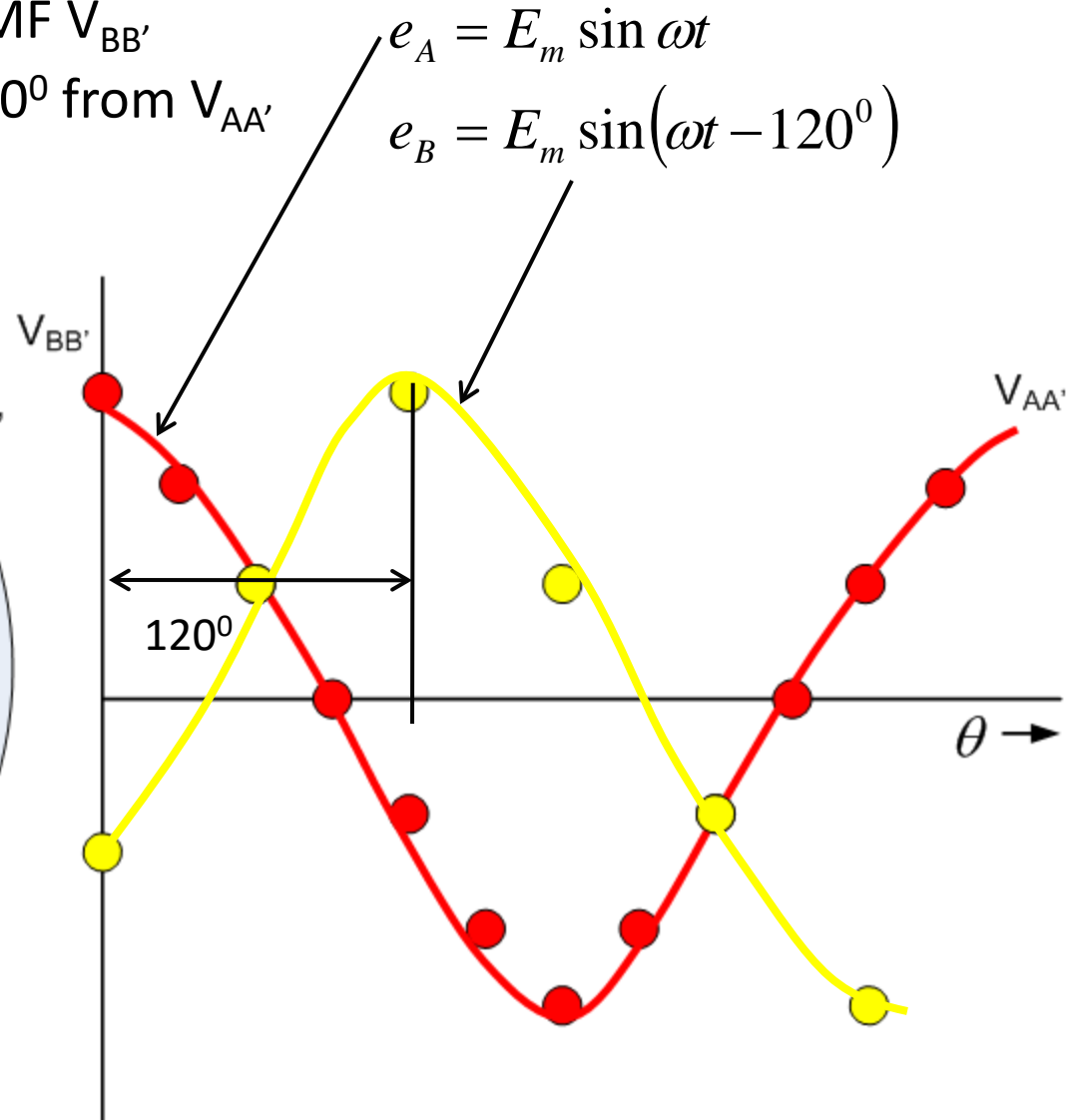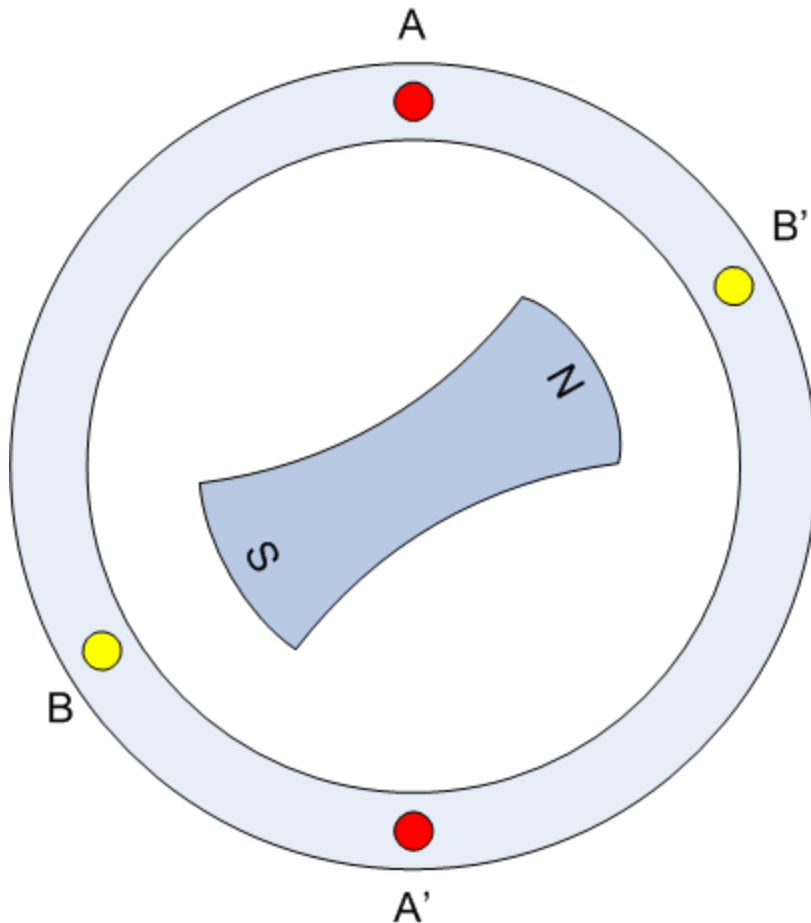- B-B' will also have induced EMF $V_{BB'}$
- $V_{BB'}$ at phase difference of 120° from $V_{AA'}$



Generation of 3-phase signal


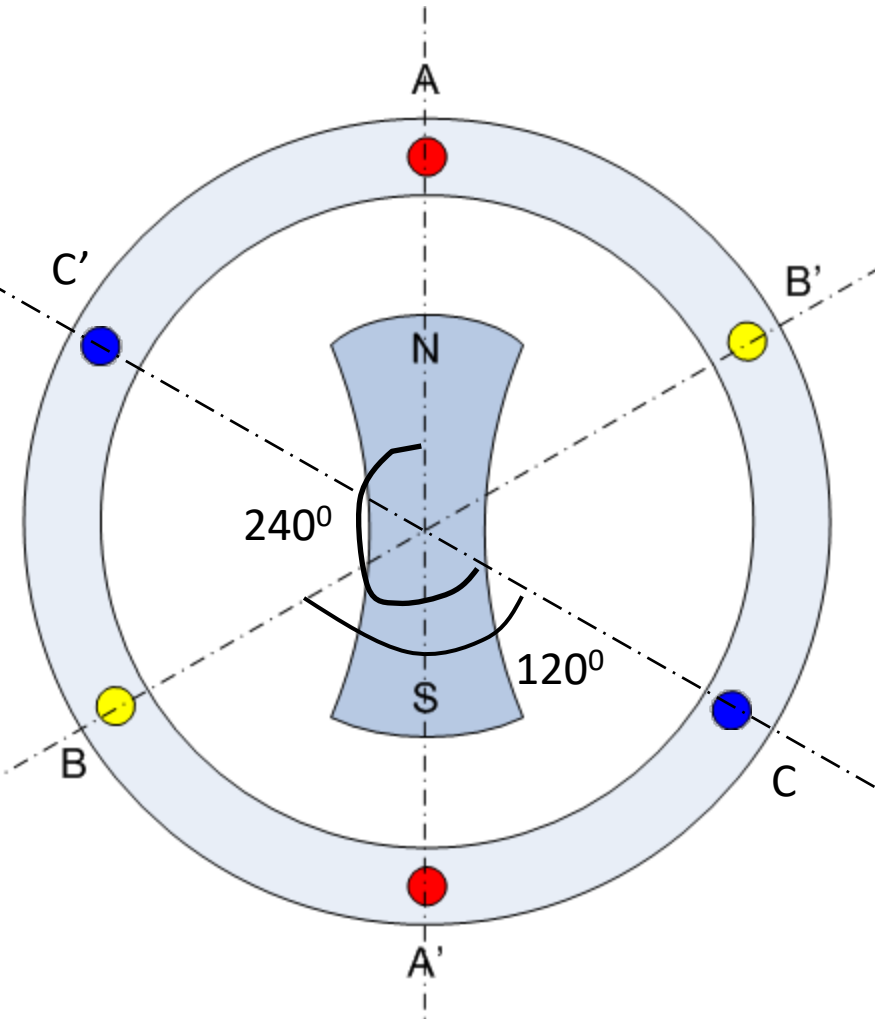
- Now have a 3rd Coil C-C' that will be 120° after B-B'



- C-C' will also have similar induced EMF
- With phase difference of 120° from $V_{BB'}$
- i.e. phase difference of 240° from $V_{AA'}$


Generation of 3-phase signal
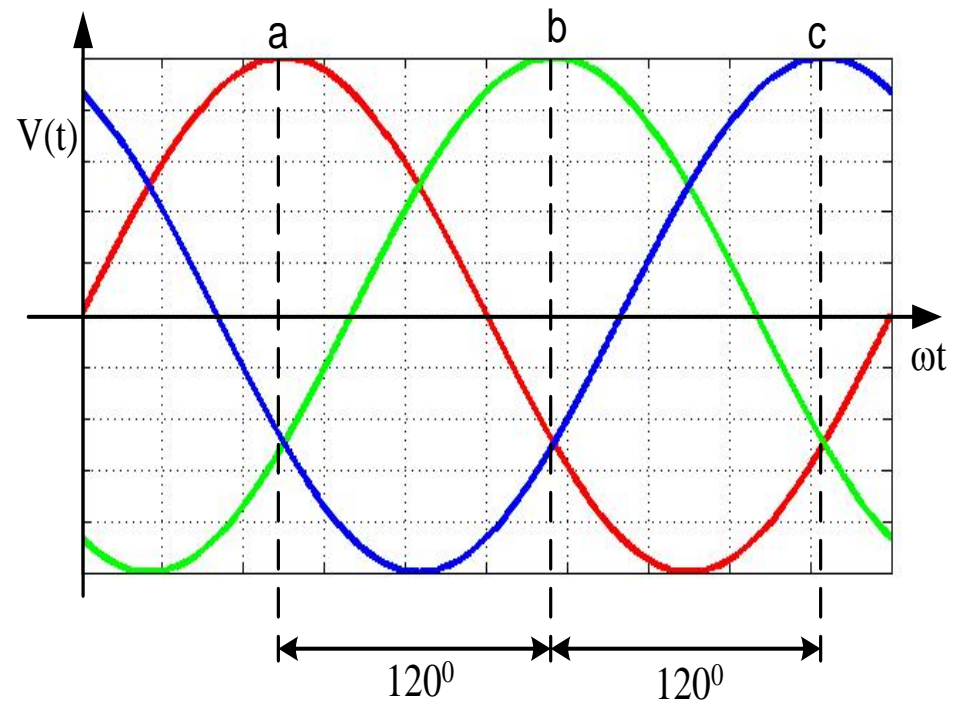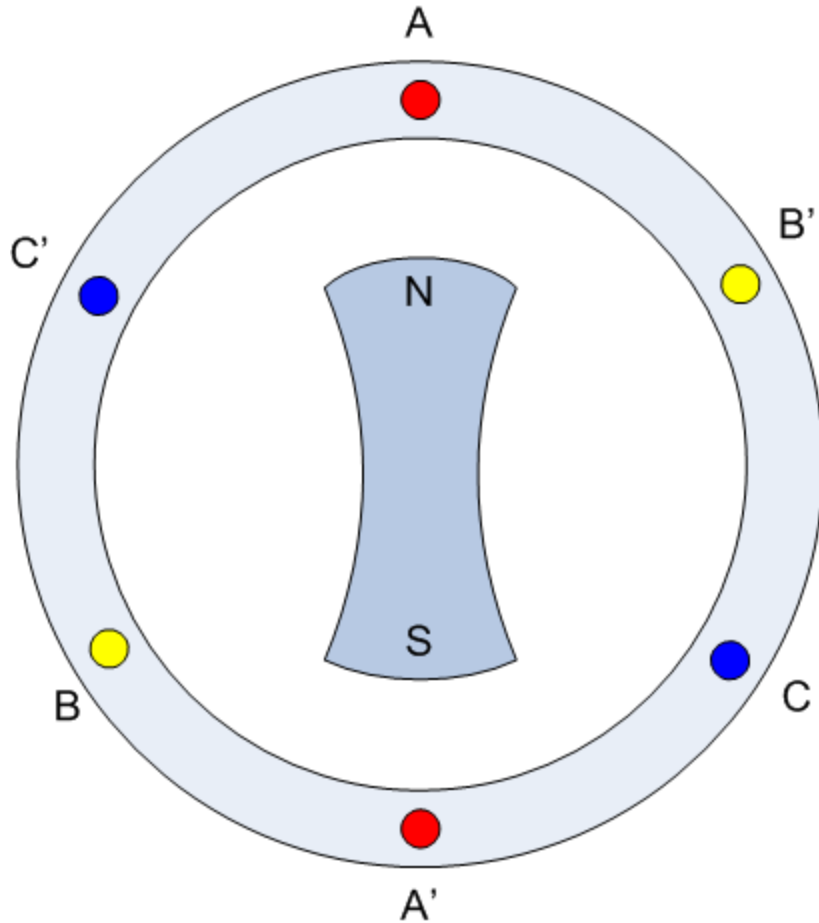
$$e_A = E_m \sin \omega t \quad e_B = E_m \sin(\omega t - 120^\circ) \quad e_C = E_m \sin(\omega t - 240^\circ)$$



Three phase signal

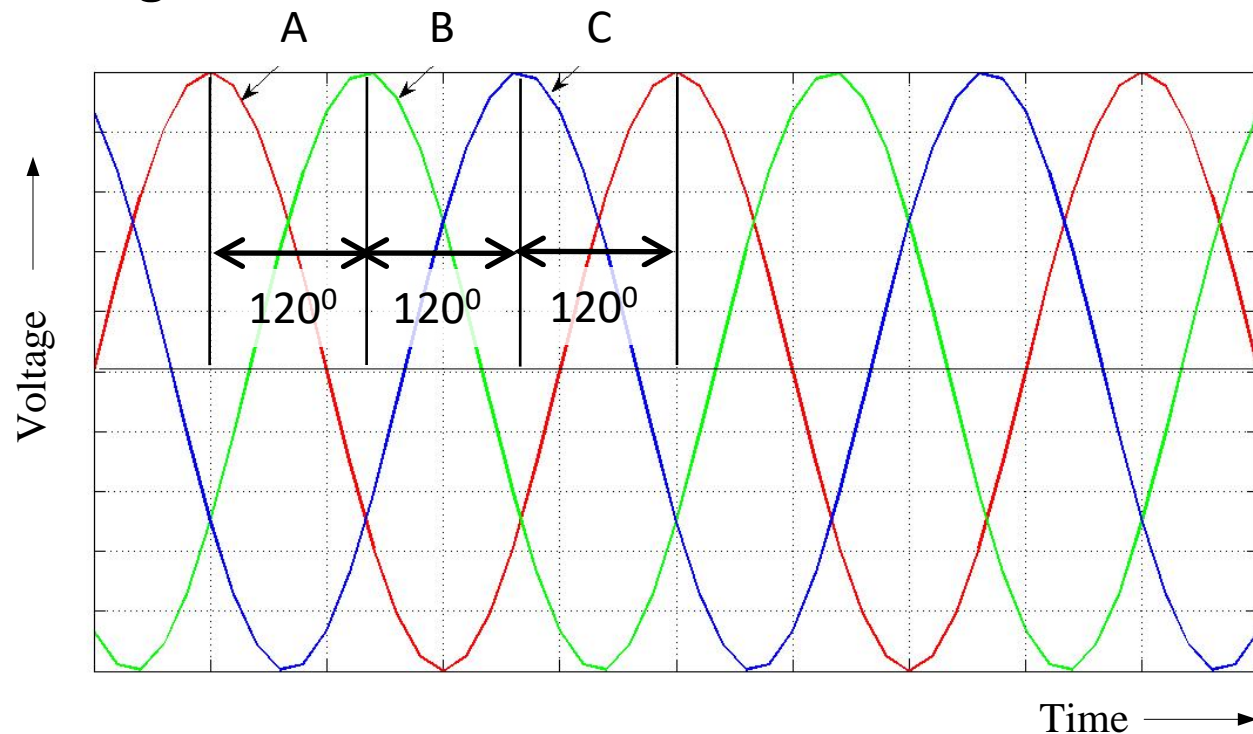
- 3-phase balanced signal (voltage or current)
- Same magnitude in all three phases
- Same frequency of all three signals
- Phase angle 120° between them



Phase sequence


- Set of 3-phase signals

Phase sequence
a-b-c

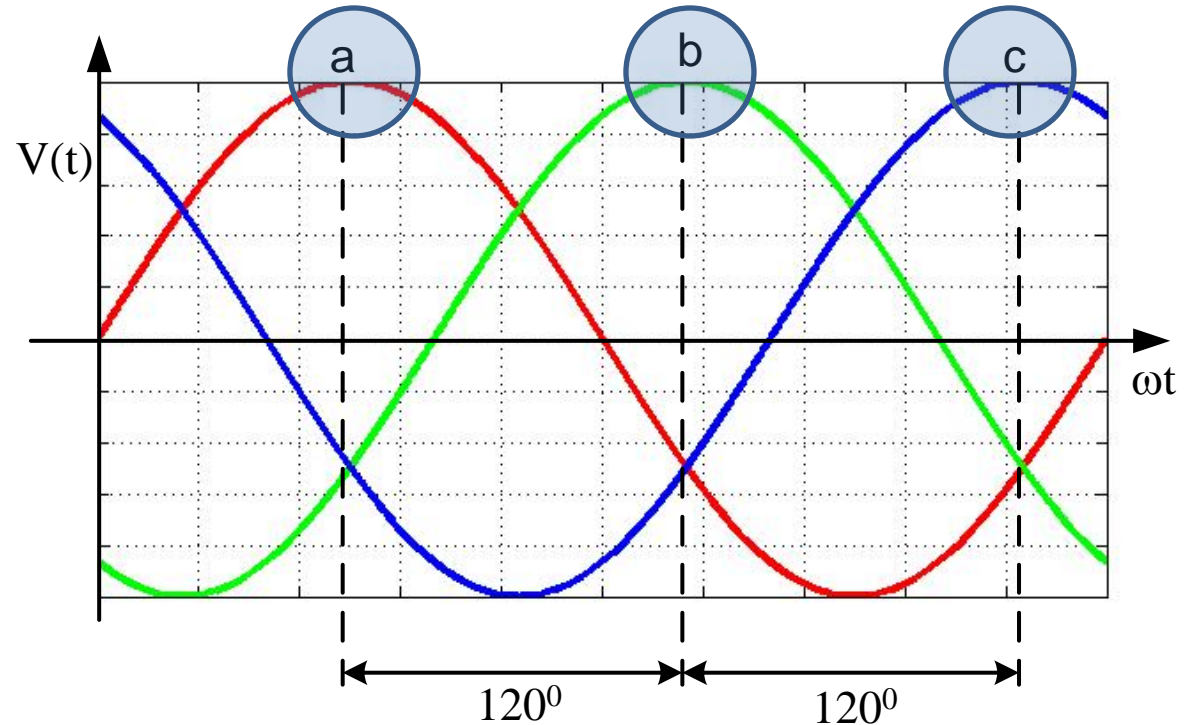

- Phase sequence of **a-b-c** indicates that phase 'a' attains its peak first in time followed by 'b' and then 'c'
- a leads b, b leads c

Phase sequence – phasor diagram

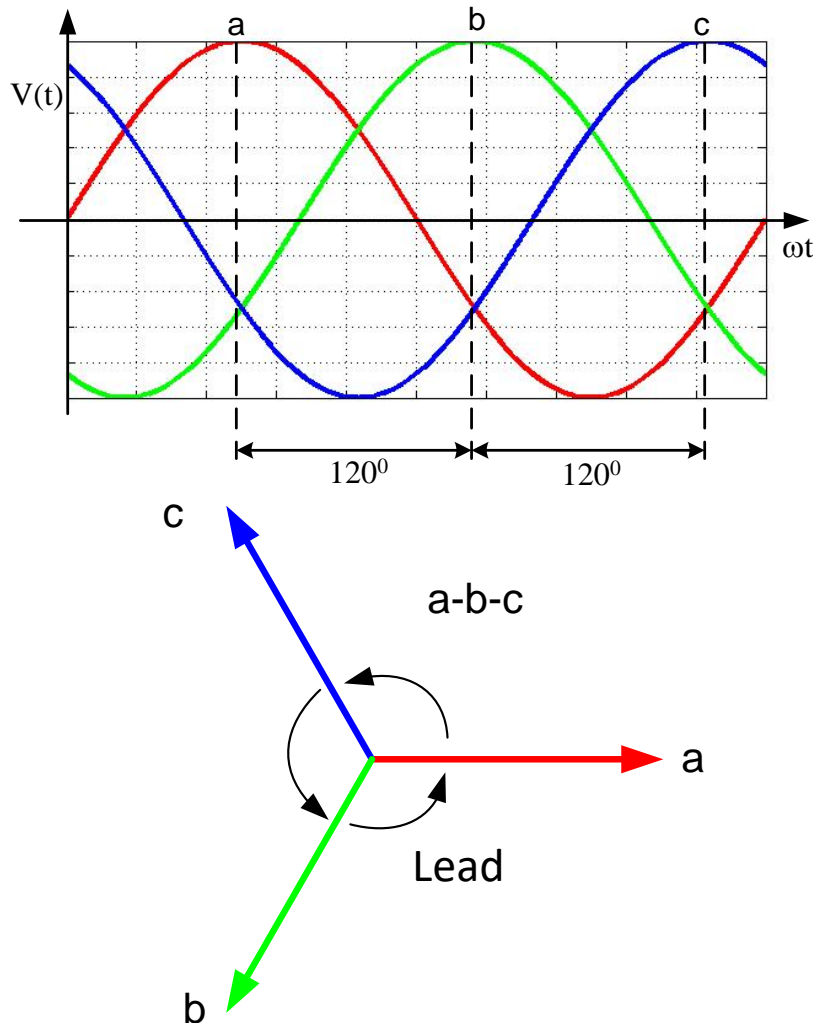

- In phasor diagram, the a-b-c phase sequence is denoted by phasors a-b-c coming in CLOCKWISE sequence as per convention
- 'a' phasor leads 'b' by 120° and 'c' by 240° in the anticlockwise direction
- RMS values

$$E_A = V \angle 0^\circ$$

$$E_B = V \angle -120^\circ$$


$$E_C = V \angle -240^\circ$$

Phase sequence – phasor diagram

- This sequence is continued in a cyclic fashion a-b-c-a-b-c-a-.....
- Thus a phase sequence of “a-b-c” is basically same as:
- ‘b-c-a’ or ‘c-a-b’


a	b	c	a	b
---	---	---	---	---

c – a – b – c

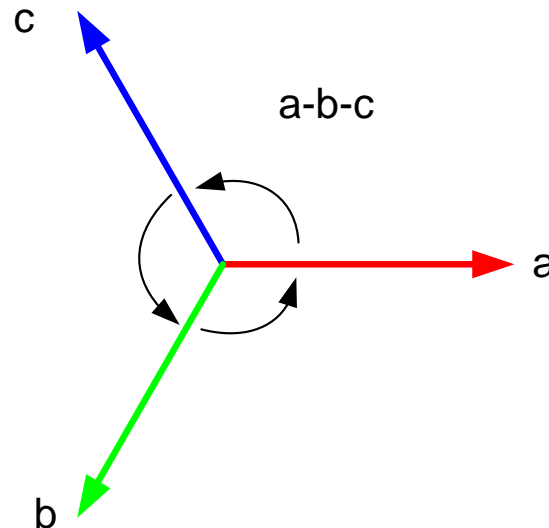

Three phase generator

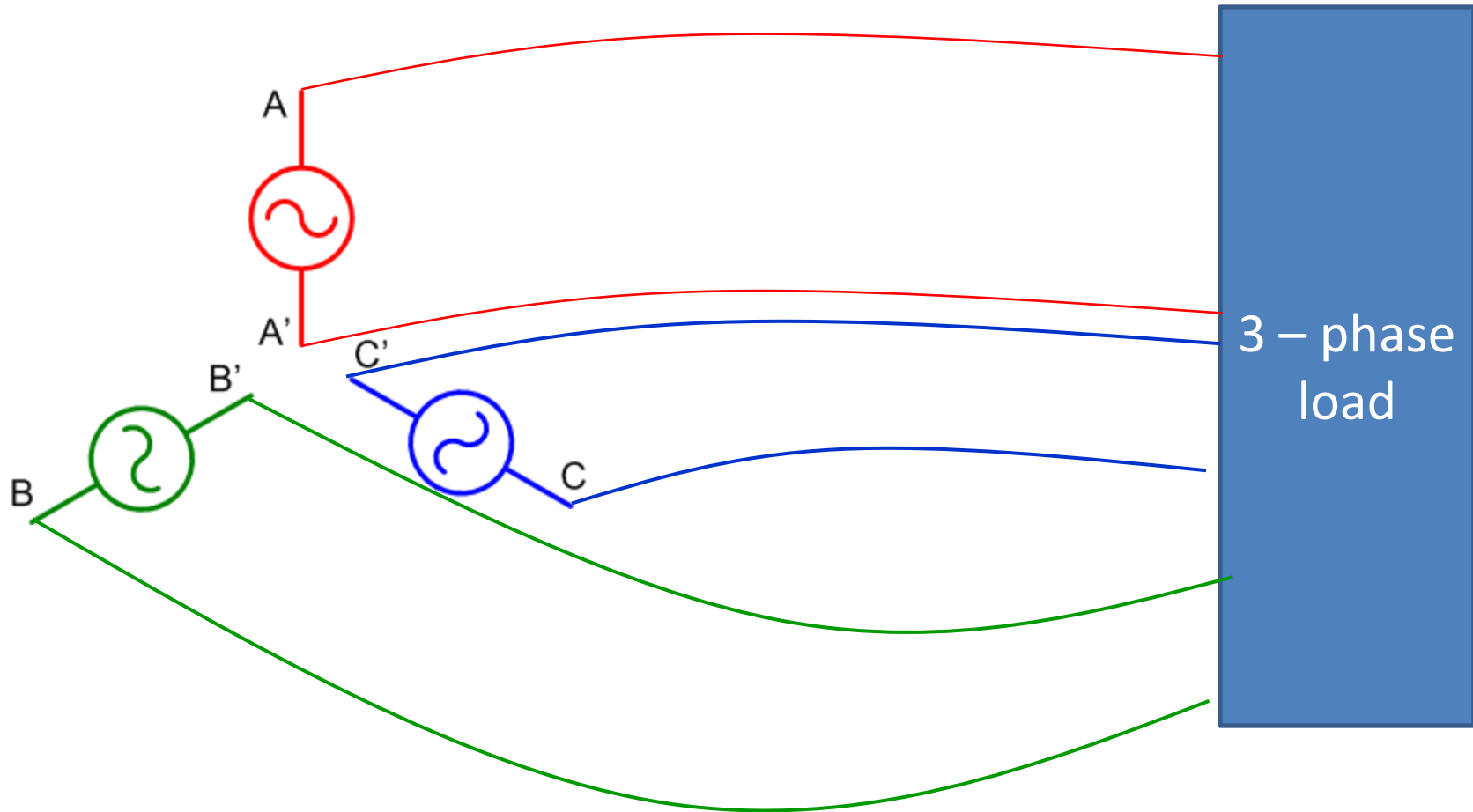- Three voltage sources (AA' coil, BB' coil, and CC' coil)
 - Equal magnitude
 - 120° phase difference





Quiz: How many conductors do we need to supply 3-phase power to load?

Can we reduce the number of conductors?

- From 6 conductors can we reduce to 3 or 4 conductors?
- Interconnect the three generator coils
 - Delta (3 conductors)
 - Star
 - with neutral (4 conductors)
 - without neutral (3 conductors)


Delta connection

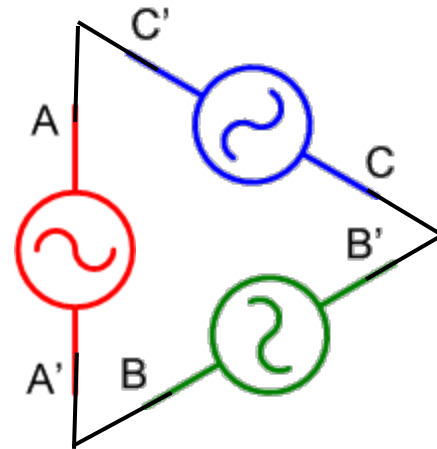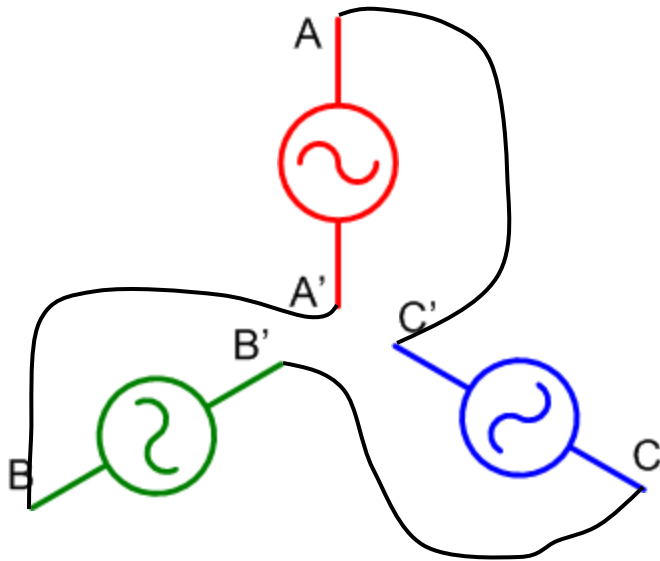- The 3 generator coils are interconnected
- Finish of one coil connected to start of the next coil, and so on



Delta connection

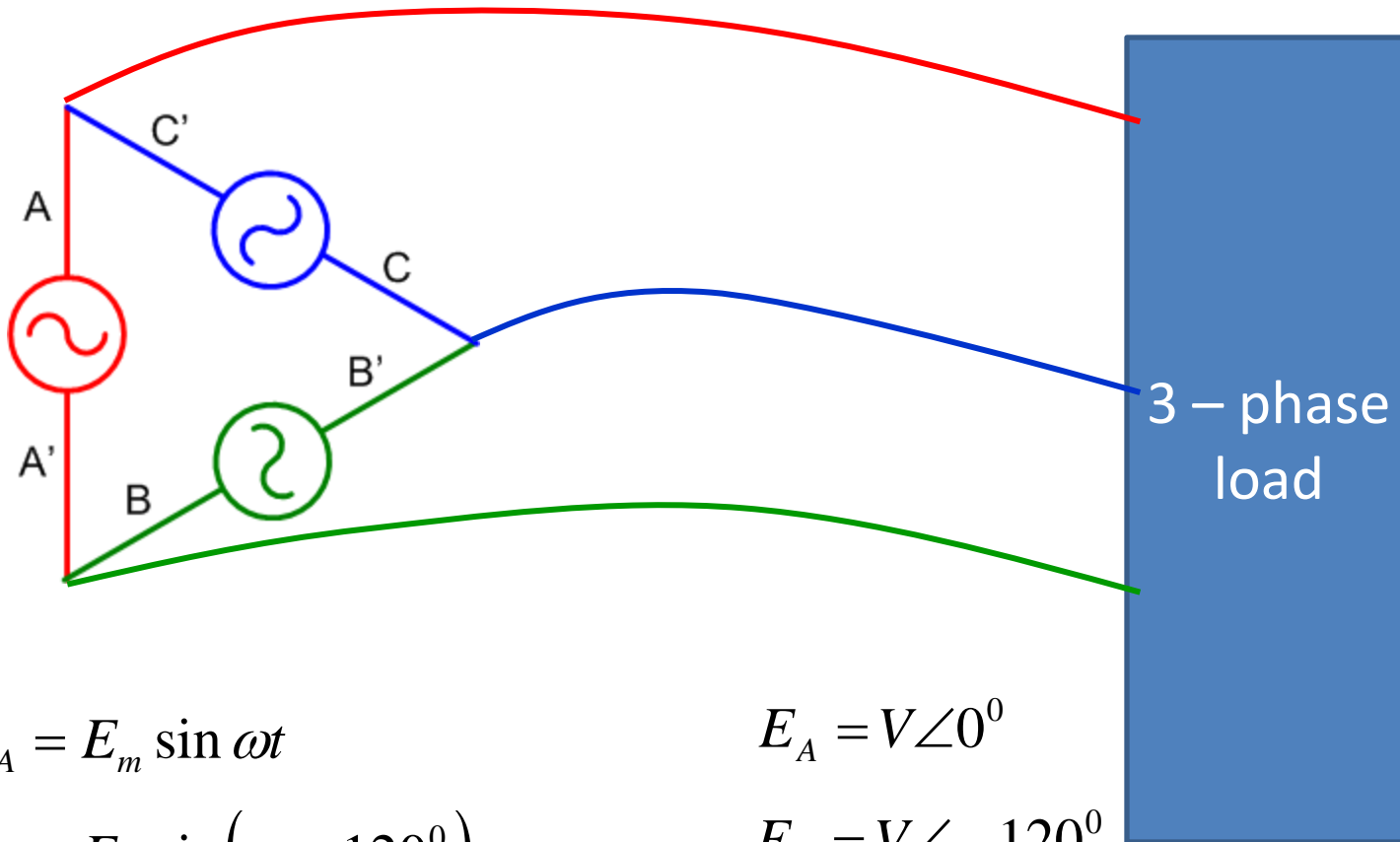- The output lines are connected to the junction points of delta



$$e_A = E_m \sin \omega t$$

$$e_B = E_m \sin(\omega t - 120^\circ)$$

$$e_C = E_m \sin(\omega t - 240^\circ)$$


$$E_A = V \angle 0^\circ$$

$$E_B = V \angle -120^\circ$$

$$E_C = V \angle -240^\circ$$


Delta connection

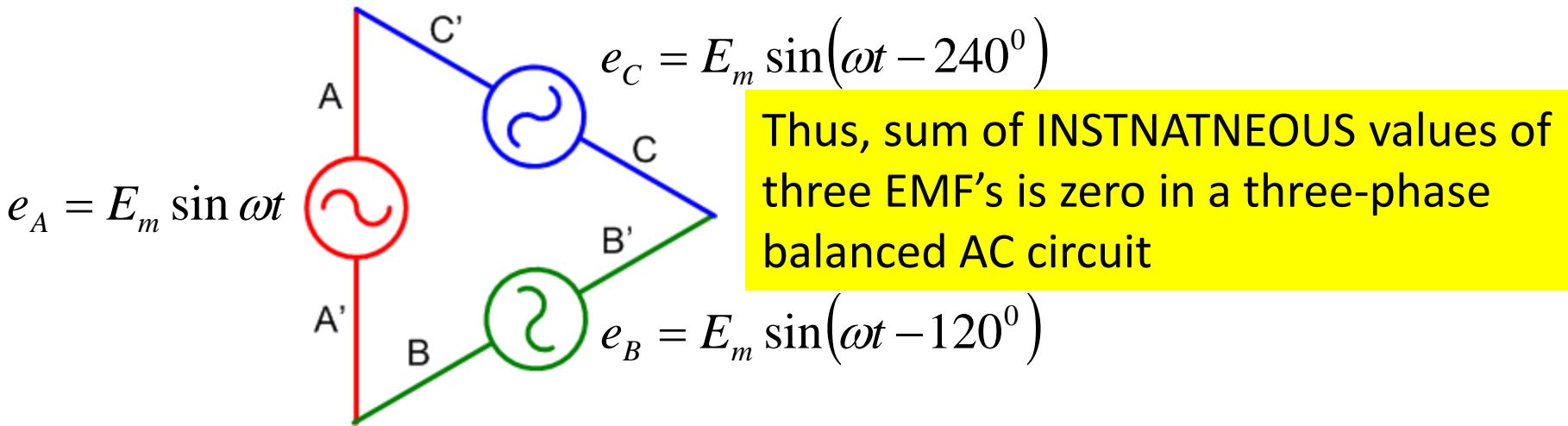- Summation of instantaneous voltages in a closed delta loop



$$\begin{aligned} & e_A + e_B + e_C \\ &= E_m \sin \omega t + E_m \sin(\omega t - 120^\circ) + E_m \sin(\omega t - 240^\circ) \\ &= E_m [\sin \omega t + \sin \omega t \cos 120^\circ - \cos \omega t \sin 120^\circ + \sin \omega t \cos 240^\circ - \cos \omega t \sin 240^\circ] \\ &= E_m [\sin \omega t - 0.5 \sin \omega t - 0.866 \cos \omega t - 0.5 \sin \omega t + 0.866 \cos \omega t] \\ &= E_m [\sin \omega t - \sin \omega t] \\ &= 0 \end{aligned}$$

Voltage & current in Delta connection

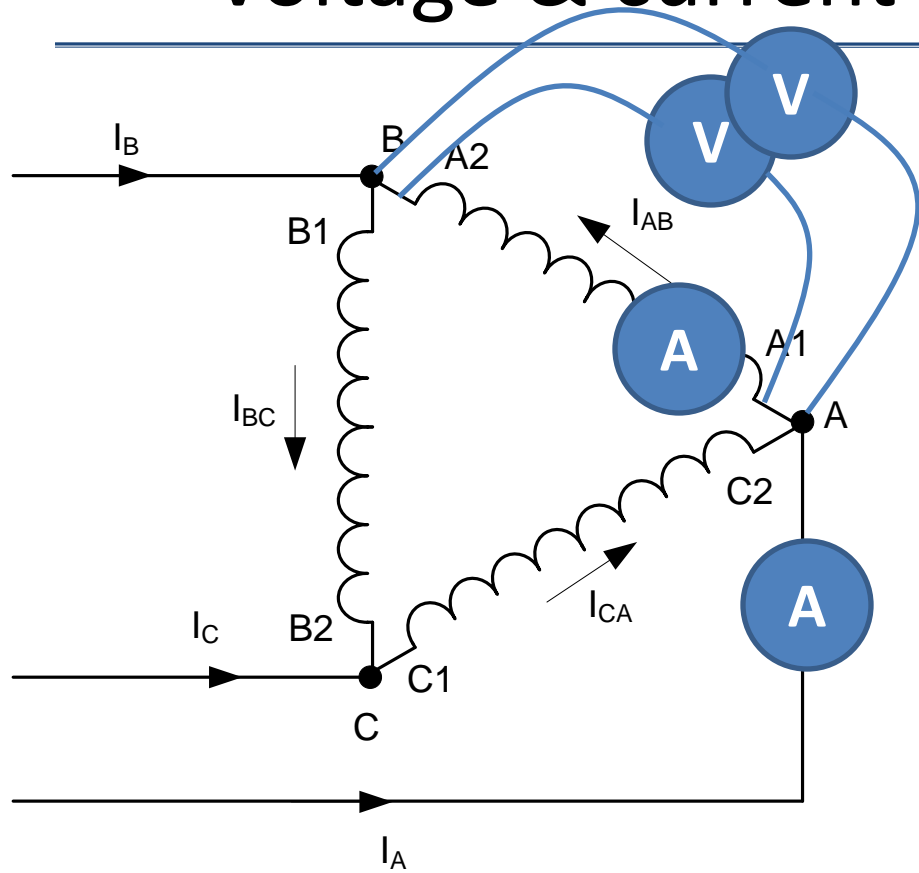

KCL at node A

$$\overline{I_A} = \overline{I_{AB}} - \overline{I_{CA}} = \overline{I_{AB}} + (-\overline{I_{CA}})$$

$$I_L \neq I_{ph}$$

Phase voltage

$$|V_{A1A2}| = |V_{B1B2}| = |V_{C1C2}| = V_{ph}$$

Line voltage

$$|V_{AB}| = |V_{BC}| = |V_{CA}| = V_L$$

$$V_L = V_{ph}$$



Phase current

$$|I_{AB}| = |I_{BC}| = |I_{CA}| = I_{ph}$$

Line current

$$|I_A| = |I_B| = |I_C| = I_L$$

Delta connection

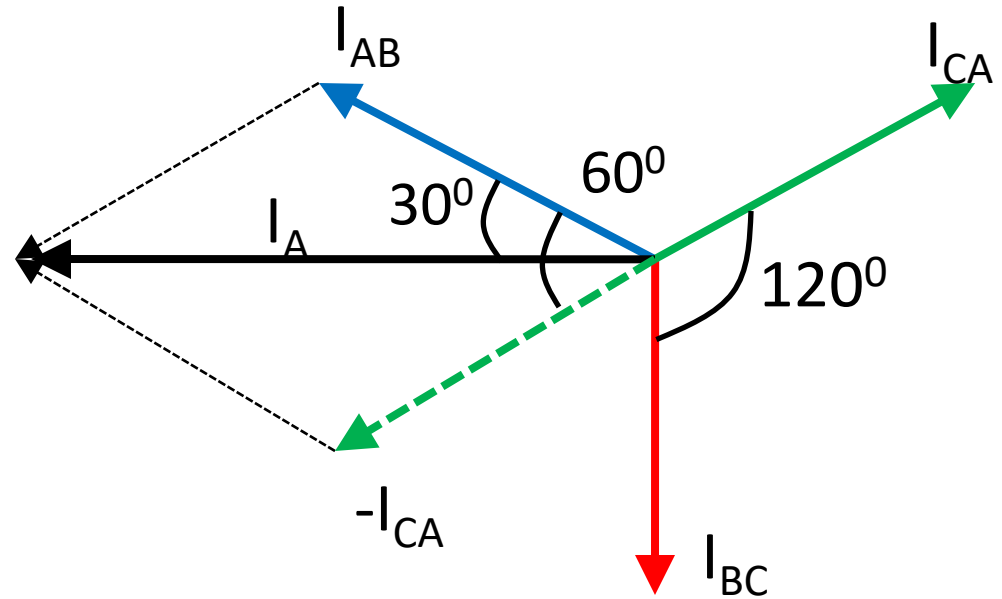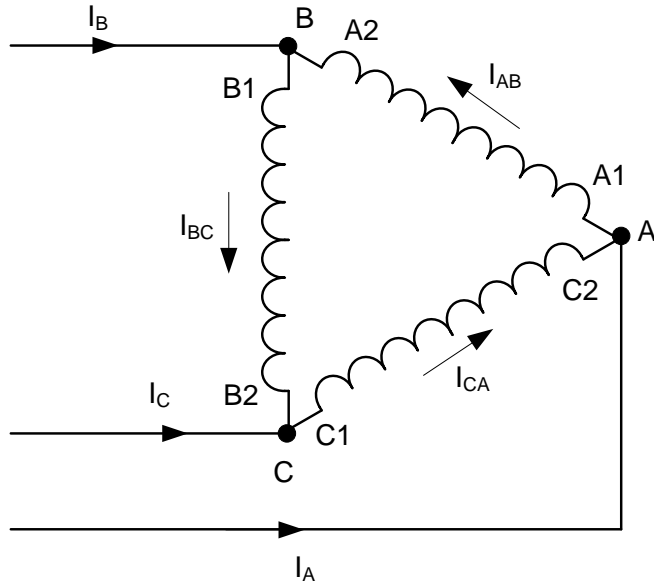

$$I_L = \overline{I_A} = \overline{I_{AB}} - \overline{I_{CA}} = \overline{I_{AB}} + (-\overline{I_{CA}})$$

$$|I_A| = \sqrt{|I_{CA}|^2 + |I_{AB}|^2 + 2 \times |I_{CA}| \times |I_{AB}| \cos 60^\circ}$$

$$= \sqrt{I_{ph}^2 + I_{ph}^2 + 2 \times I_{ph} \times I_{ph} \times \frac{1}{2}} = \sqrt{I_{ph}^2 + I_{ph}^2 + I_{ph}^2} = \sqrt{3I_{ph}^2} = \sqrt{3}I_{ph}$$


$$I_L = \sqrt{3}I_{ph}$$

In a balanced delta connected system, line voltages are equal to phase voltages, but line currents are $\sqrt{3}$ times the phase currents.

The angle between line and phase current is 30°

Delta connection

- Balanced Delta connected system

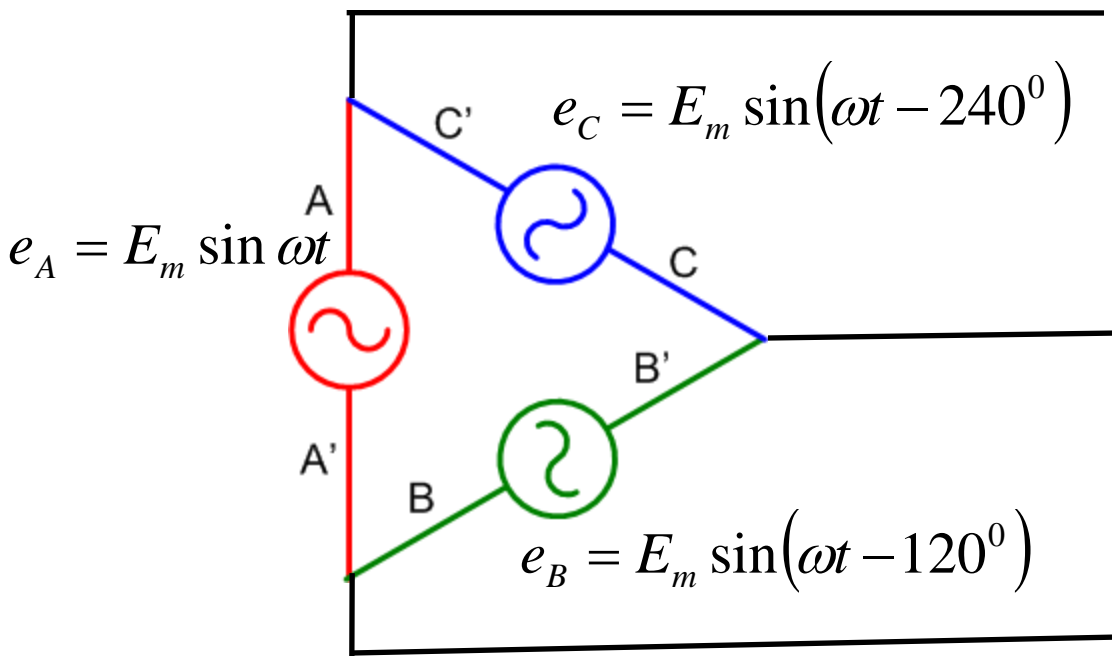


$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

Star connection – 4 Wire system

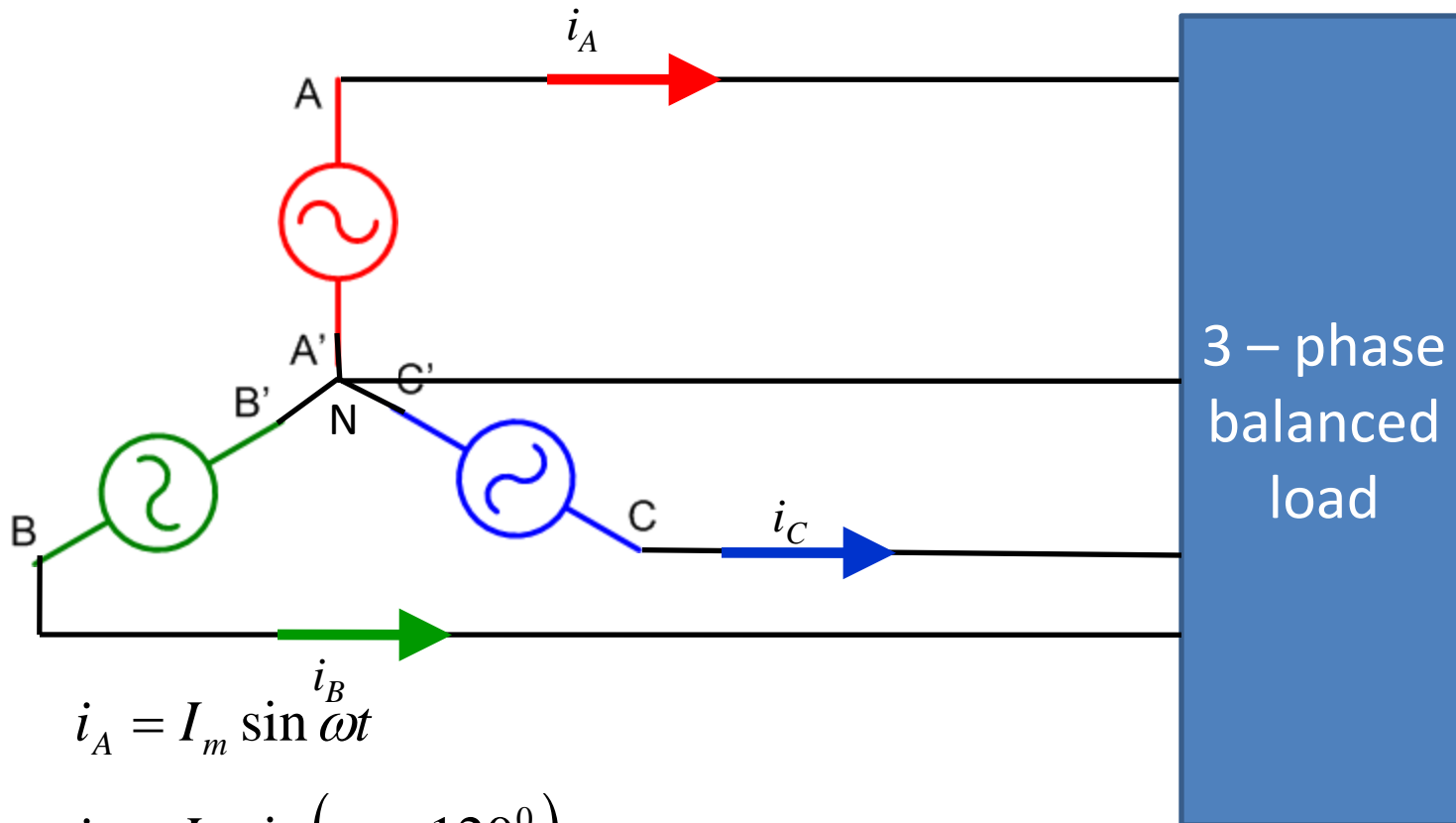- One terminal each of the 3 coils are joined together to the neutral point N
- 3 LIVE lines and 1 NEUTRAL line goes out




$$i_A = I_m \sin \omega t$$

$$i_B = I_m \sin(\omega t - 120^\circ)$$

$$i_C = I_m \sin(\omega t - 240^\circ)$$


Star connection

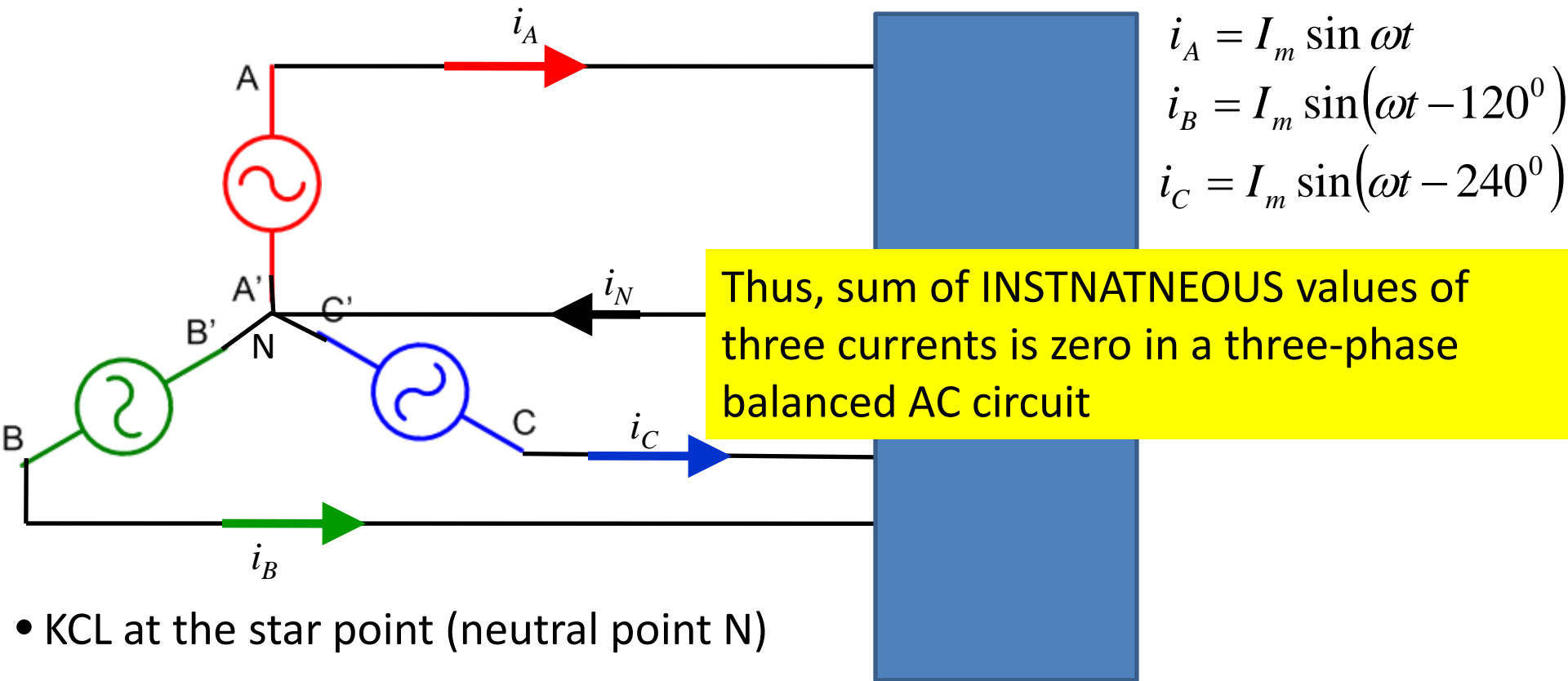

- KCL at the star point (neutral point N)

$$\begin{aligned}
 i_N &= i_A + i_B + i_C \\
 &= I_m \sin \omega t + I_m \sin(\omega t - 120^\circ) + I_m \sin(\omega t - 240^\circ) \\
 &= I_m [\sin \omega t + \sin \omega t \cos 120^\circ - \cos \omega t \sin 120^\circ + \sin \omega t \cos 240^\circ - \cos \omega t \sin 240^\circ] \\
 &= I_m [\sin \omega t - 0.5 \sin \omega t - 0.866 \cos \omega t - 0.5 \sin \omega t + 0.866 \cos \omega t] \\
 &= I_m [\sin \omega t - \sin \omega t] = 0
 \end{aligned}$$

Star connection 3-wire system

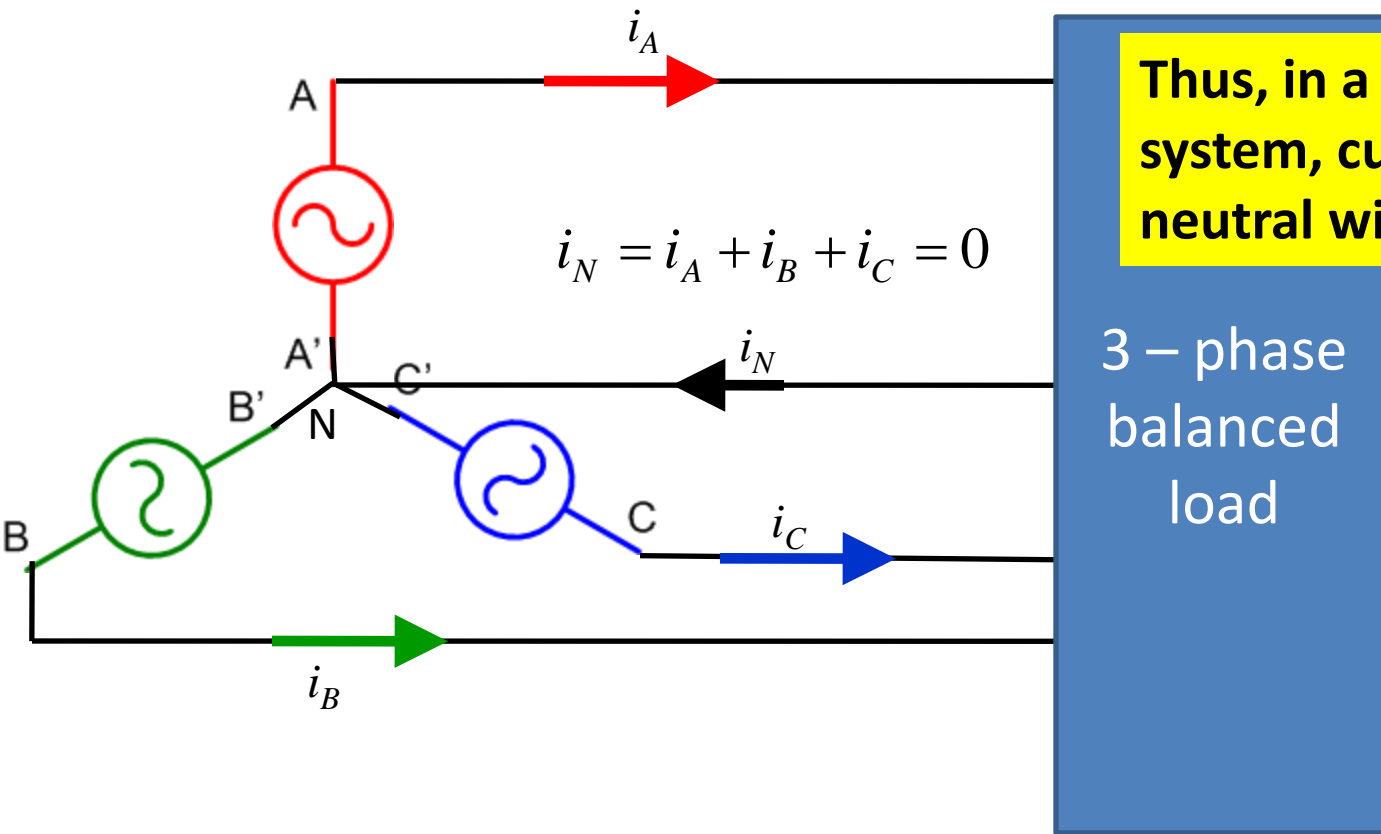


Thus, in a balanced 3-phase system, current through the neutral wire is ZERO

3 – phase
balanced
load

Thus, since the neutral wire does not carry any current in a balanced 3-phase system, often the neutral wire is not used

Thus, we have the 3-phase 3-wire system

Voltage & current in STAR connection

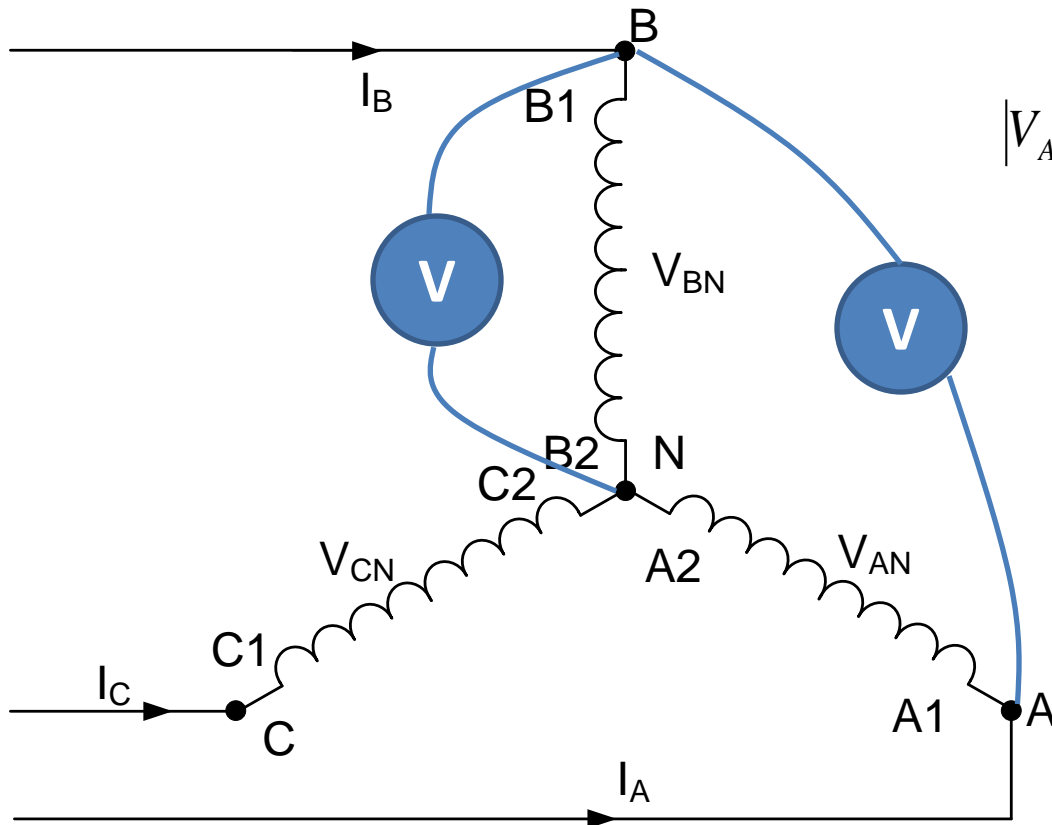


Phase voltage

$$|V_{AN}| = |V_{BN}| = |V_{CN}| = V_{ph}$$

Line voltage

$$\begin{aligned}\overline{V_{AB}} &= V_A - V_B \\ &= V_A - V_N - V_B + V_N \\ &= (V_A - V_N) - (V_B - V_N) \\ &= \overline{V_{AN}} - \overline{V_{BN}}\end{aligned}$$

STAR connection

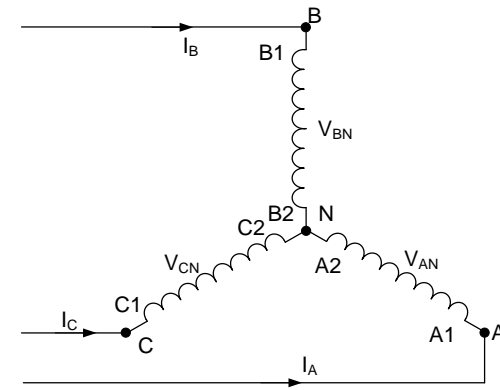

Line voltage

$$V_L = \overline{V_{AB}} = \overline{V_{AN}} - \overline{V_{BN}}$$

$$|V_{AB}| = \sqrt{|V_{AN}|^2 + |V_{BN}|^2 + 2 \times |V_{AN}| \times |V_{BN}| \cos 60^\circ}$$


$$= \sqrt{V_{ph}^2 + V_{ph}^2 + 2 \times V_{ph} \times V_{ph} \times \frac{1}{2}}$$

$$= \sqrt{V_{ph}^2 + V_{ph}^2 + V_{ph}^2}$$


$$= \sqrt{3V_{ph}^2}$$

$$= \sqrt{3}V_{ph}$$
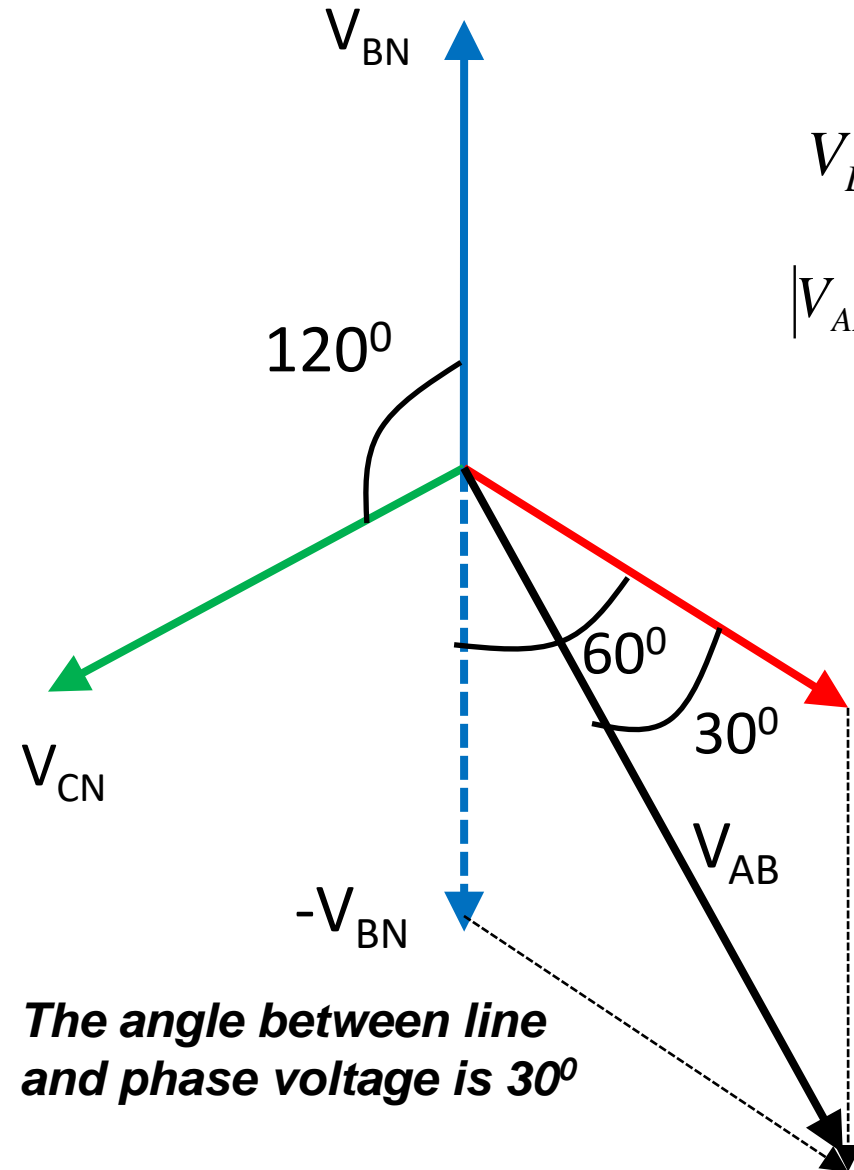
$$\boxed{V_L = \sqrt{3}V_{ph}} \text{ For balanced system}$$



STAR connection

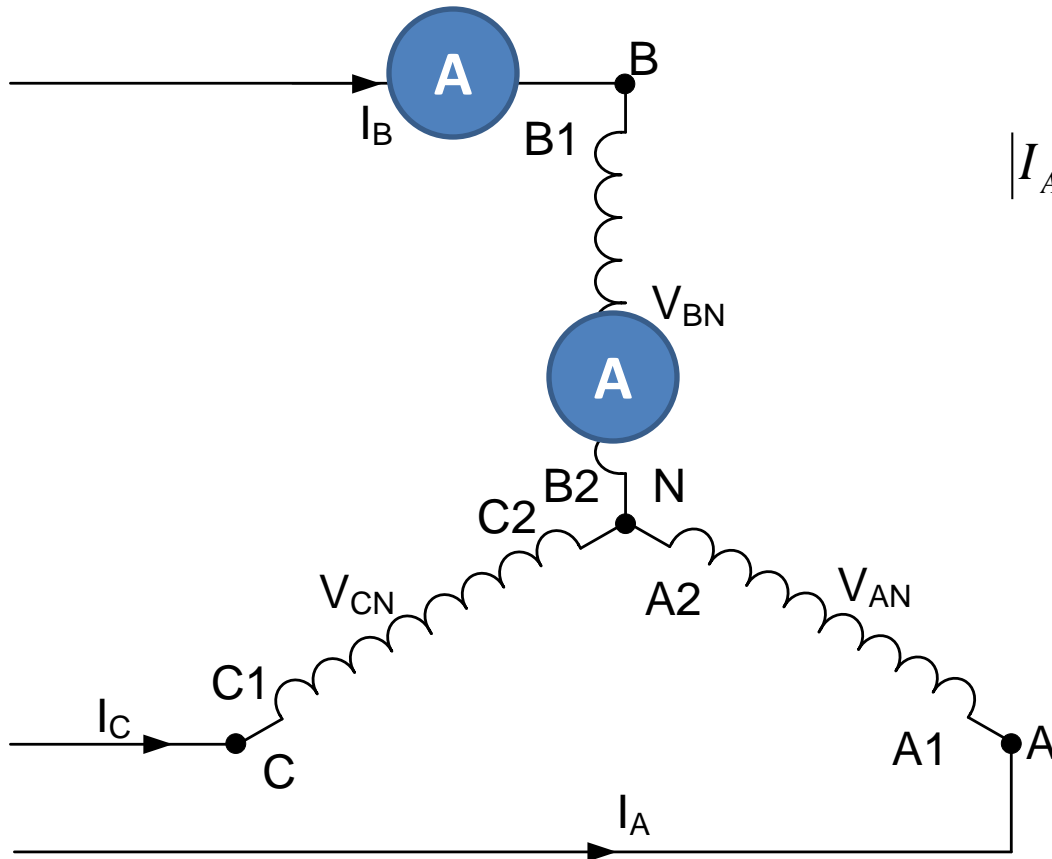

Phase current

$$|I_{AN}| = |I_{BN}| = |I_{CN}| = I_{ph}$$

Line current

$$|I_A| = |I_B| = |I_C| = I_L$$

$$I_L = I_{ph}$$

In a balanced star connected system, line currents are equal to phase currents, but line voltages are $\sqrt{3}$ times the phase voltages.