
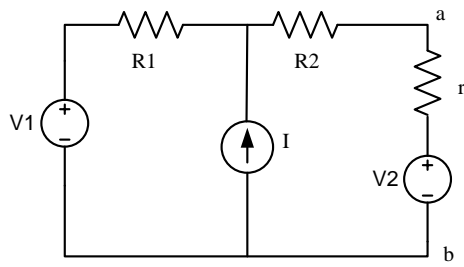


Solutions to Numerical Problems on DC Networks

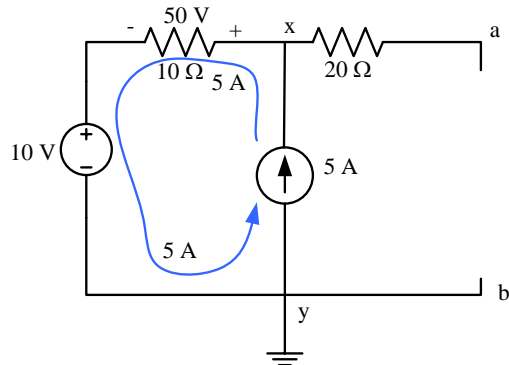
1. Find Thevenin's voltage across a-b terminal in the circuit given below. Also find the internal resistance across the open circuited a-b terminal, where $R_1 = 10\text{ohm}$, $R_2 = 20\text{ohm}$, $V_1 = 10\text{volt}$, $V_2 = 20\text{volt}$, $I = 5\text{A}$.



Solution:



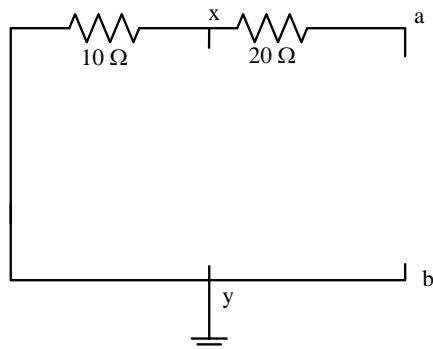
$$V_{Th} = V_{ab} = V_{xy} = 10 + 5 \times 10 = 60 \text{ V}$$




$$R_{Th} = R_{ab} = 20 + 10 = 30 \Omega$$

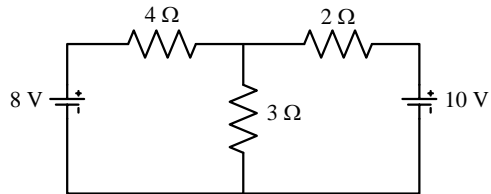2. Determine the current through the 3 ohm resistance by Superposition Theorem & verify using nodal analysis.




Solution:

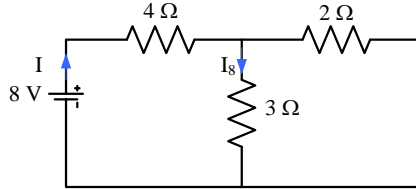

$$I = \frac{8}{4 + 3 // 2} = \frac{8}{4 + \frac{6}{5}} = \frac{40}{26} \text{ A}$$

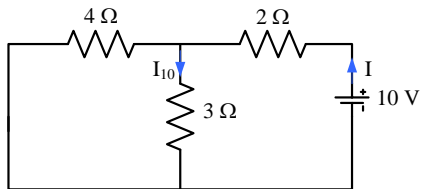
$$I_8 = I \times \frac{2}{2+3} = \frac{40}{26} \times \frac{2}{5} = \frac{16}{26} = 0.615 \text{ A}$$



$$I = \frac{10}{2 + 3 // 4} = \frac{10}{2 + \frac{12}{7}} = \frac{70}{26} \text{ A}$$

$$I_{10} = I \times \frac{4}{4+3} = \frac{70}{26} \times \frac{4}{7} = \frac{40}{26} = 1.538 \text{ A}$$
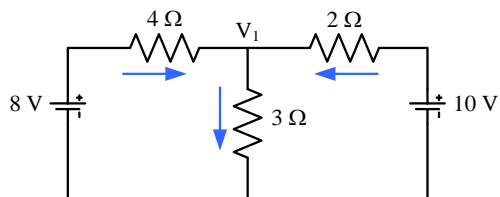
$$\therefore I_3 = I_8 + I_{10} = 0.615 + 1.538 = 2.153 \text{ A}$$




$$\frac{8 - V_1}{4} + \frac{10 - V_1}{2} = \frac{V_1}{3}$$


$$\text{or, } V_1 = 6.46 \text{ V}$$

$$\therefore I_3 = \frac{V_1}{3} = \frac{6.46}{3} = 2.153 \text{ A}$$

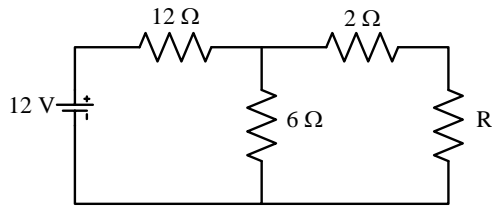
3. In the network, calculate the resistance R which will allow maximum power dissipated in it. Also calculate the maximum power.




Solution:

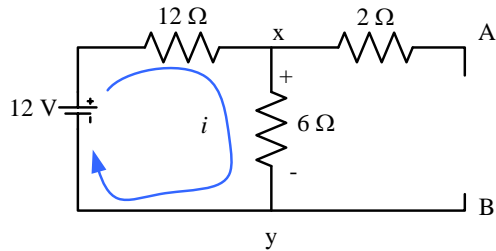
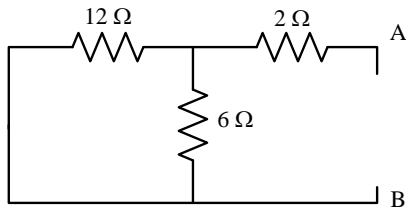
$$V_{Th} = V_{AB} = V_{xy} = 6 \times i = 6 \times \frac{12}{(12 + 6)} = 4 \text{ V}$$



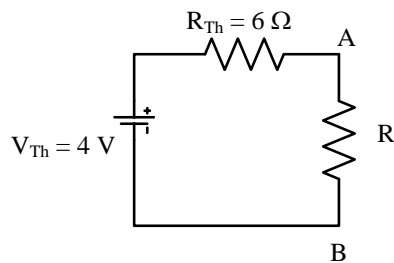
$$R_{Th} = R_{AB} = 2 + 12 // 6 = 2 + \frac{12 \times 6}{12 + 6} = 2 + 4 = 6 \Omega$$



For maximum power transfer, $R = R_{Th} = 6 \Omega$

$$\text{Maximum power, } P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{4^2}{4 \times 6} = 0.667 \text{ W}$$

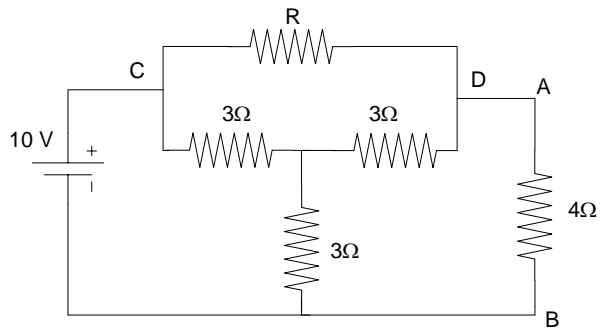
4. Determine the value of R in the following Figure such that the $4\ \Omega$ resistance consumes maximum power.




Solution:

For the resistance $4\ \Omega$, maximum power will be delivered to it when the current through it is maximum. Current through the $4\ \Omega$ is maximum in the circuit when the internal impedance of the circuit is zero. Thus value of $R = 0$.

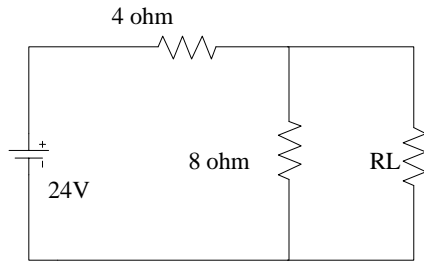
5. Find the value of load resistance (R_L) for which the power source will supply maximum power. Also find the value of maximum power for the network shown below:




Solution:

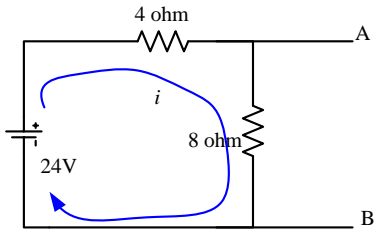
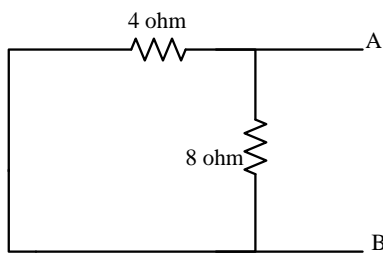
$$V_{Th} = V_{AB} = 8 \times i = 8 \times \frac{24}{(4 + 8)} = 16$$



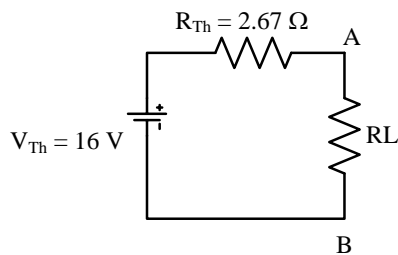
$$R_{Th} = R_{AB} = 4 // 8 = \frac{4 \times 8}{4 + 8} = 2.67 \Omega$$



For maximum power transfer, $R_L = R_{Th} = 2.67 \Omega$


$$\text{Maximum power, } P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{16^2}{4 \times 2.67} = 24 \text{ w}$$

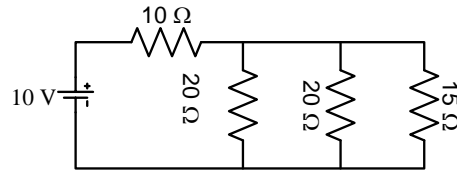6. Determine the current I_1 through the 15 ohm resistor in the network given by Norton's Theorem.




Solution:


Short circuit the 15 ohm resistance:

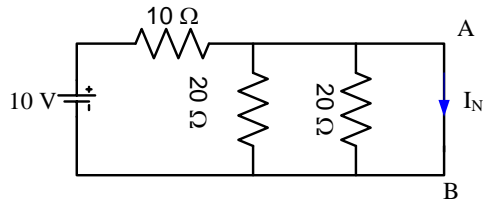

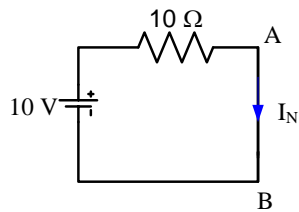
The two 20 ohm resistances in parallel with the short circuited path together becomes zero ohms:



$$I_N = \frac{10}{10} = 1 \text{ A}$$

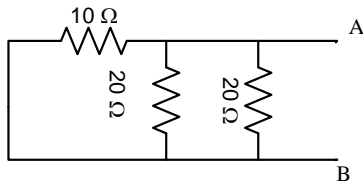

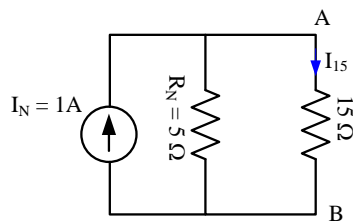
$$R_N = R_{AB} = (20 // 20) // 10 = 10 // 10 = 5 \Omega$$




$$I_{15} = 1 \times \frac{5}{5 + 15} = 0.25 \text{ A}$$

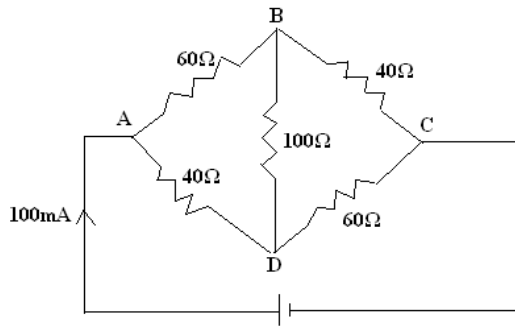7. Find the currents through R_{BC} , R_{CD} , R_{BD} in the following circuit:



Solution:

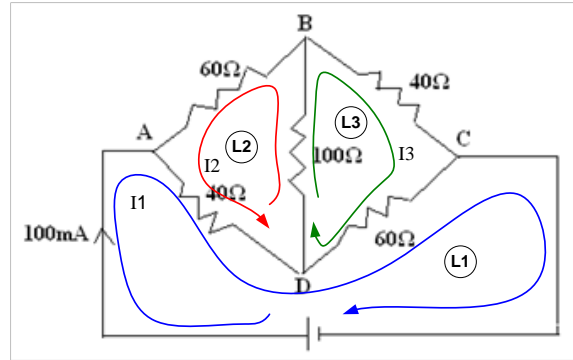

In Loop L1:

$$I_1 = 100$$

In Loop L2:

$$60I_2 + 40(I_2 + I_1) + 100(I_2 + I_3) = 0$$

$$\text{or, } 200I_2 + 100I_3 + 40I_1 = 0$$

$$\text{or, } 200I_2 + 100I_3 + 40 \times 100 = 0$$

$$\text{or, } 2I_2 + I_3 = -40 \quad (i)$$

In Loop L3:

$$40I_3 + 60(I_3 - I_1) + 100(I_2 + I_3) = 0$$

$$\text{or, } 200I_3 + 100I_2 - 60I_1 = 0$$

$$\text{or, } 200I_3 + 100I_2 - 60 \times 100 = 0$$

$$\text{or, } 2I_3 + I_2 = 60 \quad (ii)$$


Solving (i) and (ii):

$$I_2 = -140/3 \text{ mA}$$


$$I_3 = 160/3 \text{ mA}$$

$$\begin{aligned} \therefore I_{BD} &= -(I_2 + I_3) = -(-140/3 + 160/3) = -20/3 \text{ mA}, \\ I_{AD} &= (I_1 + I_2) = 100 - 140/3 = 160/3, \\ I_{AB} &= -I_2 = 140/3, \\ I_{DC} &= (I_1 - I_3) = 100 - 160/3 = 140/3 \text{ mA}, \\ I_{BC} &= I_3 = 160/3 \text{ mA} \end{aligned}$$

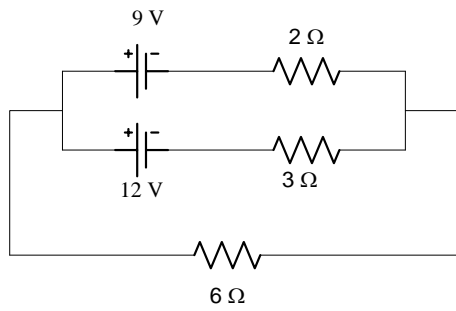8. Calculate the current flowing through the 6Ω resistor with the help of superposition theorem.




Solution:

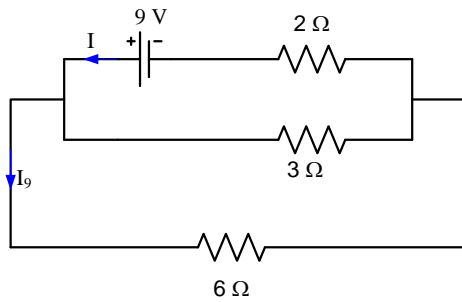

$$I = \frac{9}{6//3+2} = \frac{9}{\frac{18}{9}+2} = \frac{9}{4} \text{ A}$$
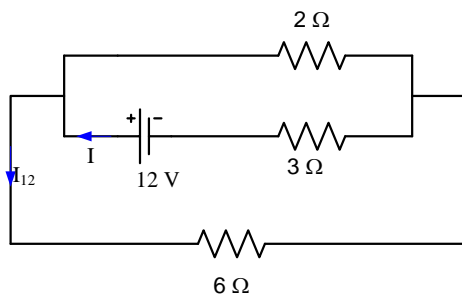
$$I_9 = \frac{9}{4} \times \frac{3}{3+6} = \frac{3}{4} \text{ A}$$




$$I = \frac{12}{6//2+3} = \frac{12}{\frac{12}{8}+3} = \frac{8}{3} \text{ A}$$

$$I_{12} = \frac{8}{3} \times \frac{2}{2+6} = \frac{2}{3} \text{ A}$$


$$\therefore I_6 = I_9 + I_{12} = \frac{3}{4} + \frac{2}{3} = \frac{17}{12} = 1.42 \text{ A}$$

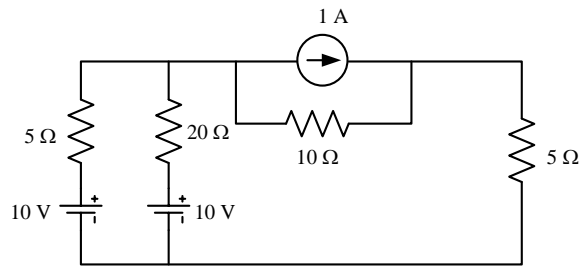9. Find the current through 5 Ω Resistor using Thevenin's Theorem in the fig. Below




Solution:

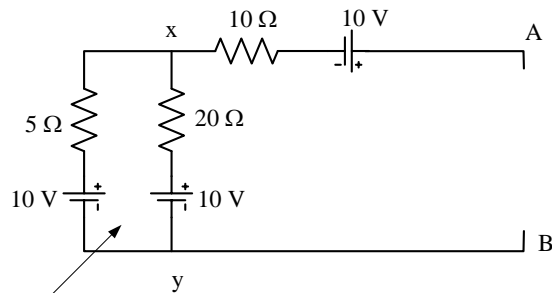Convert the 1 A current source to equivalent voltage source




No current in this loop
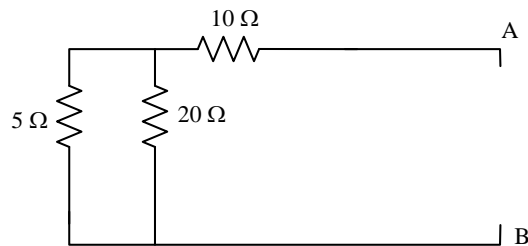
$$V_{Th} = V_{AB} = V_{Ax} + V_{xy} = 10 + 10 = 20 \text{ V}$$



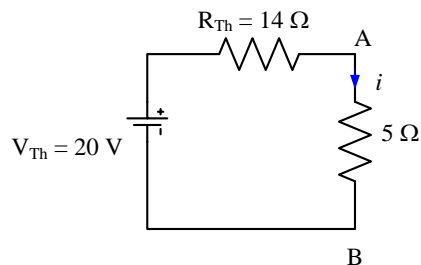
$$R_{Th} = R_{AB} = (5 // 20) + 10 = \frac{5 \times 20}{5 + 20} + 10 = 14 \Omega$$




$$i = \frac{20}{14 + 5} = 1.05 \text{ A}$$

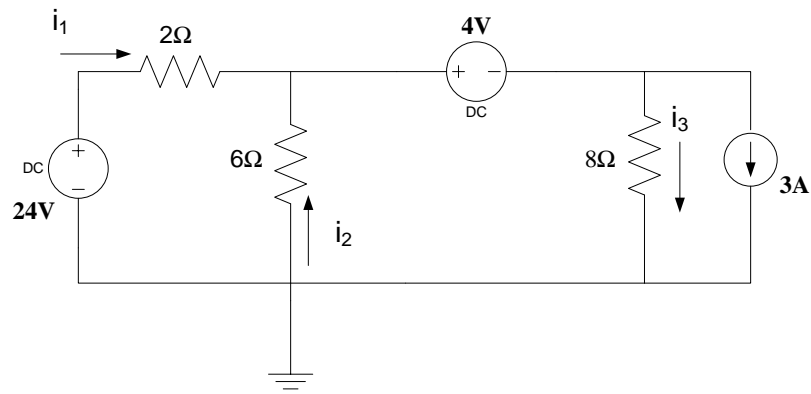10. For the circuit shown below, determine the currents i_1 , i_2 , i_3 using nodal analysis:



Solution:

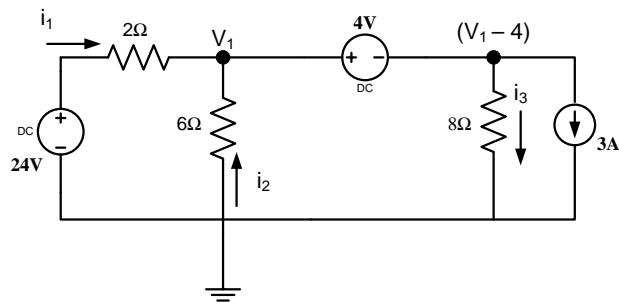

$$i_1 + i_2 = i_3 + 3$$

$$\frac{24 - V_1}{2} + \frac{0 - V_1}{6} = \frac{V_1 - 4}{8} + 3$$


$$\text{or, } V_1 = 12 \text{ V}$$

$$\therefore i_1 = \frac{24 - V_1}{2} = 6 \text{ A}$$


$$i_2 = \frac{0 - V_1}{6} = -2 \text{ A}$$

$$i_3 = \frac{V_1 - 4}{8} = 1 \text{ A}$$

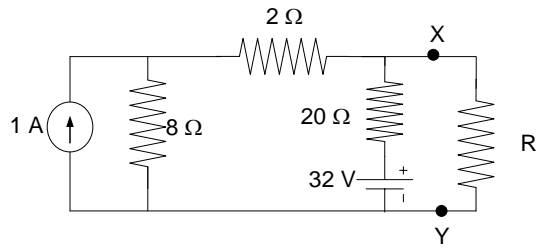11. Find the Thevenin's equivalent circuit of the following figure between the terminals X-Y.




Solution:

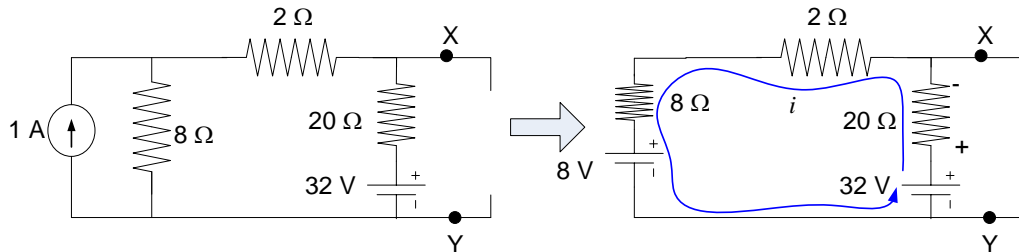


$$i = \frac{32 - 8}{20 + 2 + 8} = \frac{24}{30} \text{ A}$$

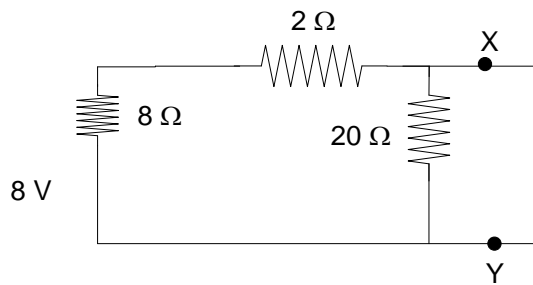
$$V_{Th} = V_{XY} = 32 - 20 \times i = 32 - 20 \times \frac{24}{30} = 32 - 16 = 16 \text{ V}$$




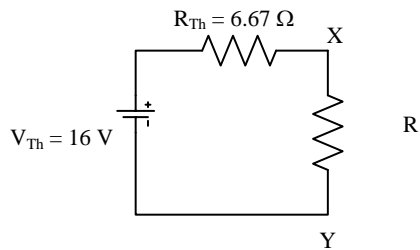
$$R_{Th} = R_{XY} = 20 \parallel (8 + 2) = \frac{20 \times 10}{20 + 10} = 6.67 \Omega$$



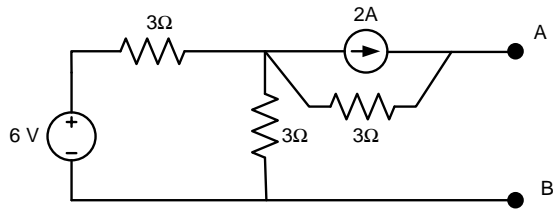
12. For the circuit shown in Figure determine equivalent source current and source resistance across A-B.



Solution:

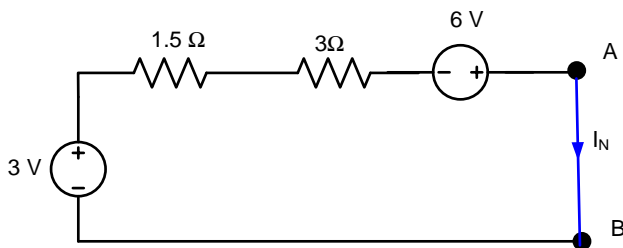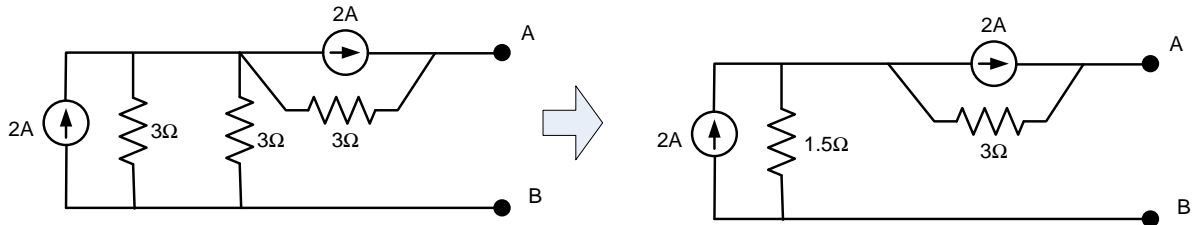

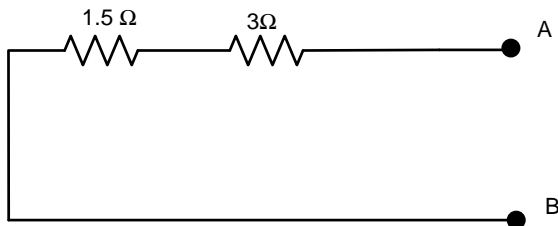
$$I_N = \frac{3+6}{1.5+3} = \frac{9}{4.5} = 2 \text{ A}$$




$$R_N = R_{AB} = 3 + 1.5 = 4.5 \Omega$$

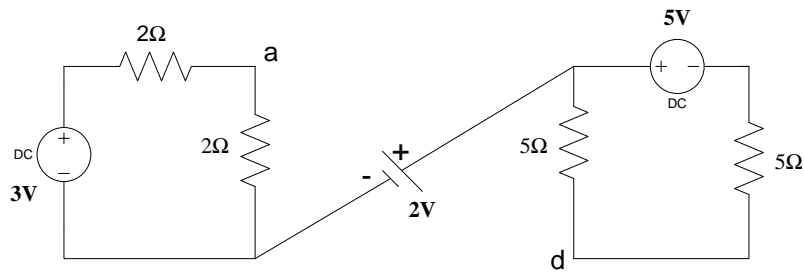13. For the circuit shown below, find the potential difference between a and d:



Solution:

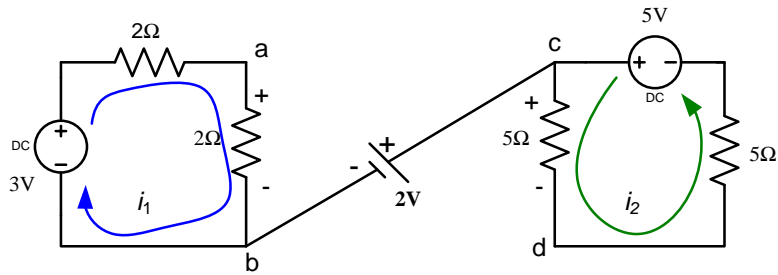

$$i_1 = \frac{3}{2+2} = 0.75 \text{ A}$$

$$i_2 = \frac{5}{5+5} = 0.5 \text{ A}$$

$$V_{ad} = V_{ab} + V_{bc} + V_{cd} = i_1 \times 2 - 2 + i_2 \times 5 = 0.75 \times 2 - 2 + 0.5 \times 5 = 1.5 - 2 + 2.5 = 2 \text{ A}$$