
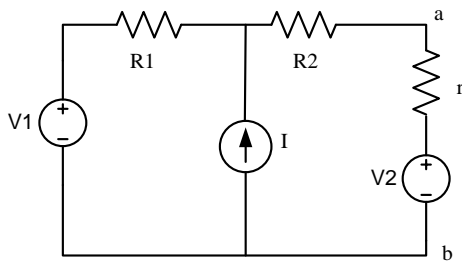


Numerical Problems on DC Networks

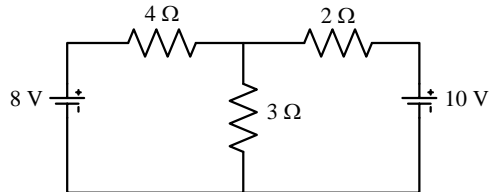
1. Find Thevenin's voltage across a-b terminal in the circuit given below. Also find the internal resistance across the open circuited a-b terminal, where $R_1 = 10\text{ohm}$, $R_2 = 20\text{ohm}$, $V_1 = 10\text{volt}$, $V_2 = 20\text{volt}$, $I = 5\text{A}$.




2. Determine the current through the 3 ohm resistance by Superposition Theorem & verify using nodal analysis.



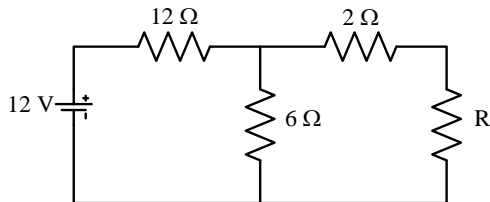
3. In the network, calculate the resistance R which will allow maximum power dissipated in it. Also calculate the maximum power.



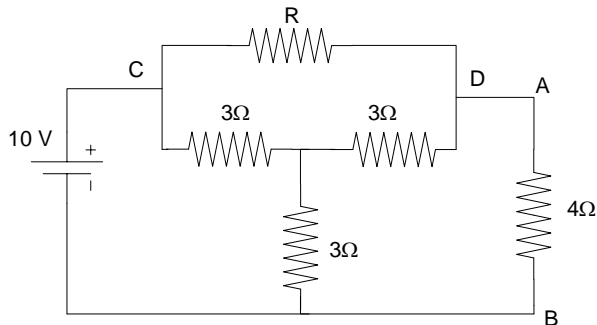
4. Determine the value of R in the following Figure such that the 4 ohm resistance consumes maximum power.



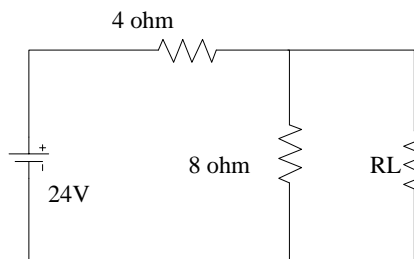
5. Find the value of load resistance (R_L) for which the power source will supply maximum power. Also find the value of maximum power for the network shown below:



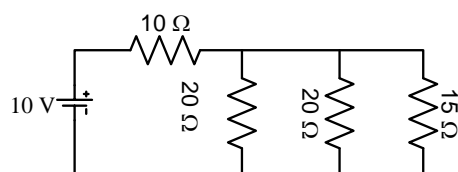
6. Determine the current I_1 through the 15 ohm resistor in the network given by Norton's Theorem.



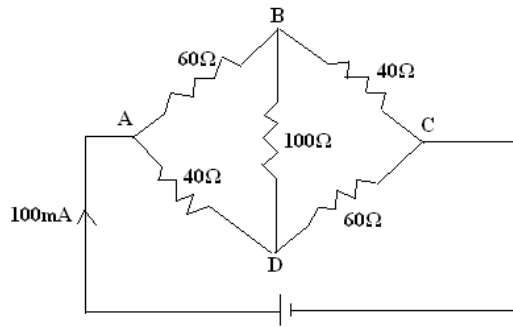
7. Find the currents through R_{BC} , R_{CD} , R_{BD} in the following circuit:



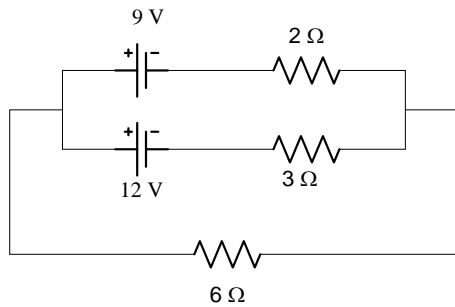
8. Calculate the current flowing through the 6Ω resistor with the help of superposition theorem.



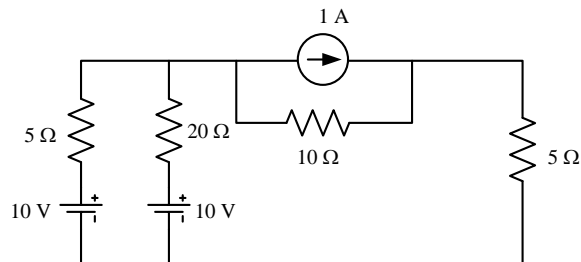
9. Find the current through 5Ω Resistor using Thevenin's Theorem in the fig. Below



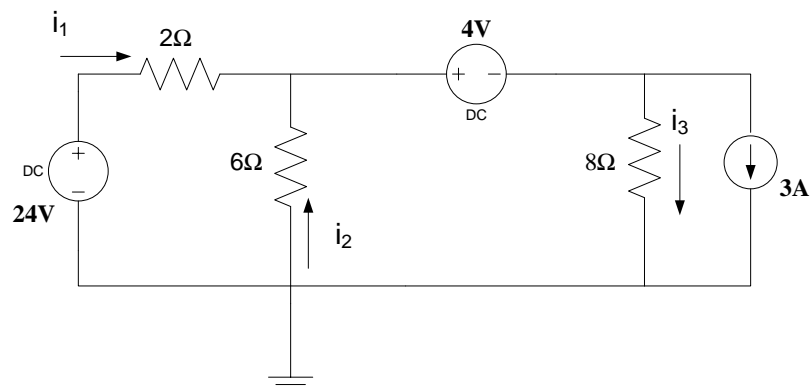
10. For the circuit shown below, determine the currents i_1 , i_2 , i_3 using nodal analysis:



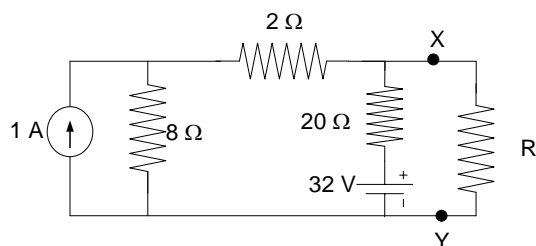
11. Find the Thevenin's equivalent circuit of the following figure between the terminals X-Y.



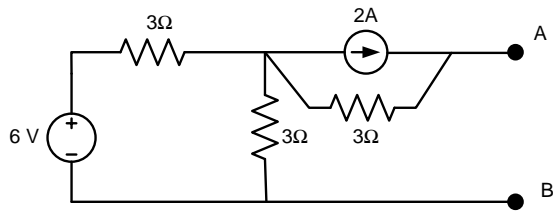12. For the circuit shown in Figure determine equivalent source current and source resistance across A-B.



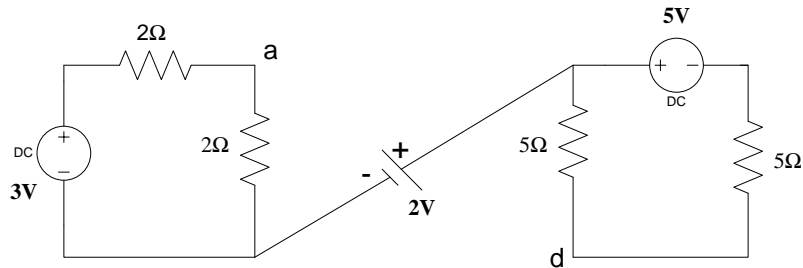13. For the circuit shown below, find the potential difference between a and d:



Answers:

1. 60 V, 30 ohm
2. 2.153 A
3. 6 ohm, 0.667 W
4. 0 ohm
5. 2.67 ohm, 24 W
6. 0.25 A
7. $I_{BC} = 160/3$ mA, $I_{DC} = 140/3$ mA, $I_{BD} = -20/3$ mA
8. 1.42 A
9. 1.05 A
10. $i_1 = 6$ A, $i_2 = -2$ A, $i_3 = 1$ A
11. $V_{th} = 16$ V, $R_{th} = 6.67$ ohm
12. $I_N = 2$ A, $R_N = 4.5$ ohm
13. 2 V