
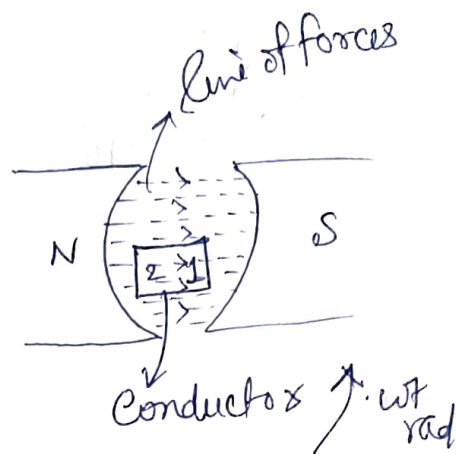


THREE PHASE AC

Introduction to 3 ϕ AC:-

Generation of 3 ϕ AC:-

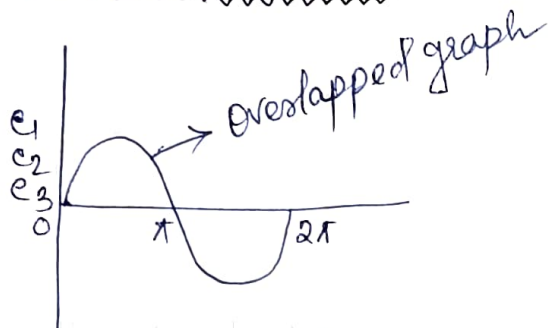

$$e = -N \cdot \frac{d\phi}{dt} \quad N_1 = N_2 = N_3$$



Magnetic field same, $\phi_1 = \phi_2 = \phi_3$

So, $e_1 = e_2 = e_3$.

$$\text{Phase difference angle} = \frac{360 \text{ Electrical degree}}{N (\text{no. of phase})}$$

$$\phi = \frac{360^\circ}{3} = 120^\circ$$

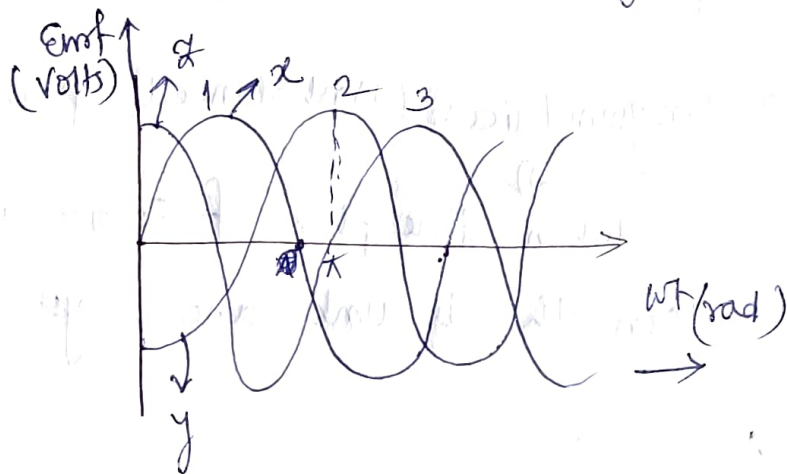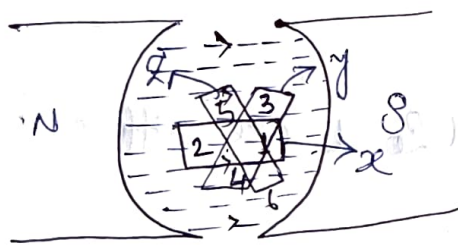For two phase, $\phi = \frac{360}{2} = 180^\circ$, So two phase AC not generated




$$\left. \begin{aligned} B &= \frac{\mu_0 \mu_r NI}{l} \\ H &= \frac{NI}{l} \end{aligned} \right\} \text{Constant}$$

$$e_1 = E_m \sin \omega t \quad \text{--- (1)}$$

$$e_2 = E_m \sin (\omega t - 2\pi/3) \quad \text{--- (2)}$$
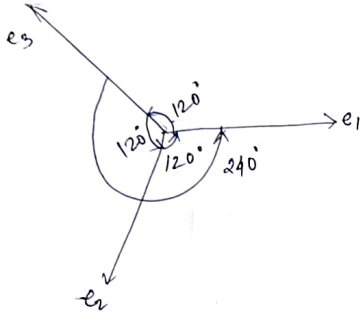
$$e_3 = E_m \sin (\omega t + 2\pi/3) \quad \text{--- (3)}$$



Phase Sequence: It's a sequence or order in which the alternating quantities attain their positive peak values.

R Y B
↓ ↓ ↓
Red Yellow ~~Black~~ Blue


Types of Three Phase AC:-

① Symmetrical (Balanced System)


Source Load
Three phase Three phase
Magnitude equal or
Impedance equal.

② Unsymmetrical (Unbalanced System)

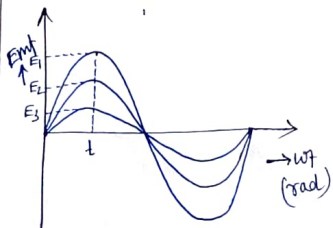When three phase of source and load are different then this is unbalanced system.



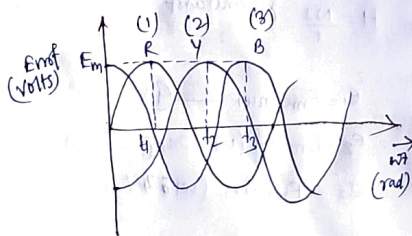(No phase diff due to same peak value in same time)




$$E_m = E_{m1} = E_{m2} = E_{m3}$$

R Y B → Positive Phase Sequence



B Y R → Negative phase Sequence.

∴ Connection of 3φ AC:-

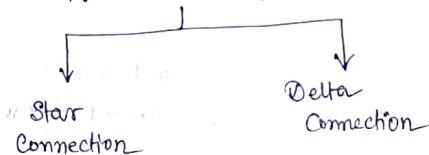

Star Connection:- (Balanced Circuit)

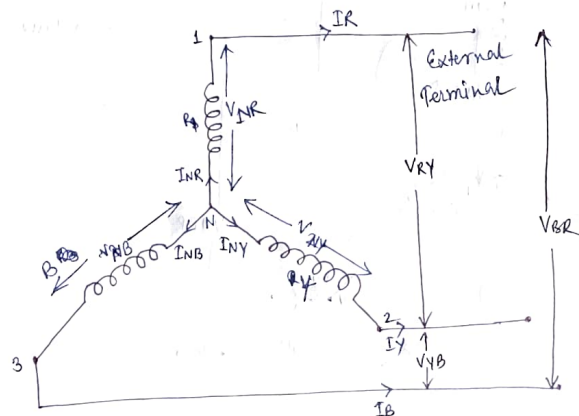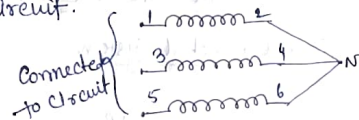It is a type of connection where one terminal from each winding is connected to a common point and the remaining three terminals are connected to the circuit.



3 Phase AC Generator ke Eise sab Current Outgoing hai.
 3 " " Motor " " Current ingoin incoming hai.

Line Quantities:


- (a) Line Voltages: $V_{RY} = V_{YB} = V_{BR} = V_L$
 (b) Line Current: $I_R = I_Y = I_B = I_L$

Phase Quantities:-

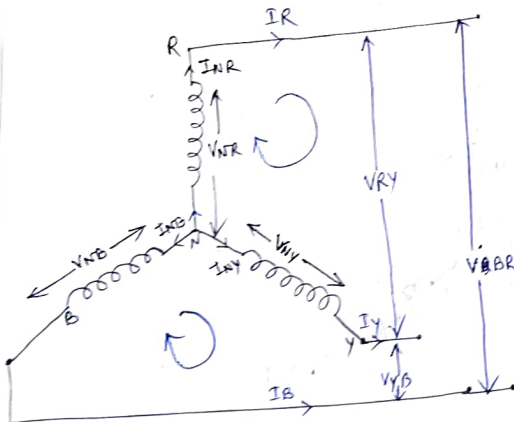- (a) phase Voltages: $V_{NR} = V_{NY} = V_{NB} = V_{ph}$
 (b) Phase Currents: $I_{NR} = I_{NY} = I_{NB} = I_{ph}$

(equal due to
Balanced System)

Relation between Line and Phase Quantity for a Balanced 3 ϕ Star Connected System:-



→ phase
→ line

For a Balanced 3 ϕ Connection:-

Line Currents: $I_R = I_Y = I_B = I_L$

Line Voltages: $V_{RY} = V_{YB} = V_{BR} = V_L$

(a) Relation between Line and Phase Currents:-

$$I_{NR} = I_R$$

$$I_{NY} = I_Y$$

$$I_{NB} = I_B$$

$$I_{ph} = I_L$$

(b) Relation b/w Line and Phase Voltages:-

Applying KVL in mesh NRYN,

$$\vec{V}_{NR} + \vec{V}_{RY} - \vec{V}_{NY} = 0$$

$$\Rightarrow \vec{V}_{RY} = \vec{V}_{NY} - \vec{V}_{NR} \quad \text{--- (i)}$$

Applying KVL in mesh NYBN,

$$-\vec{V}_{NB} + \vec{V}_{NY} + \vec{V}_{YB} = 0$$

$$\Rightarrow \vec{V}_{YB} = \vec{V}_{NB} - \vec{V}_{NY} \quad \text{--- (ii)}$$

Applying KVL in mesh NRBN,

$$\vec{V}_{NR} - \vec{V}_{BR} - \vec{V}_{NB} = 0$$

$$\Rightarrow \vec{V}_{BR} = \vec{V}_{NR} - \vec{V}_{NB} \quad \text{--- (iii)}$$

From eqn (i)


$$V_{RY} = \sqrt{V_{NY}^2 + V_{NR}^2 + 2V_{NY}V_{NR}\cos 60^\circ}$$

$$\Rightarrow V_L = \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph}^2\cos 60^\circ}$$

$$\Rightarrow V_L = \sqrt{3} V_{ph}$$


$$\therefore V_L = \sqrt{3} V_{ph}$$

Phasor Diagram:-

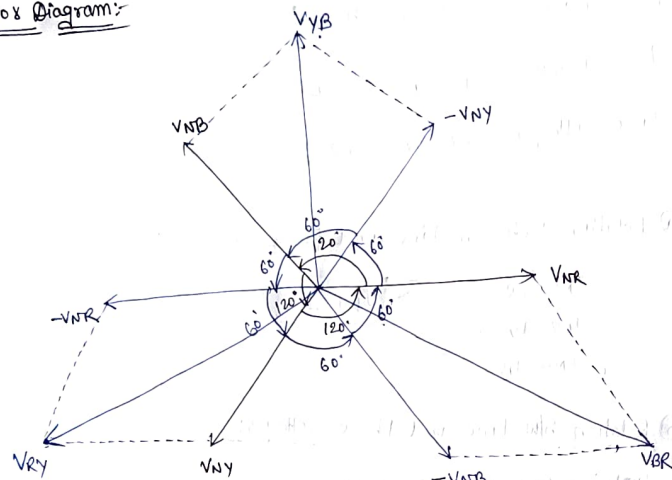

Delta Connection:-

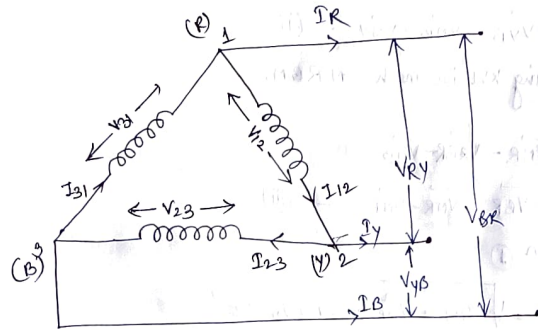→ It is a type of connection of 3 ϕ windings where all the coils are connected in a back to back arrangement.



Line Quantities:-

(a) Line Voltages:- $V_{RY} = V_{YB} = V_{BR} = V_L$

(b) Line Currents:- $I_R = I_Y = I_B = I_L$

Phase Quantities:-

(a) Phase Voltages:- $V_{12} = V_{23} = V_{31} = V_{ph}$

(b) Phase Currents:- $I_{12} = I_{23} = I_{31} = I_{ph}$

Relation B/w Line and Phase Voltages:-

$$V_{RY} = V_{12} \quad \text{--- (i)}$$

$$V_{YB} = V_{23} \quad \text{--- (ii)}$$

$$V_{BR} = V_{31} \quad \text{--- (iii)}$$

$$V_L = V_{ph}$$

Reln b/w Line & phase Currents:-

By Applying KCL at jn R,

$$\vec{I}_{31} - \vec{I}_{12} - \vec{I}_R = 0$$

$$\Rightarrow \vec{I}_R = \vec{I}_{31} - \vec{I}_{12}$$

Applying KCL at jn Y,

$$\vec{I}_{12} - \vec{I}_{23} - \vec{I}_Y = 0$$

$$\Rightarrow \vec{I}_Y = \vec{I}_{12} - \vec{I}_{23}$$

Applying KCL at jn B,

$$-\vec{I}_{31} + \vec{I}_{23} - \vec{I}_B = 0$$

$$\Rightarrow \vec{I}_B = \vec{I}_{23} - \vec{I}_{31}$$


Taking eqn (3),

$$I_R = \sqrt{(I_{31})^2 + (I_{12})^2 + 2 I_{31} I_{12} \cos \phi}$$

$$\Rightarrow I_L = \sqrt{I_{ph}^2 + I_{ph}^2 + 2 I_{ph}^2 \cos \phi \cos 60^\circ}$$

$$\Rightarrow I_L = \sqrt{3} I_{ph}$$

Phasor Diagram:-

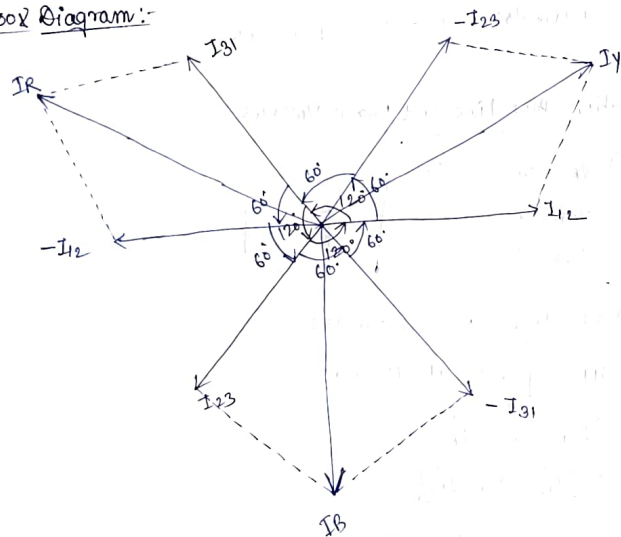


÷ Power in 3φ AC Circuit ÷

(a) Active Power (P) = $V_{rms} I_{rms} \cos \phi$

(b) Reactive Power (Q) = $V_{rms} I_{rms} \sin \phi$

(c) Apparent power (S) = $V_{rms} I_{rms}$

Star Connection

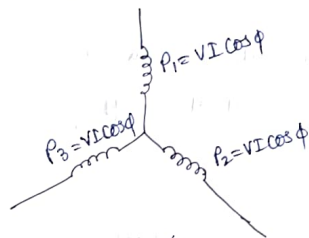


$$V_1 = V_2 = V_3 = V_{ph}$$

$$I_1 = I_2 = I_3 = I_{ph}$$

$$P_T = 3 V_{ph} I_{ph} \cos \phi$$

Delta Connection

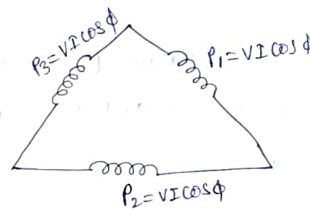

$$V_1 = V_2 = V_3 = V_{ph}$$

$$I_1 = I_2 = I_3 = I_{ph}$$

$$P_T = 3 V_{ph} I_{ph} \cos \phi$$

Power in 3φ AC

Terms of Phase Quantity

Terms of line Quantity

(i) A.P = $3 V_{ph} I_{ph} \cos \phi$ (Watts)

(ii) R.P = $3 V_{ph} I_{ph} \sin \phi$ (VAR)

(iii) Apparent P = $3 V_{ph} I_{ph} \cos \phi$ (VA)

Same of Star & Delta Connⁿ.

* Star

$$I_L = I_{ph}$$

$$V_L = \sqrt{3} V_{ph}$$

$$P_{lin} = 3 \cdot \frac{V_L}{\sqrt{3}} \cdot I_L \cos \phi$$

$$\Rightarrow P_{lin} = \sqrt{3} V_L I_L \cos \phi$$

Delta

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

$$P_{lin} = \sqrt{3} V_L I_L \cos \phi$$


Same for Star & Delta.

∴ Numericals on 3 phase ac circuits ∴

Q If a 3 ϕ Balanced star connected system is having a coil of resistance 10Ω and inductance 0.75 mH at a supply of 31 . Calculate —

- Total Impedence
- Total Supply Voltage
- Net power
- Phasors

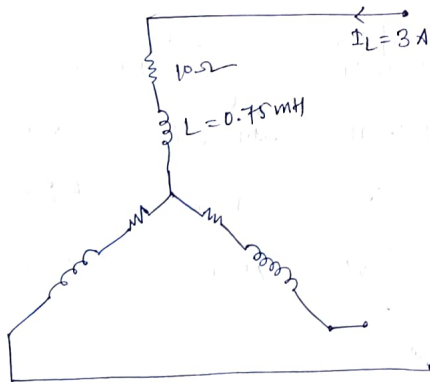Δ Always in term of phase
 $V, I, P \rightarrow$ always calculate in line form until the question is in phase
 (resistor enter phase 0°)



$$R = 10\Omega, \quad L = 0.75 \times 10^{-3} \text{ H}$$

$$X_L = 2\pi f L = 2\pi \times 50 \times 0.75 \times 10^{-3}$$

$$= 0.235\Omega$$

$$(a) \text{ Impedence } (Z_{ph}) = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{10^2 + 0.235^2}$$

$$= 10.002\Omega$$

$$(2) \cdot V_L = I_L \times Z_{ph}$$

$$\therefore V_{ph} = I_{ph} \times Z_{ph}$$

$$I_{ph} = I_L = 3\text{ A for } 3\phi \text{ balanced star connected system.}$$

$$V_{ph} = 3 \times 10.002 = 30.006\text{ V}$$

$$V_L = \sqrt{3} \cdot V_{ph} = \sqrt{3} \times 30.006\text{ V}$$

$$= 51.971\text{ V.}$$

$$(3) \text{ Net power } (P) = \sqrt{3} \times V_L I_L \cos \phi$$

$$= \sqrt{3} \times 51.971 \times 3 \times 0.999\text{ W}$$

$$= 269.779\text{ W.}$$

$$\cos \phi = \frac{R}{Z_{ph}}$$


$$= \frac{10}{10.002} = 0.999$$

(4) Phasors

$$V_m = 51.971 \times \sqrt{2} = 73.498\text{ V} = V_{m1} = V_{m2} = V_{m3}$$

$$I_m = 3 \times \sqrt{2} = 4.242\text{ A} = I_{m1} = I_{m2} = I_{m3}$$

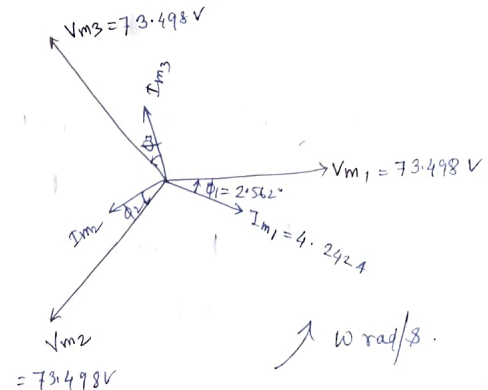
$$\phi = \cos^{-1}(0.999) = 2.562^\circ = \phi_1 = \phi_2 = \phi_3$$



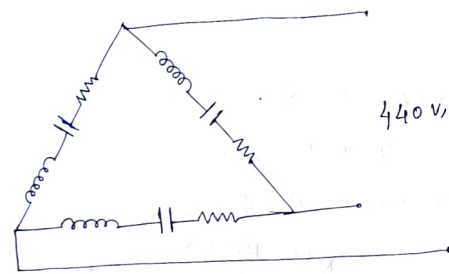8. If a load of $Z = 3 - j7 - 5$ in series with an inductor of 5Ω is connected in a balanced 3-phase delta connection across 440V, 50Hz supply. Then calculate —

- Total Impedance
- Net Supply Current
- If same load at same current is connected in 3-phase balanced star formation. Find its KVAR Rating.
- Phasor

→ $R = 3\Omega$, $X_C = 7\Omega$, $X_L = 5\Omega$, $V_L = 440V$, $f = 50Hz$.



$$\textcircled{1} Z_T = Z_{ph} = \sqrt{R^2 + (X_C - X_L)^2} = \sqrt{9 + 4} \quad \{X_C > X_L\}$$

$$= \sqrt{13} = 3.605\Omega$$

$$\textcircled{II} I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{440}{3.605} A \quad [\text{for delta, } V_L = V_{ph}]$$


$$= 122.052 A$$

$$I_L = \sqrt{3} I_{ph}$$

$$= \sqrt{3} \times 122.052$$

$$= 211.400 A$$

③

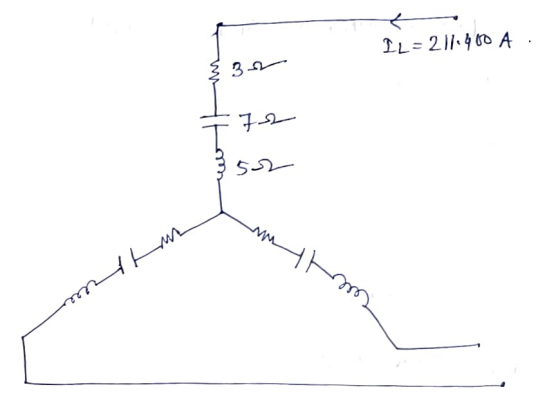

$$KVAR (\phi) = \sqrt{3} V_L I_L \sin \phi$$

Here use same load so, the Impedance will be same.

$$Z_{ph} = 3.605 A$$

$$I_L = 211.400 A$$

$$I_{ph} = 211.400 A \quad \{I_L = I_{ph} \text{ for star}\}$$

$$V_{ph} = I_{ph} \cdot Z_{ph} = 211.400 \times 3.605 V$$

$$= 762.097 V$$

$$V_L = \sqrt{3} \times 762.097 V$$

$$= 1319.990 V$$

$$\cos \phi = \frac{R}{Z} = \frac{3}{3.605} = 0.832$$

$$\Rightarrow \phi = 33.695^\circ$$

$$\therefore Q = \sqrt{3} \times 1319.990 \times 211.400 \times \sin(33.695^\circ)$$

$$= 268133.234 \text{ VAR}$$

$$= 268.133 \text{ KVAR.}$$

④ Phasor

$$V_m = 440 \times \sqrt{2} = 622.253 \text{ V}$$

$$I_m = \sqrt{2} \times 211.400 = 298.964 \text{ A}$$

$$\phi = 33.695^\circ$$

