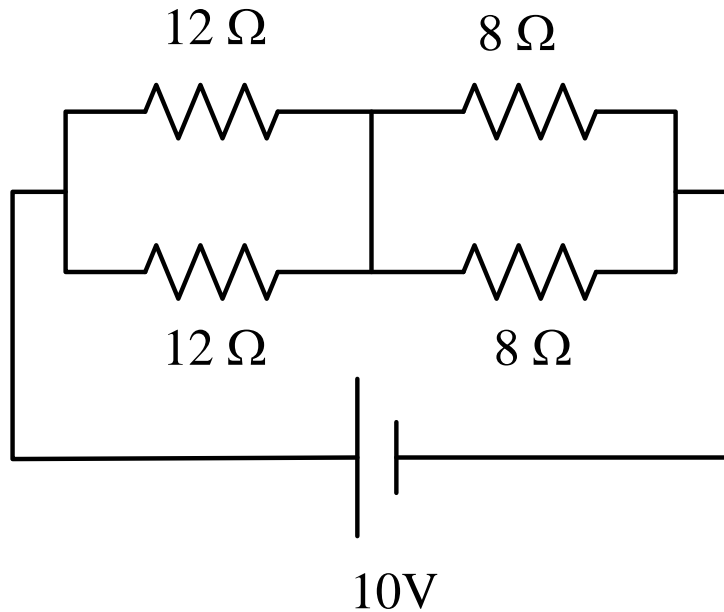


Tutorial 1



- ILOs
 - Solve numerical problems related to:
 - Series-parallel combination of resistances
 - Star-Delta transformation
 - Current & voltage division

Find current flowing out of the 10 V source.



Solution:



- 1st step: Redraw

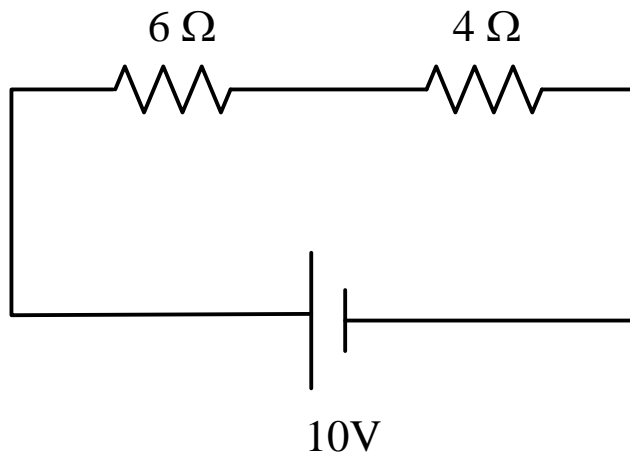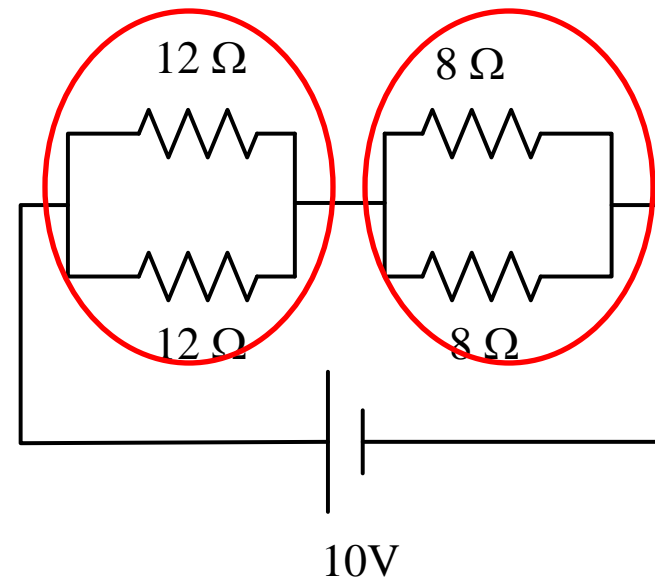

- 2nd step:
 $12 // 12 = 6$, $8 // 8 = 4$

Find current flowing out of the 10 V source.


- 3rd step: 6 and 4 in series

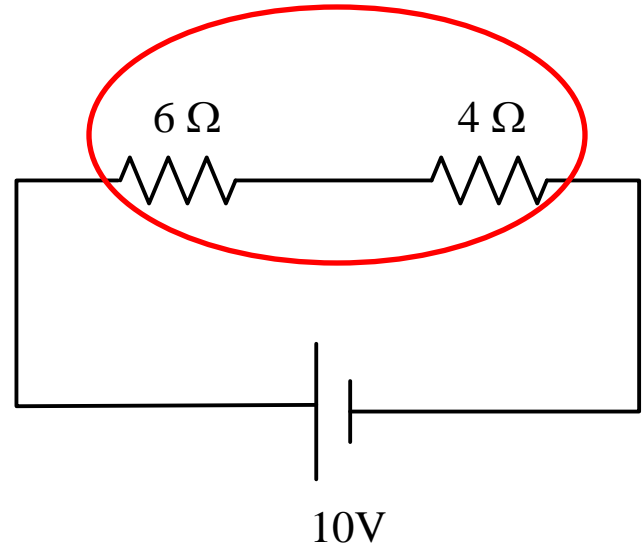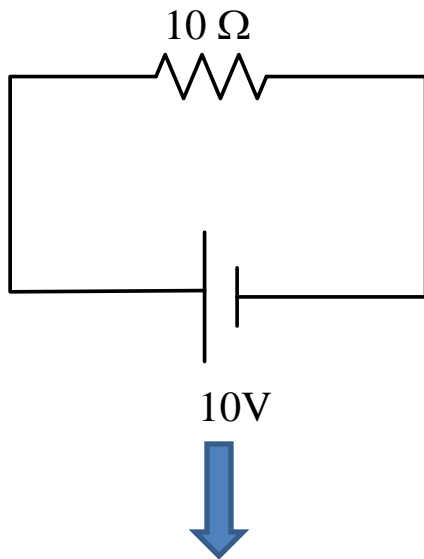

- Finally:

$$I = \frac{10}{10} = 1 \text{ A}$$

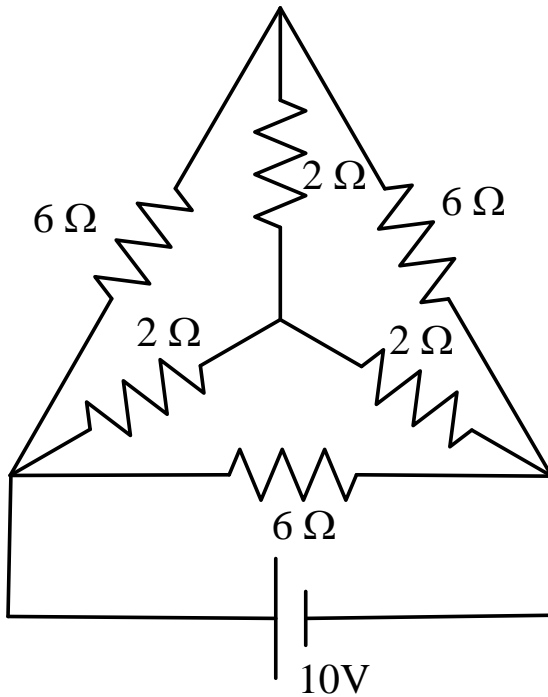Find current flowing out of the 10 V source.




Solution:


- It is almost impossible to find out equivalent resistance of the circuit by simple series-parallel combination.
 - In this case, it is necessary to introduce a new concept – called the **Star-Delta Transformation** technique.
-

Star-Delta Transformation

STAR network



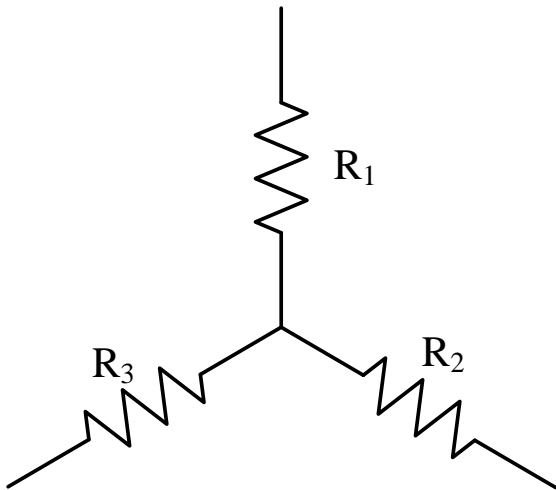


DELTA network

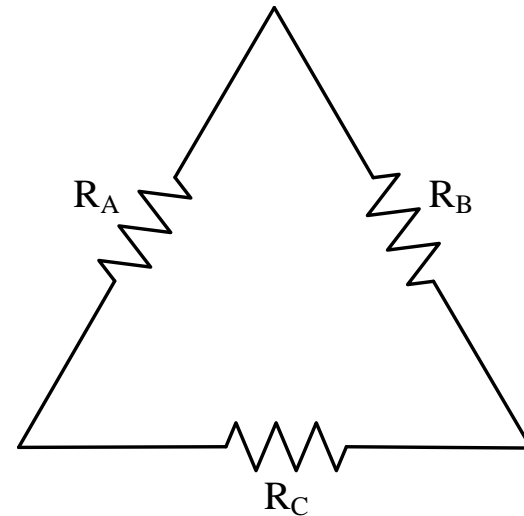

- It is possible to equivalently represent a star network by a delta network and vice versa without affecting the external signals.

Converting Star to Delta

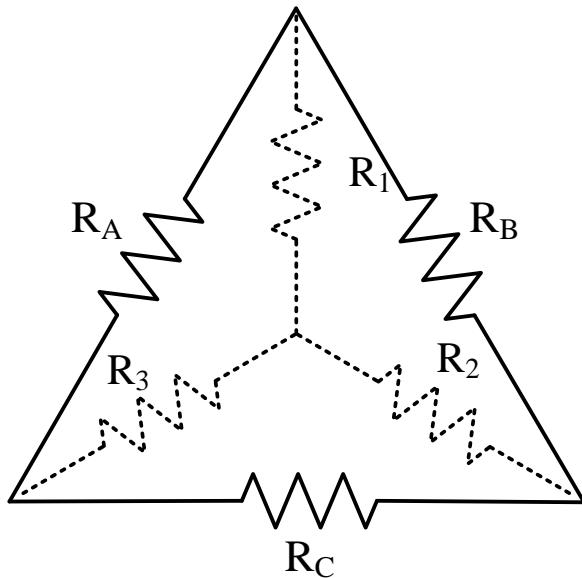
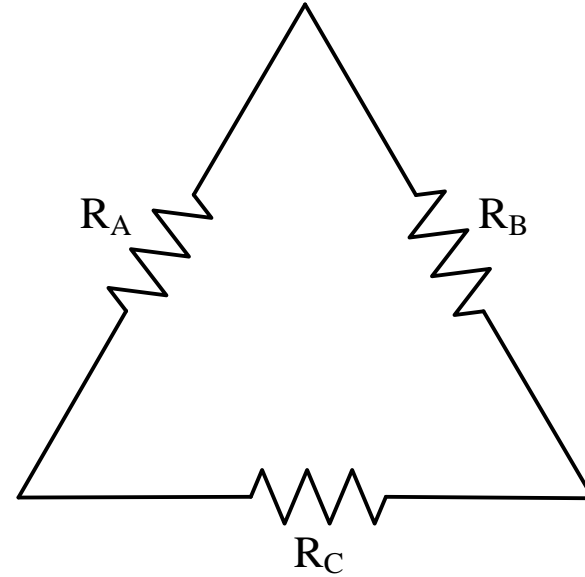
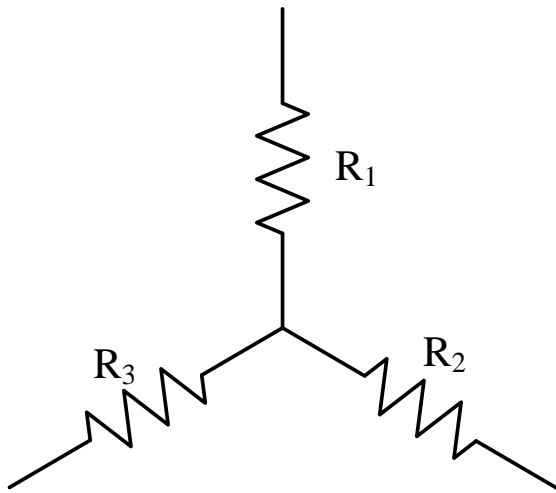


$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

Converting Delta to Star

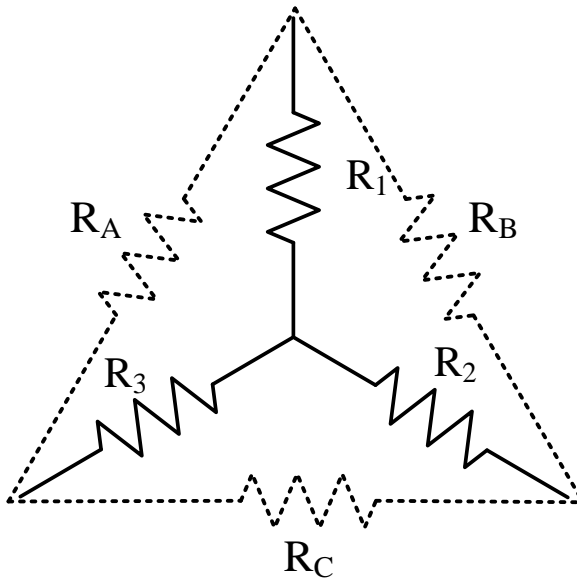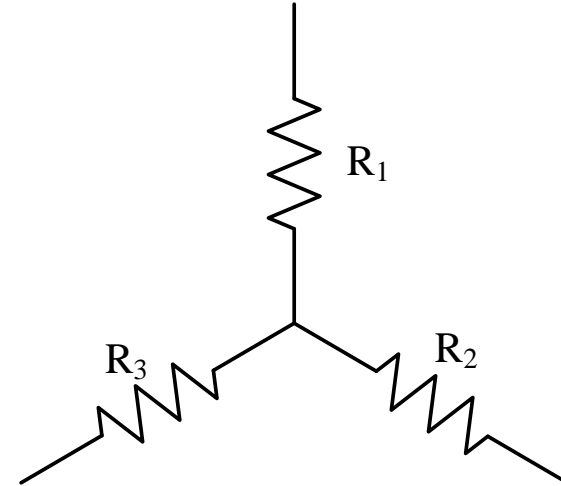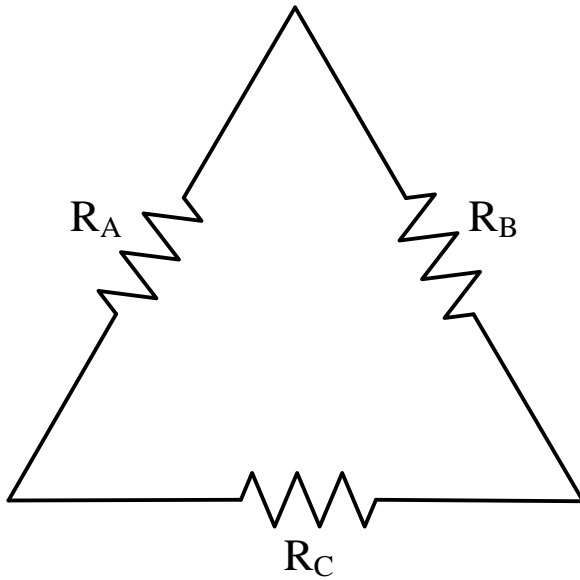

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$



$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_C R_A}{R_A + R_B + R_C}$$

Find current flowing out of the 10 V source.

Solution:

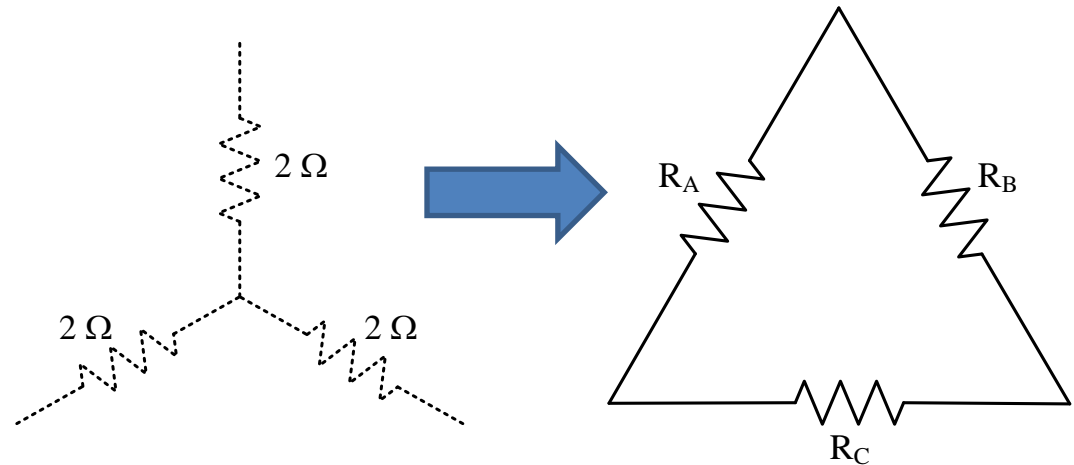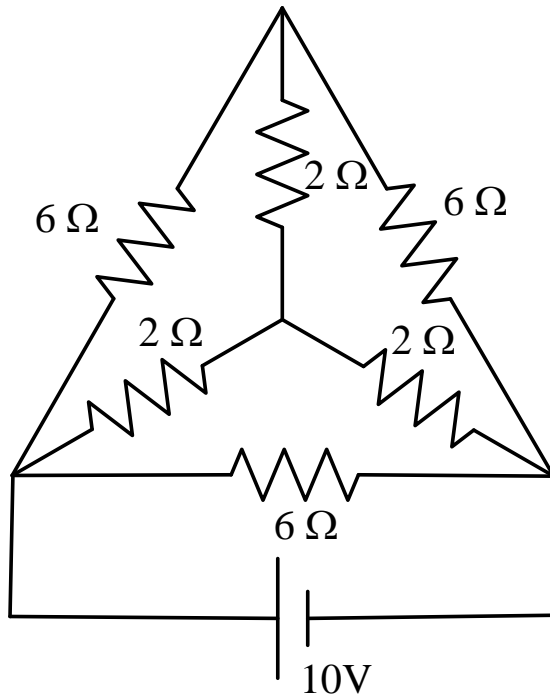Step 1: Convert the inner $2\ \Omega$ star network into its equivalent delta network.





$$R_A = R_B = R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{2 \times 2 + 2 \times 2 + 2 \times 2}{2} = 6\ \Omega$$

Find current flowing out of the 10 V source.

Solution:


Step 1: Convert the inner $2\ \Omega$ star network into its equivalent delta network.

$$R_A = R_B = R_C = 6\ \Omega$$

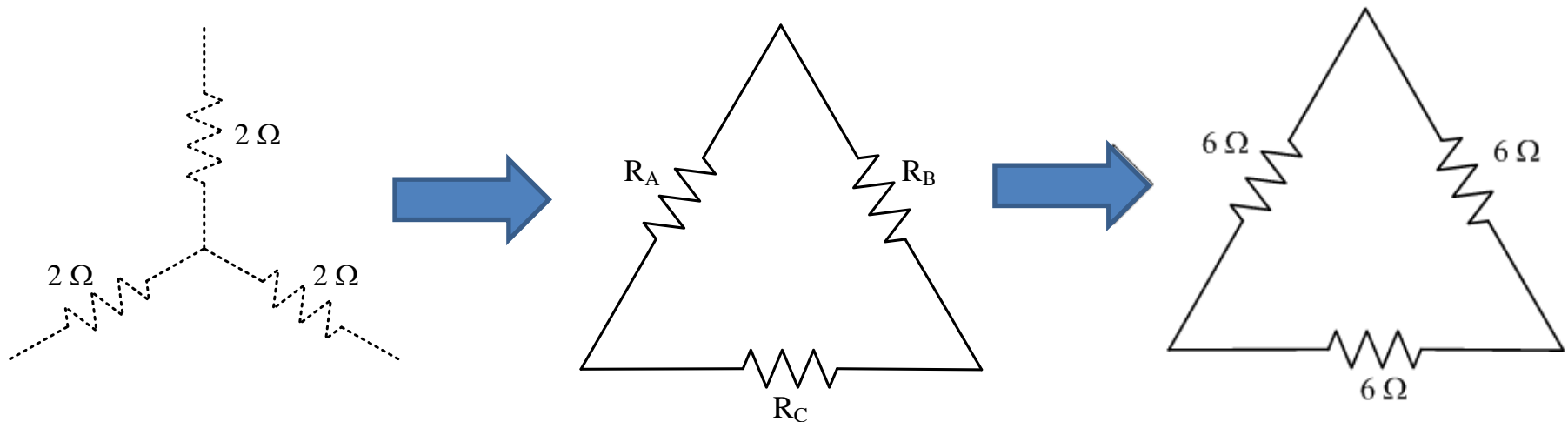
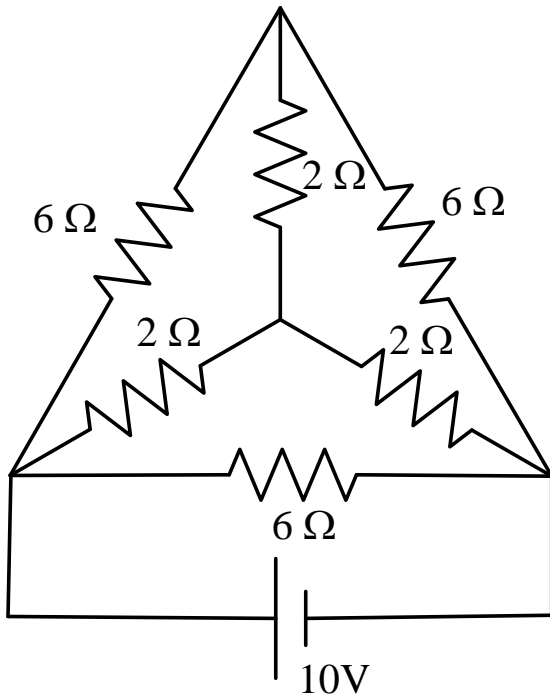


Step 2:



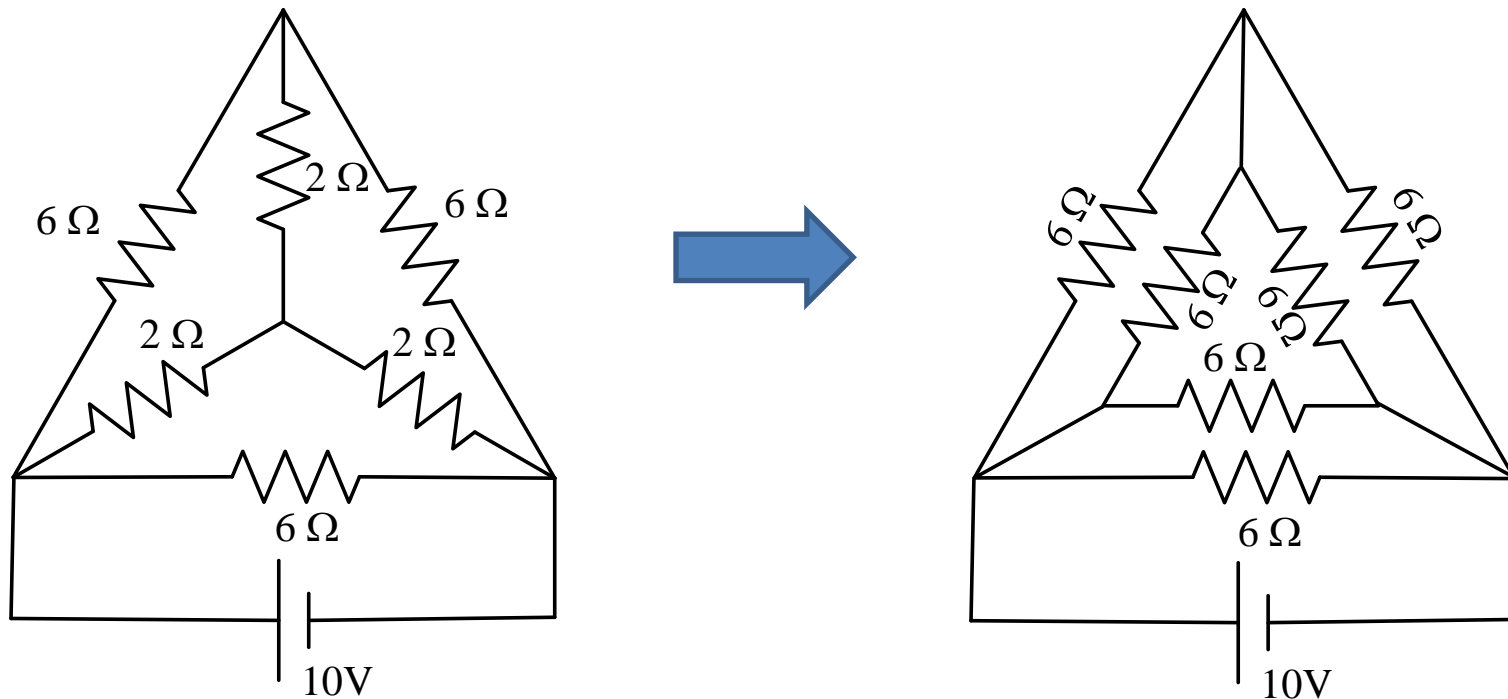
- The circuit already contains another delta network that is placed outside (6 ohm each).
- So the new delta (converted from 2 ohm star) and the original outer delta network now will be combined as shown below:



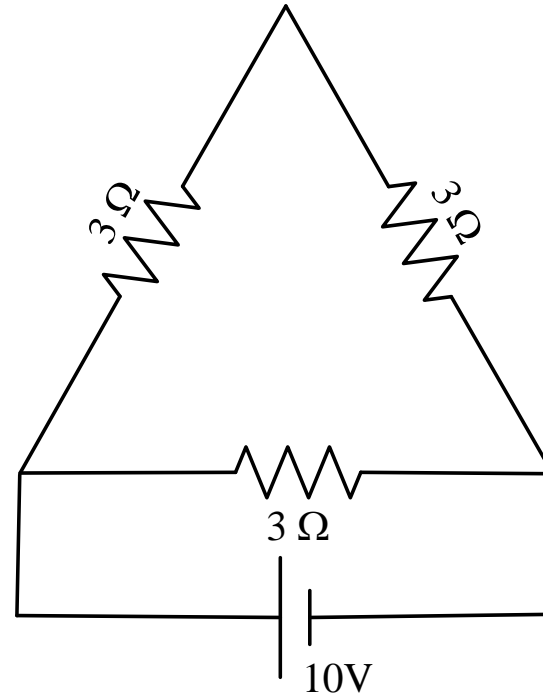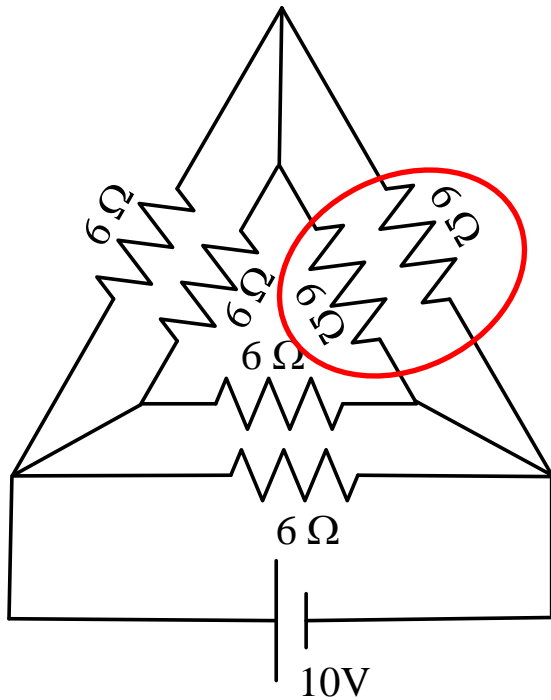Step 3: Two 6Ω resistances in parallel in each of the three arms
Thus, $6//6 = 3$






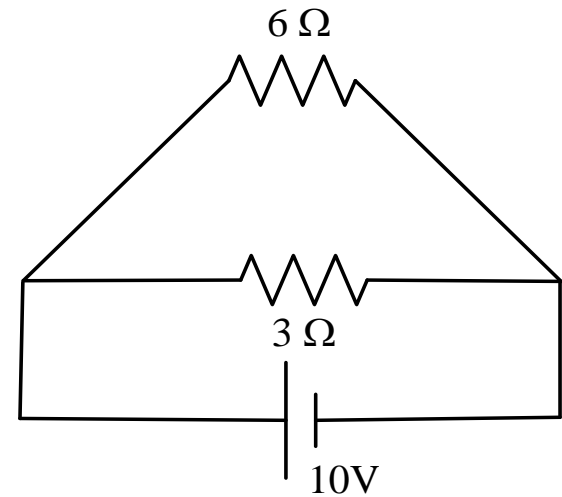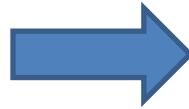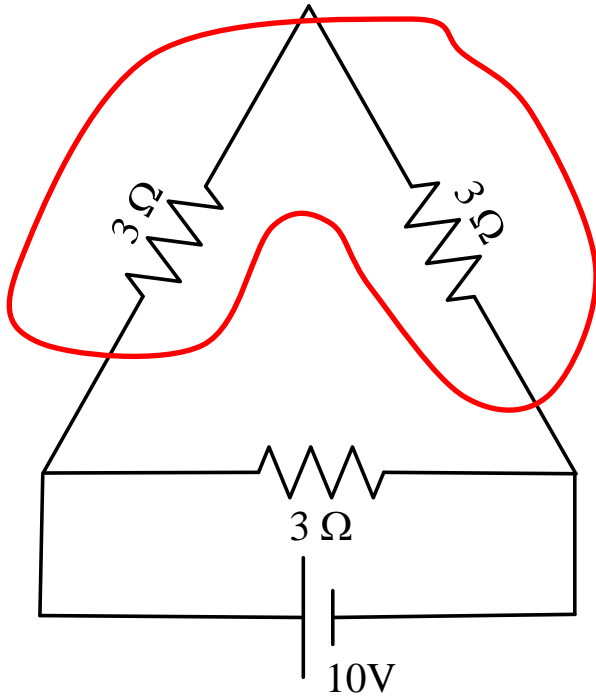Step 4: The two upper $3\ \Omega$ resistances are in series:



Step 5: The $6\ \Omega$ and $3\ \Omega$ resistances now become in parallel:

$$6//3 = \frac{6 \times 3}{6 + 3} = 2$$

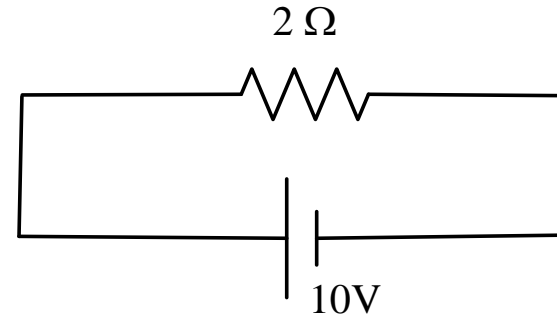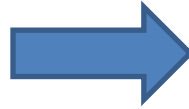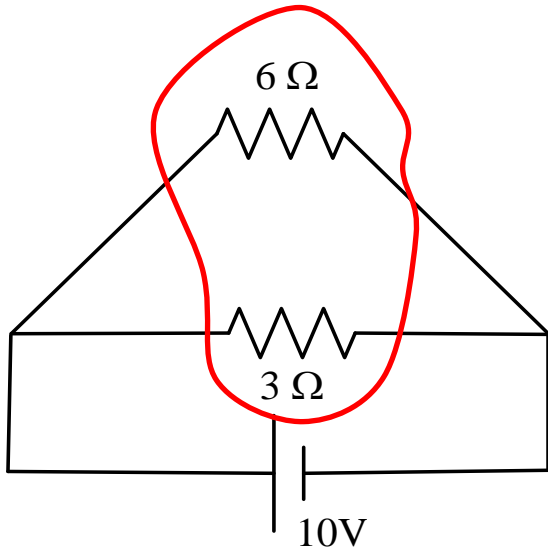


Step 6: Calculate current:

$$I = \frac{10}{2} = 5\ A$$

Voltage & current division

Voltage division in series circuit

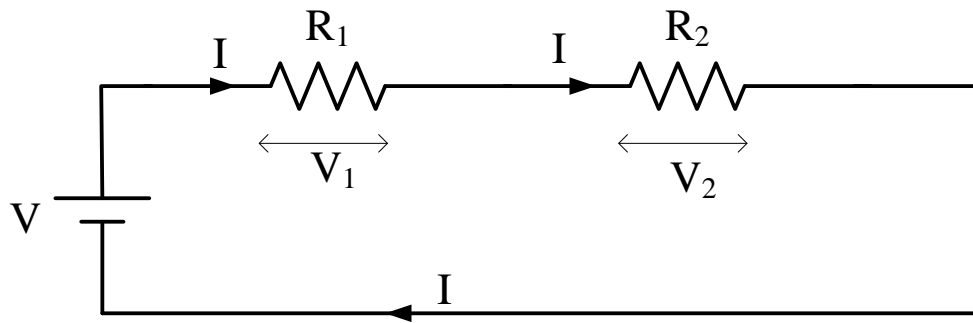- When two or more elements are connected in series, the total supply voltage gets divided among the individual elements.
- The share of voltage depends on the value of resistance.



$$V = V_1 + V_2$$

$$I = \frac{V}{R_1 + R_2}$$


Thus, voltage across a resistance in a series circuit is the total voltage multiplied by value of the own resistance divided by summation of all the resistances connected in series.

$$V_1 = IR_1 = \frac{V}{R_1 + R_2} R_1 = V \times \frac{R_1}{R_1 + R_2}$$

$$V_2 = IR_2 = \frac{V}{R_1 + R_2} R_2 = V \times \frac{R_2}{R_1 + R_2}$$

Current division in parallel circuit

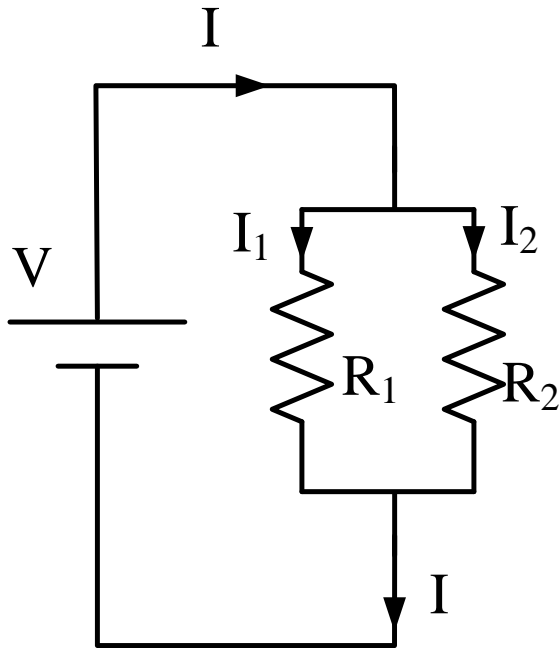- When two or more elements are connected in parallel, the total supply current gets divided among the individual elements.
- The share of current carried by each resistance depends on the value of resistance.



Two resistances connected in parallel

∴ Equivalent resistance:

$$\therefore R = \frac{R_1 R_2}{R_1 + R_2}$$

∴ Total supply current:

$$I = \frac{V}{R} = \frac{V}{\frac{R_1 R_2}{R_1 + R_2}}$$


$$\text{or, } I = V \times \frac{(R_1 + R_2)}{R_1 R_2}$$

$$\therefore V = I \times \frac{R_1 R_2}{R_1 + R_2}$$

Current division in parallel circuit

$$V = I \times \frac{R_1 R_2}{R_1 + R_2}$$

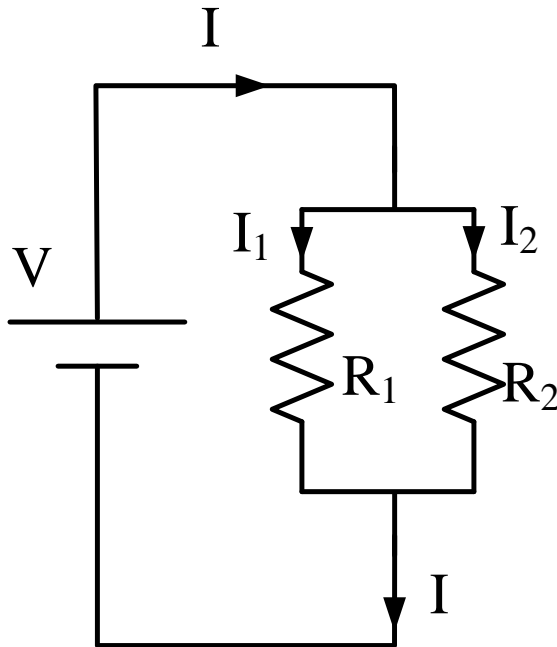Since the two resistances are connected in parallel, they get the same supply voltage V



$$V = I_1 R_1 = I_2 R_2$$


Total current is shared between the two

$$I = I_1 + I_2$$

$$I_1 = \frac{V}{R_1} = I \times \frac{R_1 R_2}{R_1 + R_2} \times \frac{1}{R_1} = I \times \frac{R_2}{R_1 + R_2}$$

$$I_2 = \frac{V}{R_2} = I \times \frac{R_1 R_2}{R_1 + R_2} \times \frac{1}{R_2} = I \times \frac{R_1}{R_1 + R_2}$$

Current division in parallel circuit

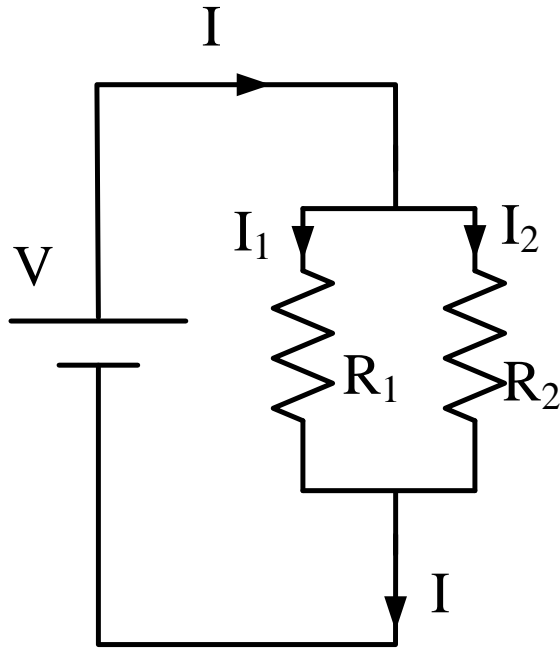


$$I_1 = I \times \frac{R_2}{R_1 + R_2}$$

$$I_2 = I \times \frac{R_1}{R_1 + R_2}$$


*Thus, current through a resistance in a parallel circuit is the total current multiplied by value of the **opposite resistance** divided by summation of the two resistances.*

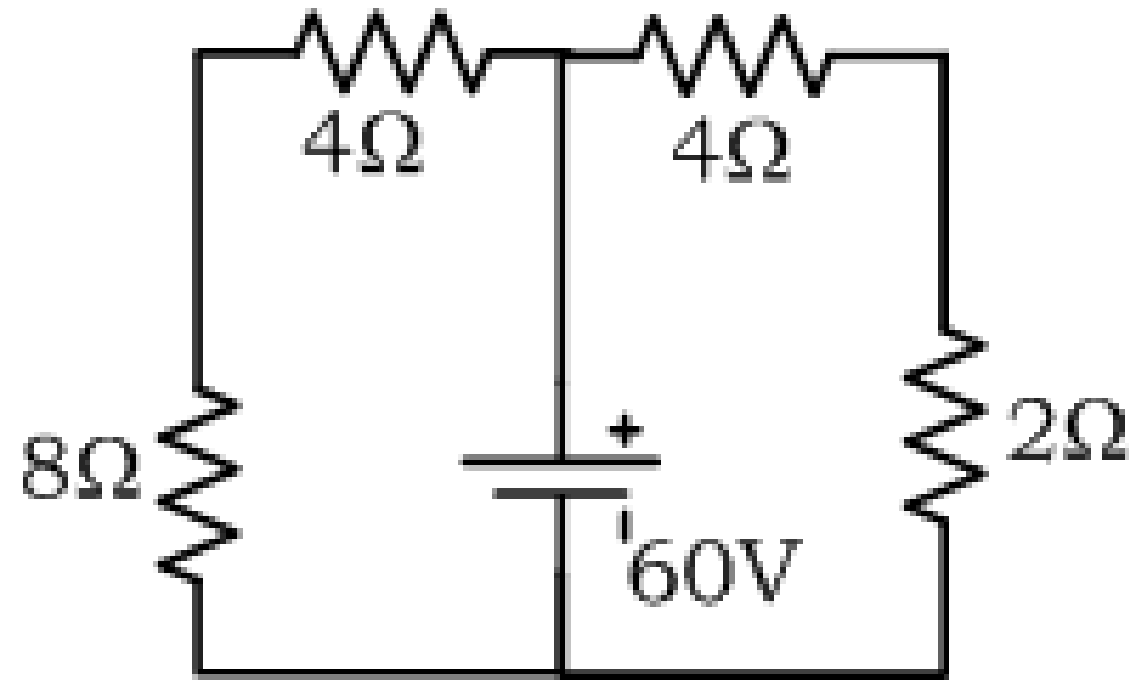In the circuit shown in figure , find the voltage across each element



In the circuit shown in figure , find the voltage across each element

Solution:

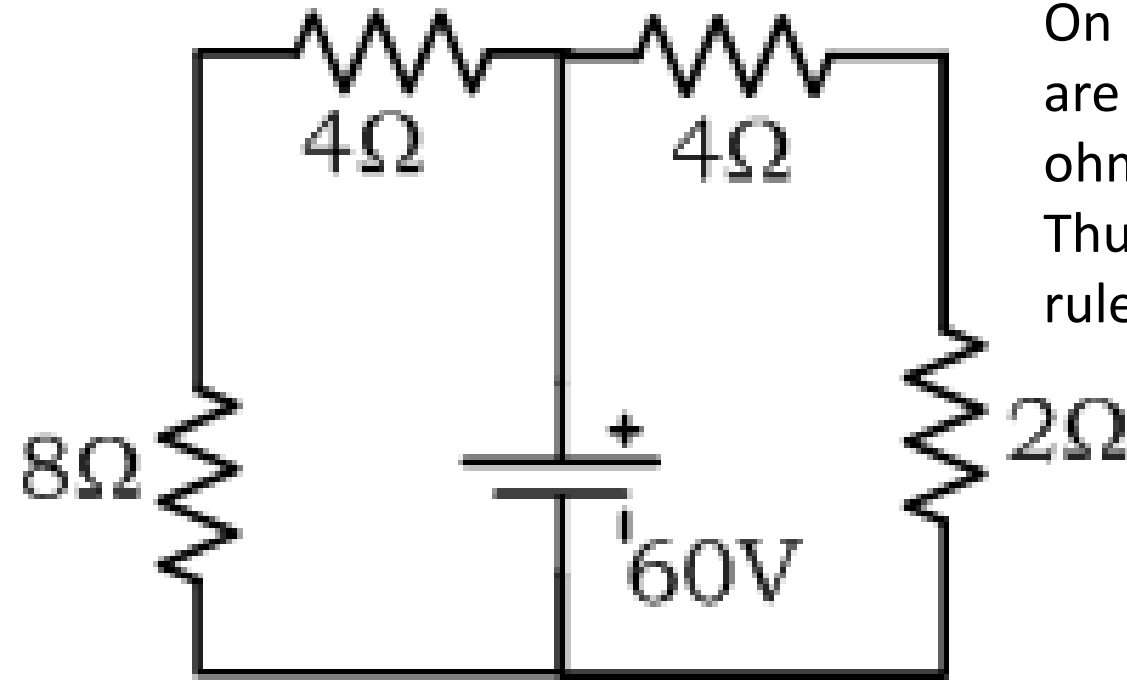

On left side branch:

$$V_{8\Omega} = 60 \times \frac{8}{8+4} = 40 \text{ V} \quad V_{4\Omega} = 60 \times \frac{4}{8+4} = 20 \text{ V}$$

On both sides of the circuit, there are series connections of 4 and 2 ohm resistances.

Thus, we can apply voltage division rule


$$V_1 = V \times \frac{R_1}{R_1 + R_2}$$

On right side branch:

$$V_{2\Omega} = 60 \times \frac{2}{2+4} = 20 \text{ V}$$

$$V_{4\Omega} = 60 \times \frac{4}{2+4} = 40 \text{ V}$$

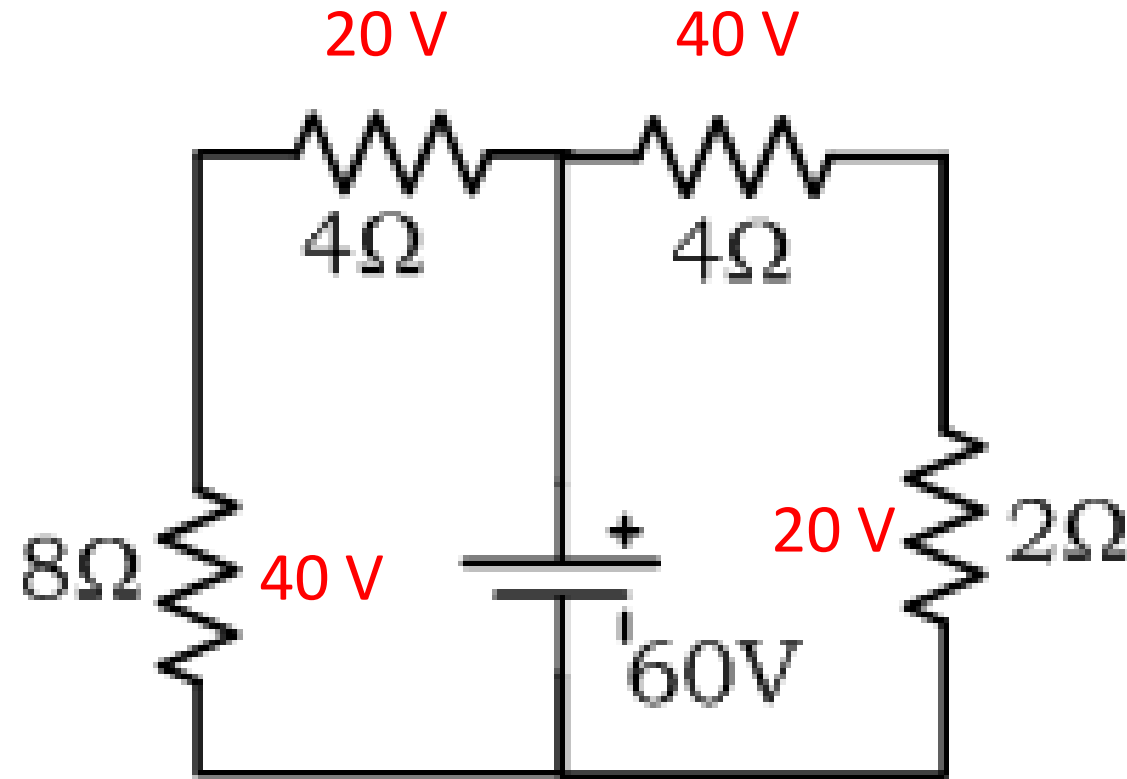In the circuit shown in figure , find the voltage across each element



On right side branch:

$$V_{2\Omega} = 60 \times \frac{2}{2+4} = 20V$$

$$V_{4\Omega} = 60 \times \frac{4}{2+4} = 40V$$

On left side branch:

$$V_{8\Omega} = 60 \times \frac{8}{8+4} = 40V$$

$$V_{4\Omega} = 60 \times \frac{4}{8+4} = 20V$$