

Chapter 6

Non-sinusoidal periodic waves

Day 40

Power in Harmonics
+ Tutorial 1

ILOs – Day 40

- Derive expressions for
 - Active power supplied by a complex wave
 - Power factor of a circuit with complex wave
- Solve numerical problems related to complex waves and harmonics

Power supplied by a complex wave

- For single frequency sinusoidal AC signals, the active power supplied is: $P = VI \cos \phi$
- Where, V and I are RMS values of voltage and current with ϕ being the phase angle between them
- But since complex waves contain signals of different frequencies, calculation of active power needs special attention
- Let the complex voltage wave applied to a circuit is given by:

$$e = E_{m1} \sin(\omega t + \phi_1) + E_{m2} \sin(2\omega t + \phi_2) + \dots + E_{mn} \sin(n\omega t + \phi_n) \dots$$

- The resulting current, which is also a complex waveform, has an equation such as:

$$i = I_{m1} \sin(\omega t + \psi_1) + I_{m2} \sin(2\omega t + \psi_2) + \dots + I_{mn} \sin(n\omega t + \psi_n) \dots$$

Power supplied by a complex wave

$$e = E_{m1} \sin(\omega t + \phi_1) + E_{m2} \sin(2\omega t + \phi_2) + \dots + E_{mn} \sin(n\omega t + \phi_n) \dots$$

$$i = I_{m1} \sin(\omega t + \psi_1) + I_{m2} \sin(2\omega t + \psi_2) + \dots + I_{mn} \sin(n\omega t + \psi_n) \dots$$

- The instantaneous value of the power in the circuit is $p = ei$ watt
- For obtaining the value of this product, we will have to multiply every term of the voltage wave, in turn, by every term in the current wave
- The average power supplied during a cycle:

$$P = \frac{1}{T} \int_0^T p dt = \frac{1}{T} \int_0^T e i dt$$

$$= \frac{1}{T} \int_0^T \left[\sum_x E_{mx} \sin(x\omega t + \phi_x) \right] \times \left[\sum_y I_{my} \sin(y\omega t + \psi_y) \right] dt$$

Power supplied by a complex wave

$$P = \frac{1}{T} \int_0^T \left[\sum_x E_{mx} \sin(x\omega t + \phi_x) \right] \times \left[\sum_x I_{mx} \sin(x\omega t + \psi_x) \right] dt$$

- When expanded, we get the following terms:
 - Product of two sine functions of different frequencies, for example the term:
 $E_{m1} \sin(\omega t + \phi_1) \times I_{m2} \sin(2\omega t + \psi_1)$
 - Product of two sine functions of same frequency, for example the term:
 $E_{m3} \sin(3\omega t + \phi_1) \times I_{m3} \sin(3\omega t + \psi_1)$
- We already have seen earlier that the average value of all product terms involving harmonics of different frequencies will be zero over one cycle
- So that we need consider only the products of current and voltage harmonics of the same frequency

Power supplied by a complex wave

$$E_{m3} \sin(3\omega t + \phi_1) \times I_{m3} \sin(3\omega t + \psi_1)$$

- Let us consider a general term of this nature i.e.

$$E_{mn} \sin(n\omega t + \phi_n) \times I_{mn} \sin(n\omega t + \psi_n)$$

- And find its average value over one cycle

$$\begin{aligned} P_n &= \frac{1}{T} \int_0^T E_{mn} \sin(n\omega t + \phi_n) \times I_{mn} \sin(n\omega t + \psi_n) dt \\ &= \frac{1}{T} \int_0^T E_{mn} \sin\left(n \frac{2\pi}{T} t + \phi_n\right) \times I_{mn} \sin\left(n \frac{2\pi}{T} t + \psi_n\right) dt \\ &= \frac{E_{mn} I_{mn}}{T} \int_0^T \frac{1}{2} \left[\cos(\phi_n - \psi_n) - \cos\left(\frac{4n\pi}{T} t + \phi_n + \psi_n\right) \right] dt \end{aligned}$$

Power supplied by a complex wave

$$= \frac{E_{mn} I_{mn}}{T} \int_0^T \frac{1}{2} \left[\cos(\phi_n - \psi_n) - \cos\left(\frac{4n\pi}{T}t + \phi_n + \psi_n\right) \right] dt$$

$$= \frac{E_{mn} I_{mn}}{T} \frac{1}{2} \left[\cos(\phi_n - \psi_n)t - \frac{T}{4n\pi} \sin\left(\frac{4n\pi}{T}t + \phi_n + \psi_n\right) \right]_0^T$$

$$= \frac{E_{mn} I_{mn}}{2T} [\cos(\phi_n - \psi_n)T - 0]$$

$$= \frac{E_{mn} I_{mn}}{2} \cos(\phi_n - \psi_n)$$

$$= \frac{E_{mn}}{\sqrt{2}} \frac{I_{mn}}{\sqrt{2}} \cos(\phi_n - \psi_n)$$

$$= E_n I_n \cos \theta_n$$

= Active power of the n^{th} harmonic component

Power supplied by a complex wave

Active power of the n^{th} harmonic component

$$P_n = \frac{E_{mn}}{\sqrt{2}} \frac{I_{mn}}{\sqrt{2}} \cos(\phi_n - \psi_n) = E_n I_n \cos \theta_n$$

Where, $E_n = \frac{E_{mn}}{\sqrt{2}}$ is RMS value of n^{th} voltage harmonic

$I_n = \frac{I_{mn}}{\sqrt{2}}$ is RMS value of n^{th} current harmonic

$\theta_n = (\phi_n - \psi_n)$ is the phase angle between n^{th} voltage and current harmonic waves

Thus, total active power, i.e. average power over one complete cycle due to all the harmonics taken together is:

$$P = \sum_i P_i = \sum_i E_i I_i \cos \theta_i = E_1 I_1 \cos \theta_1 + E_2 I_2 \cos \theta_2 + \dots + E_n I_n \cos \theta_n$$

Power supplied by a complex wave

$$P = \sum_i P_i = \sum_i E_i I_i \cos \theta_i = E_1 I_1 \cos \theta_1 + E_2 I_2 \cos \theta_2 + \dots + E_n I_n \cos \theta_n$$

- Hence, total average power supplied by a complex wave is the sum of the average power supplied by each harmonic component acting independently
- *No power results from voltages and currents of different frequencies*

Power factor of a complex wave

The overall power factor of the system is given by:

$$pf = \frac{\text{Total Watt}}{\text{Total apparent power}} = \frac{E_1 I_1 \cos \theta_1 + E_2 I_2 \cos \theta_2 + \dots + E_n I_n \cos \theta_n}{EI}$$

Where,

E = RMS value of the overall complex voltage wave

I = RMS value of the overall complex current wave

- *Note that when harmonics are present, the overall p.f. of the circuit cannot be stated lagging or leading*
- *It is simply the ratio of power in watts to volt-amperes*


Tutorial 1

#1) Draw one complete cycle of the following wave.


$$i = 100 \sin \omega t + 40 \sin 5\omega t$$

Determine the average value, the r.m.s. value and form factor of the wave.

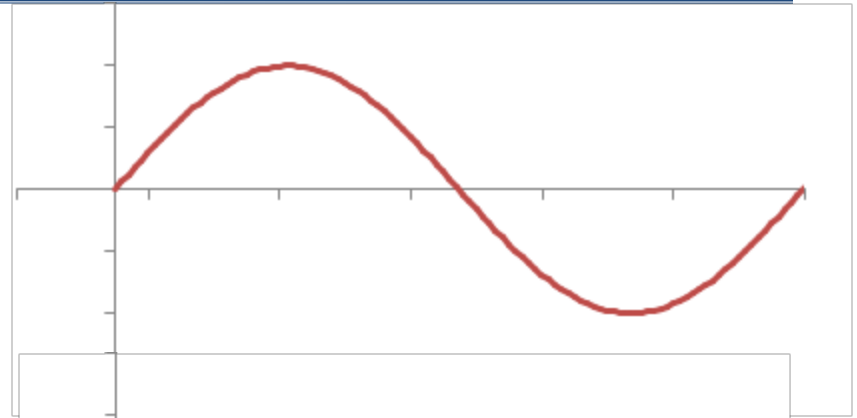
One complete cycle of the signal $i_1 = 100 \sin \omega t$, which we take as the fundamental, looks like:



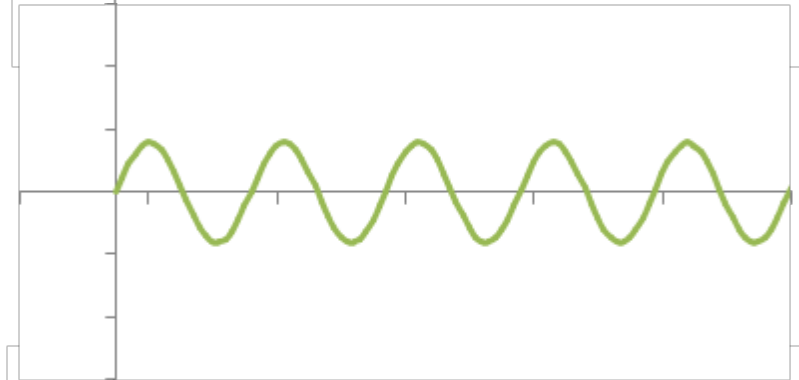One complete cycle of the signal $i_5 = 40 \sin 5\omega t$, which is the 5th harmonic signal, looks like:



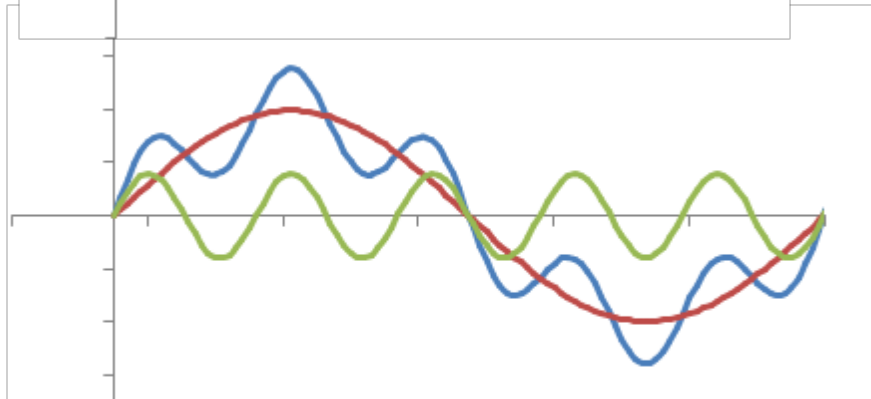Now the combined signal $i = 100 \sin \omega t + 40 \sin 5\omega t$ will look like:



#1) Draw one complete cycle of the following wave.

$$i = 100 \sin \omega t + 40 \sin 5\omega t$$

Determine the average value, the r.m.s. value and form factor of the wave.

Average value:

$$i_{av} = \frac{2}{\pi} \left(I_{m1} + \frac{I_{m5}}{5} \right) = \frac{2}{\pi} \left(100 + \frac{40}{5} \right) = 68.7 \text{ A}$$

RMS value:

$$I_{RMS} = \sqrt{\frac{I_{m1}^2}{2} + \frac{I_{m5}^2}{2}} = \sqrt{\frac{100^2}{2} + \frac{40^2}{2}} = 76.16 \text{ A}$$

$$\therefore \text{Form factor} = \frac{I_{RMS}}{i_{av}} = \frac{76.16}{68.7} = 1.109$$

#2) A single-phase voltage source 'e' is given by

$$e = 141 \sin \omega t + 42.3 \sin 3\omega t + 28.8 \sin 5\omega t$$

The corresponding current in the load circuit is given by

$$i = 16.5 \sin(\omega t + 54.5^\circ) + 8.43 \sin(3\omega t - 38^\circ) + 4.65 \sin(5\omega t - 34.3^\circ)$$

Find the power supplied by the source.

It is best to deal with each harmonic separately.

Power at fundamental,

$$P_1 = E_1 I_1 \cos \phi_1 = \frac{E_{m1}}{\sqrt{2}} \frac{I_{m1}}{\sqrt{2}} \cos \phi_1 = \frac{141}{\sqrt{2}} \times \frac{16.5}{\sqrt{2}} \cos(0^\circ - 54.5^\circ) = 675.5 \text{ W}$$

Power at 3rd harmonic,

$$P_3 = E_3 I_3 \cos \phi_3 = \frac{E_{m3}}{\sqrt{2}} \frac{I_{m3}}{\sqrt{2}} \cos \phi_3 = \frac{42.3}{\sqrt{2}} \times \frac{8.43}{\sqrt{2}} \cos(0^\circ + 38^\circ) = 140.5 \text{ W}$$

Power at 5th harmonic,

$$P_5 = E_5 I_5 \cos \phi_5 = \frac{E_{m5}}{\sqrt{2}} \frac{I_{m5}}{\sqrt{2}} \cos \phi_5 = \frac{28.8}{\sqrt{2}} \times \frac{4.65}{\sqrt{2}} \cos(0^\circ - 34.3^\circ) = 55.5 \text{ W}$$

#2) A single-phase voltage source 'e' is given by

$$e = 141 \sin \omega t + 42.3 \sin 3\omega t + 28.8 \sin 5\omega t$$

The corresponding current in the load circuit is given by

$$i = 16.5 \sin(\omega t + 54.5^\circ) + 8.43 \sin(3\omega t - 38^\circ) + 4.65 \sin(5\omega t - 34.3^\circ)$$

Find the power supplied by the source.

$$P_1 = 675.5 \text{ W}$$

$$P_3 = 140.5 \text{ W}$$

$$P_5 = 55.5 \text{ W}$$

$$\text{Total power supplied} = 675.5 + 140.5 + 55.5 = 871.5 \text{ W}$$

#3) A single-phase voltage source 'e' is given by

$$e = 50 + 50 \sin 5000t + 30 \sin 1000t$$

The corresponding current in the load circuit is given by

$$i = 11.2 \sin(5000t + 63.4^\circ) + 10.6 \sin(1000t + 45^\circ)$$

Find the power supplied by the source.

Power at DC, $P_0 = E_0 I_0 = 50 \times 0 = 0 \text{ W}$

Power at 5000 rad/s harmonic:

$$P_5 = E_5 I_5 \cos \phi_5 = \frac{E_{m5}}{\sqrt{2}} \frac{I_{m5}}{\sqrt{2}} \cos \phi_5 = \frac{50}{\sqrt{2}} \times \frac{11.2}{\sqrt{2}} \cos(0^\circ - 63.4^\circ) = 125.37 \text{ W}$$

Power at 1000 rad/s harmonic:

$$P_1 = E_1 I_1 \cos \phi_1 = \frac{E_{m1}}{\sqrt{2}} \frac{I_{m1}}{\sqrt{2}} \cos \phi_1 = \frac{30}{\sqrt{2}} \times \frac{10.6}{\sqrt{2}} \cos(0^\circ - 45^\circ) = 112.43 \text{ W}$$

$$\text{Total power supplied} = 0 + 125.37 + 112.43 = 237.8 \text{ W}$$

#4) A complex voltage is given by

$$e = 60 \sin \omega t + 24 \sin \left(3\omega t + \frac{\pi}{6} \right) + 12 \sin \left(5\omega t + \frac{\pi}{3} \right)$$

The corresponding current in the load circuit is given by

$$i = 0.6 \sin \left(\omega t - \frac{2\pi}{10} \right) + 0.12 \sin \left(3\omega t - \frac{2\pi}{24} \right) + 0.1 \sin \left(5\omega t + \frac{3\pi}{4} \right)$$

Find (i) r.m.s value of current and voltage (ii) total power supplied and (iii) the overall power factor.

RMS values of voltage components:

$$E_1 = \frac{E_{m1}}{\sqrt{2}} = \frac{60}{\sqrt{2}} = 42.43 \text{ V} \quad E_3 = \frac{E_{m3}}{\sqrt{2}} = \frac{24}{\sqrt{2}} = 16.97 \text{ V} \quad E_5 = \frac{E_{m5}}{\sqrt{2}} = \frac{12}{\sqrt{2}} = 8.49 \text{ V}$$

\therefore RMS value of total voltage,

$$E = \sqrt{E_1^2 + E_3^2 + E_5^2} = \sqrt{42.43^2 + 16.97^2 + 8.49^2} = 46.47 \text{ V}$$

#4) A complex voltage is given by

$$e = 60 \sin \omega t + 24 \sin \left(3\omega t + \frac{\pi}{6} \right) + 12 \sin \left(5\omega t + \frac{\pi}{3} \right)$$

The corresponding current in the load circuit is given by

$$i = 0.6 \sin \left(\omega t - \frac{2\pi}{10} \right) + 0.12 \sin \left(3\omega t - \frac{2\pi}{24} \right) + 0.1 \sin \left(5\omega t + \frac{3\pi}{4} \right)$$

Find (i) r.m.s value of current and voltage (ii) total power supplied and (iii) the overall power factor.

RMS values of current components:

$$I_1 = \frac{I_{m1}}{\sqrt{2}} = \frac{0.6}{\sqrt{2}} = 0.424 \text{ A} \quad I_3 = \frac{I_{m3}}{\sqrt{2}} = \frac{0.12}{\sqrt{2}} = 0.085 \text{ A} \quad I_5 = \frac{I_{m5}}{\sqrt{2}} = \frac{0.1}{\sqrt{2}} = 0.071 \text{ A}$$

\therefore RMS value of total current,

$$I = \sqrt{I_1^2 + I_3^2 + I_5^2} = \sqrt{0.424^2 + 0.085^2 + 0.071^2} = 0.438 \text{ A}$$

#4) A complex voltage is given by

$$e = 60 \sin \omega t + 24 \sin \left(3\omega t + \frac{\pi}{6} \right) + 12 \sin \left(5\omega t + \frac{\pi}{3} \right)$$

The corresponding current in the load circuit is given by

$$i = 0.6 \sin \left(\omega t - \frac{2\pi}{10} \right) + 0.12 \sin \left(3\omega t - \frac{2\pi}{24} \right) + 0.1 \sin \left(5\omega t + \frac{3\pi}{4} \right)$$

Find (i) r.m.s value of current and voltage (ii) total power supplied and (iii) the overall power factor.

Total power supplied:

$$\begin{aligned} P &= E_1 I_1 \cos \phi_1 + E_3 I_3 \cos \phi_3 + E_5 I_5 \cos \phi_5 \\ &= 42.43 \times 0.424 \times \cos \left(0 + \frac{2\pi}{10} \right) + 16.97 \times 0.085 \times \cos \left(\frac{\pi}{6} + \frac{2\pi}{24} \right) + 8.49 \times 0.071 \times \cos \left(\frac{\pi}{3} - \frac{3\pi}{4} \right) \\ &= 42.43 \times 0.424 \times \cos 36^\circ + 16.97 \times 0.085 \times \cos 45^\circ + 8.49 \times 0.071 \times \cos 75^\circ \\ &= 14.55 + 1.02 + 0.16 \\ &= 15.73 \text{ W} \end{aligned}$$

#4) A complex voltage is given by

$$e = 60 \sin \omega t + 24 \sin \left(3\omega t + \frac{\pi}{6} \right) + 12 \sin \left(5\omega t + \frac{\pi}{3} \right)$$

The corresponding current in the load circuit is given by

$$i = 0.6 \sin \left(\omega t - \frac{2\pi}{10} \right) + 0.12 \sin \left(3\omega t - \frac{2\pi}{24} \right) + 0.1 \sin \left(5\omega t + \frac{3\pi}{4} \right)$$

Find (i) r.m.s value of current and voltage (ii) total power supplied and (iii) the overall power factor.

Overall power factor:

$$pf = \frac{\text{Total Watt}}{\text{Total apparent power}} = \frac{15.73}{46.47 \times 0.438} = 0.773$$

#5) The following voltage is applied to a series circuit of resistance $20\ \Omega$ and inductance $0.05\ \text{H}$.

$$e = 250 \sin \omega t + 50 \sin \left(3\omega t + \frac{\pi}{3} \right) + 20 \sin \left(5\omega t + \frac{5\pi}{6} \right)$$

Derive (a) an expression for the current (b) the RMS value of voltage (c) the RMS value of current (d) the total power supplied (e) the power factor. Take $\omega=314\ \text{rad/s}$.

For fundamental:

Inductive reactance: $X_1 = \omega L = 314 \times 0.05 = 15.7\ \Omega$

Impedance: $Z_1 = 20 + j15.7 = 25.43 \angle 38.13^\circ\ \Omega$

For 3rd harmonic:

Inductive reactance: $X_3 = 3\omega L = 3 \times 314 \times 0.05 = 47.1\ \Omega$

Impedance: $Z_3 = 20 + j47.1 = 51.17 \angle 67^\circ\ \Omega$

#5) The following voltage is applied to a series circuit of resistance $20\ \Omega$ and inductance $0.05\ \text{H}$.

$$e = 250 \sin \omega t + 50 \sin \left(3\omega t + \frac{\pi}{3} \right) + 20 \sin \left(5\omega t + \frac{5\pi}{6} \right)$$

Derive (a) an expression for the current (b) the RMS value of voltage (c) the RMS value of current (d) the total power supplied (e) the power factor. Take $\omega=314\ \text{rad/s}$.

For 5th harmonic:

Inductive reactance: $X_5 = 5\omega L = 5 \times 314 \times 0.05 = 78.5\ \Omega$

Impedance: $Z_5 = 20 + j78.5 = 81 \angle 75.7^\circ\ \Omega$

#5) The following voltage is applied to a series circuit of resistance $20\ \Omega$ and inductance $0.05\ \text{H}$.

$$e = 250 \sin \omega t + 50 \sin \left(3\omega t + \frac{\pi}{3} \right) + 20 \sin \left(5\omega t + \frac{5\pi}{6} \right)$$

Derive (a) an expression for the current (b) the RMS value of voltage (c) the RMS value of current (d) the total power supplied (e) the power factor. Take $\omega=314\ \text{rad/s}$.

$$Z_1 = 25.43 \angle 38.13^\circ\ \Omega$$

$$Z_3 = 51.17 \angle 67^\circ\ \Omega$$

$$Z_5 = 81 \angle 75.7^\circ\ \Omega$$

(a) Expression for current is:

$$i = \frac{250}{25.43} \sin(\omega t - 38.1^\circ) + \frac{50}{51.17} \sin \left(3\omega t + \frac{\pi}{3} - 67^\circ \right) + \frac{20}{81} \sin \left(5\omega t + \frac{5\pi}{6} - 75.7^\circ \right)$$

$$\therefore i = 9.84 \sin(\omega t - 38.1^\circ) + 0.9 \sin(3\omega t - 7^\circ) + 0.25 \sin(5\omega t + 74.3^\circ)$$

#5) The following voltage is applied to a series circuit of resistance $20\ \Omega$ and inductance $0.05\ \text{H}$.

$$e = 250 \sin \omega t + 50 \sin \left(3\omega t + \frac{\pi}{3} \right) + 20 \sin \left(5\omega t + \frac{5\pi}{6} \right)$$

Derive (a) an expression for the current (b) the RMS value of voltage (c) the RMS value of current (d) the total power supplied (e) the power factor. Take $\omega=314\ \text{rad/s}$.

(b) RMS value of voltage:

$$\begin{aligned} V &= \sqrt{\frac{V_{m1}^2}{2} + \frac{V_{m3}^2}{2} + \frac{V_{m5}^2}{2}} \\ &= \sqrt{\frac{250^2}{2} + \frac{50^2}{2} + \frac{20^2}{2}} \\ &= 180.8\ \text{V} \end{aligned}$$

#5) The following voltage is applied to a series circuit of resistance $20\ \Omega$ and inductance $0.05\ \text{H}$.

$$e = 250 \sin \omega t + 50 \sin \left(3\omega t + \frac{\pi}{3} \right) + 20 \sin \left(5\omega t + \frac{5\pi}{6} \right)$$

Derive (a) an expression for the current (b) the RMS value of voltage (c) the RMS value of current (d) the total power supplied (e) the power factor. Take $\omega = 314\ \text{rad/s}$.

(b) RMS value of current:

$$i = 9.84 \sin(\omega t - 38.1^\circ) + 0.9 \sin(3\omega t - 7^\circ) + 0.25 \sin(5\omega t + 74.3^\circ)$$

$$\begin{aligned} I &= \sqrt{\frac{I_{m1}^2}{2} + \frac{I_{m3}^2}{2} + \frac{I_{m5}^2}{2}} \\ &= \sqrt{\frac{9.84^2}{2} + \frac{0.9^2}{2} + \frac{0.25^2}{2}} \\ &= 6.99\ \text{A} \end{aligned}$$

#5) The following voltage is applied to a series circuit of resistance $20\ \Omega$ and inductance $0.05\ \text{H}$.

$$e = 250 \sin \omega t + 50 \sin \left(3\omega t + \frac{\pi}{3} \right) + 20 \sin \left(5\omega t + \frac{5\pi}{6} \right)$$

Derive (a) an expression for the current (b) the RMS value of voltage (c) the RMS value of current (d) the total power supplied (e) the power factor. Take $\omega=314\ \text{rad/s}$.

$$V = 180.8\ \text{V} \quad I = 6.99\ \text{A}$$

(d) Total power supplied:

$$P = I^2 R = 6.99^2 \times 20 = 978\ \text{W}$$

You can check the result by alternate method of power calculation

#5) The following voltage is applied to a series circuit of resistance $20\ \Omega$ and inductance $0.05\ \text{H}$.

$$e = 250 \sin \omega t + 50 \sin \left(3\omega t + \frac{\pi}{3} \right) + 20 \sin \left(5\omega t + \frac{5\pi}{6} \right)$$

Derive (a) an expression for the current (b) the RMS value of voltage (c) the RMS value of current (d) the total power supplied (e) the power factor. Take $\omega = 314\ \text{rad/s}$.

$$V = 180.8\ \text{V} \qquad I = 6.99\ \text{A} \qquad P = 978\ \text{W}$$

(e) Power factor:

$$pf = \frac{\text{Active power}}{\text{Apparent power}} = \frac{\text{Watt}}{VI} = \frac{978}{180.8 \times 6.99} = 0.773$$