

3-Phase systems

Day 28

Unbalanced 3-phase systems
Tutorial 1

ILOs – Day 28

- Define and characterize unbalanced 3-phase systems
- Calculate for an unbalanced 3-phase system
 - Phase currents
 - Line currents
 - Apparent power
 - Active power
 - Reactive power
 - Power factor


Unbalanced 3-phase system

- A 3-phase system is said to be unbalanced when:
 - The three voltages are unbalanced
 - Magnitudes may be different
 - Phase angle difference may not be 120°
 - The three currents are unbalanced
 - Magnitudes may be different
 - Phase angle difference may not be 120°
- By definition, an unbalanced circuit has at least one phase current that is not equal to the other phase currents
- Of course, all three phase currents could be of unequal magnitude
- Such unbalances may be in the
 - Supply system
 - Load
- Unbalances may be due to
 - Naturally occurring unbalances in load
 - Faults and disturbances in the power system

Unbalanced 3-phase system

Let us analyze such an unbalanced system using an example

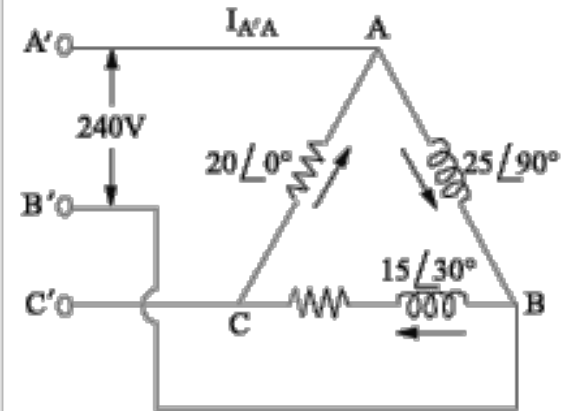A 3-phase, 3-wire, 240 volt, CBA system supplies a delta-connected load in which $Z_{AB} = 25 \angle 90^\circ$, $Z_{BC} = 15 \angle 30^\circ$, $Z_{CA} = 20 \angle 0^\circ$ ohms. Find the line currents and total power.



In C-B-A phase sequence (which can be written as C-B-A-C-B-A), if we take V_{AB} as the reference, then V_{CA} lags behind V_{AB} by 120° , and V_{BC} lags behind V_{AB} by 240° .

Thus, $V_{AB} = V \angle 0^\circ$, $V_{CA} = V \angle -120^\circ$, $V_{BC} = V \angle -240^\circ = V \angle +120^\circ$

The phase currents are calculated as:

$$I_{AB} = \frac{V_{AB}}{Z_{AB}} = \frac{240 \angle 0^\circ}{25 \angle 90^\circ} = 9.6 \angle -90^\circ = 0 - j9 \text{ A}$$


$$I_{BC} = \frac{V_{BC}}{Z_{BC}} = \frac{240 \angle 120^\circ}{15 \angle 30^\circ} = 16 \angle 90^\circ = 0 + j16 \text{ A}$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}} = \frac{240 \angle -120^\circ}{20 \angle 0^\circ} = 12 \angle -120^\circ = -6 - j10.4 \text{ A}$$

Unbalanced 3-phase system


Let us analyze such an unbalanced system using an example

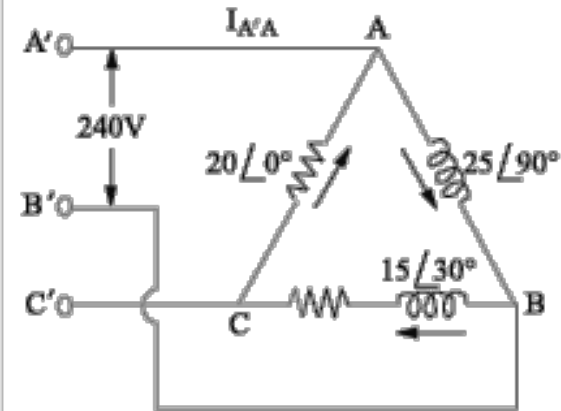A 3-phase, 3-wire, 240 volt, CBA system supplies a delta-connected load in which $Z_{AB} = 25 \angle 90^\circ$, $Z_{BC} = 15 \angle 30^\circ$, $Z_{CA} = 20 \angle 0^\circ$ ohms. Find the line currents and total power.



$$V_{AB} = V \angle 0^\circ, V_{CA} = V \angle -120^\circ, V_{BC} = V \angle +120^\circ$$


$$I_{AB} = 9.6 \angle -90^\circ, I_{BC} = 16 \angle 90^\circ, I_{CA} = 12 \angle -120^\circ$$

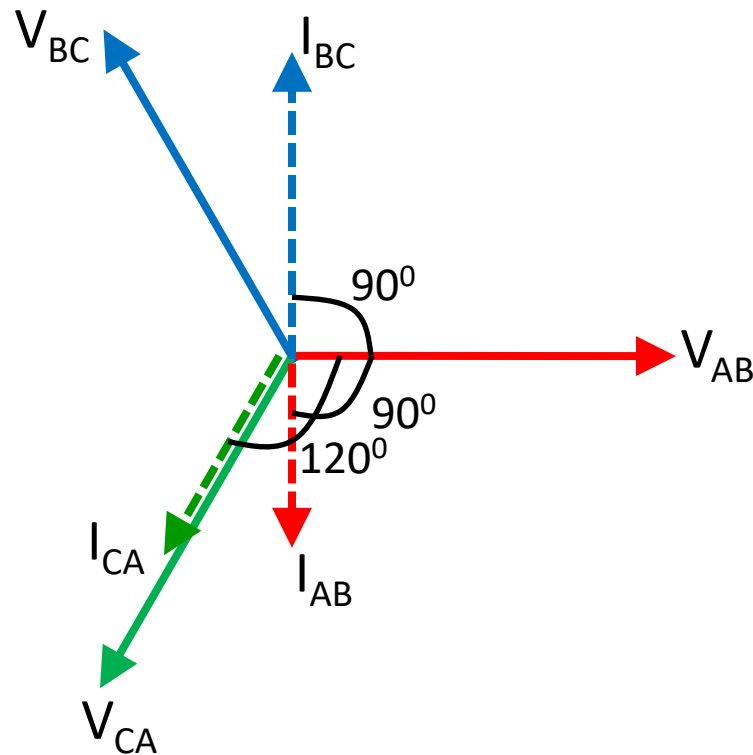

Unbalanced 3-phase system

Let us analyze such an unbalanced system using an example

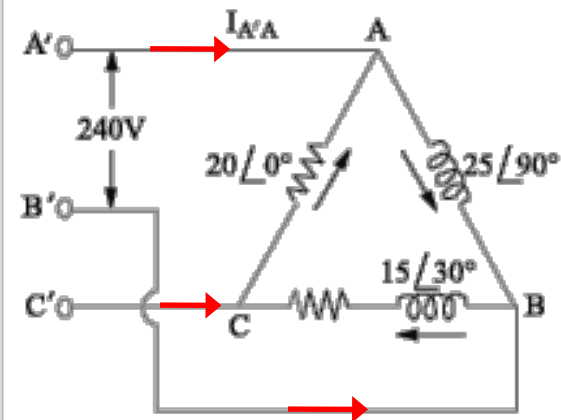A 3-phase, 3-wire, 240 volt, CBA system supplies a delta-connected load in which $Z_{AB} = 25 \angle 90^\circ$, $Z_{BC} = 15 \angle 30^\circ$, $Z_{CA} = 20 \angle 0^\circ$ ohms. Find the line currents and total power.



$$I_{AB} = -j9.6 \text{ A} \quad I_{BC} = j16 \text{ A} \quad I_{CA} = -6 - j10.4 \text{ A}$$

The LINE currents are hence calculated as:

$$I_{A'A} = I_{AB} - I_{CA} = -j9.6 - (-6 - j10.4) = 6 + j0.8 \text{ A}$$

$$I_{B'B} = I_{BC} - I_{AB} = j16 - (-j9.6) = j25.6 \text{ A}$$

$$I_{C'C} = I_{CA} - I_{BC} = (-6 - j10.4) - j16 = -6 - j26.4 \text{ A}$$

Total active power is the summation of active powers in three phases:

$$V_{AB} = 240 \angle 0^\circ, I_{AB} = 9.6 \angle -90^\circ \Rightarrow P_{AB} = V_{AB} I_{AB} \cos(\angle \theta_{AB}) = 240 \times 9.6 \times \cos(\angle 0^\circ + 90^\circ) = 2304 \cos(90^\circ) = 0$$

$$\begin{aligned} V_{BC} = 240 \angle 120^\circ, I_{BC} = 16 \angle 90^\circ &\Rightarrow P_{BC} = V_{BC} I_{BC} \cos(\angle \theta_{BC}) \\ &= 240 \times 16 \times \cos(\angle 120^\circ - 90^\circ) = 3840 \cos(30^\circ) = 3326 \text{ W} \end{aligned}$$


$$\begin{aligned} V_{CA} = 240 \angle -120^\circ, I_{CA} = 12 \angle -120^\circ &\Rightarrow P_{CA} = V_{CA} I_{CA} \cos(\angle \theta_{CA}) \\ &= 240 \times 12 \times \cos(\angle -120^\circ + 120^\circ) = 2880 \cos(0^\circ) = 2880 \text{ W} \end{aligned}$$

$$\Rightarrow P = P_{AB} + P_{BC} + P_{CA} = 0 + 3326 + 2880 = 6206 \text{ W}$$

Unbalanced 3-phase system

Let us analyze such an unbalanced system using an example

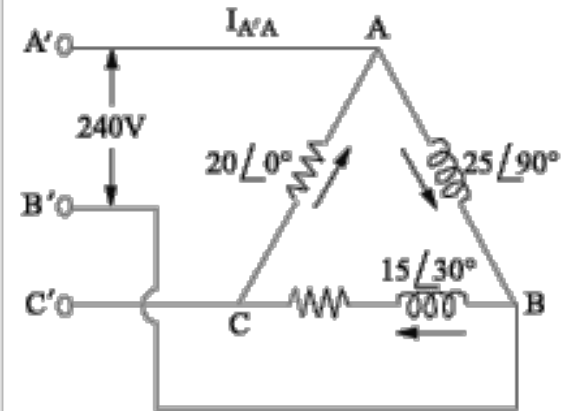A 3-phase, 3-wire, 240 volt, CBA system supplies a delta-connected load in which $Z_{AB} = 25 \angle 90^\circ$, $Z_{BC} = 15 \angle 30^\circ$, $Z_{CA} = 20 \angle 0^\circ$ ohms. Find the line currents and total power.



$$V_{AB} = V \angle 0^\circ, V_{CA} = V \angle -120^\circ, V_{BC} = V \angle +120^\circ$$

$$I_{AB} = 9.6 \angle -90^\circ, I_{BC} = 16 \angle 90^\circ, I_{CA} = 12 \angle -120^\circ$$

In case we are interested in finding out:

- Apparent power
- Reactive power
- Power factor

$$V_{AB} = 240 \angle 0^\circ = 240 + j0, V_{BC} = 240 \angle 120^\circ = -120 + j207.8, V_{CA} = 240 \angle -120^\circ = -120 - j207.8$$

$$I_{AB} = -j9.6$$

$$I_{BC} = j16$$

$$I_{CA} = -6 - j10.4$$


- As we are working with an unbalanced circuit we must calculate the power for each phase
- So let's calculate the apparent power for each phase in the complex form
- Apparent power in complex form is calculated by the product between the voltage and the **conjugate complex** of the current, i.e. $S = V \times I^*$

Conjugate is used to get the phase **difference** between voltage and current while calculating S , otherwise simple $V \times I$ would have added up their phase angles rather than taking their difference

Unbalanced 3-phase system

Let us analyze such an unbalanced system using an example

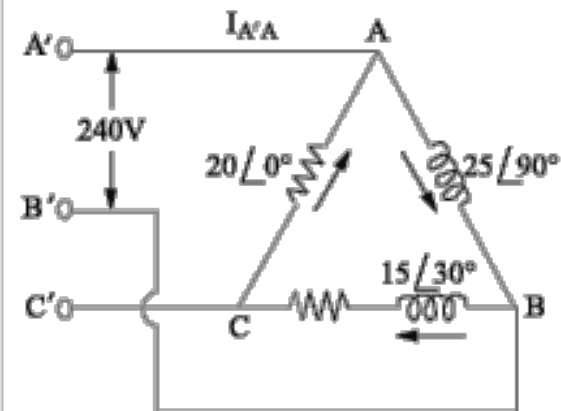A 3-phase, 3-wire, 240 volt, CBA system supplies a delta-connected load in which $Z_{AB} = 25 \angle 90^\circ$, $Z_{BC} = 15 \angle 30^\circ$, $Z_{CA} = 20 \angle 0^\circ$ ohms. Find the line currents and total power.



$$V_{AB} = 240 + j0, V_{BC} = -120 + j207.8, V_{CA} = -120 - j207.8$$

$$I_{AB} = -j9.6 \quad I_{BC} = j16 \quad I_{CA} = -6 - j10.4$$

Apparent power in complex form:

$$S_{AB} = V_{AB} \times I_{AB}^* = (240 + j0) \times (j9.6) = j2304$$

$$S_{BC} = V_{BC} \times I_{BC}^* = (-120 + j207.8) \times (-j16) = 3324.8 + j1920$$

$$S_{CA} = V_{CA} \times I_{CA}^* = (-120 - j207.8) \times (-6 + j10.4) = 2880 + j0$$

Total apparent power in complex form:

$$S = S_{AB} + S_{BC} + S_{CA} = j2304 + 3324.8 + j1920 + 2880 = 6204.8 + j4224$$

Total active power = real part of the complex apparent power: $P = \text{Re}(S) = 6204.8 \text{ W}$

Total reactive power = imaginary part of the complex apparent power: $Q = \text{Im}(S) = 4224 \text{ VAR}$

Total apparent power: $S = \sqrt{P^2 + Q^2} = \sqrt{6204.8^2 + 4224^2} = 7506 \text{ VA}$

Overall power factor: $\cos \theta = \frac{P}{S} = \frac{6204.8}{7506} = 0.826 \text{ (lag)}$

Unbalanced 3-phase system


Let us solve another example to make things clearer:

Let us have a circuit with load in the configuration delta, with the following values of voltage and impedances:

$$V_{AB} = 300\angle 30^\circ, \quad V_{BC} = 200\angle -60^\circ, \quad V_{CA} = 150\angle 150^\circ,$$
$$Z_{AB} = 10\angle 30^\circ, \quad Z_{BC} = 10\angle 45^\circ \quad \text{and} \quad Z_{CA} = 15\angle -70^\circ.$$

a) Calculate the phase and line currents.

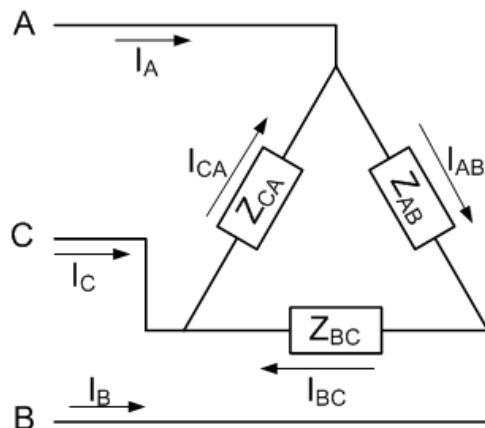b) Calculate the total apparent, real and reactive power and average power factor



a) The phase currents are calculated as:

$$I_{AB} = \frac{V_{AB}}{Z_{AB}} = \frac{300\angle 30^\circ}{10\angle 30^\circ} = 30\angle 0^\circ = 30 + j0 \text{ A}$$

$$I_{BC} = \frac{V_{BC}}{Z_{BC}} = \frac{200\angle -60^\circ}{10\angle 45^\circ} = 20\angle -105^\circ = -5.2 - j19.3 \text{ A}$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}} = \frac{150\angle 150^\circ}{15\angle -70^\circ} = 10\angle 220^\circ = -7.7 - j6.4 \text{ A}$$

The LINE currents are hence calculated as:

$$I_A = I_{AB} - I_{CA} = 30 + j0 - (-7.7 - j6.4) = 37.7 + j6.4 \text{ A} = 38.2\angle 9.6^\circ \text{ A}$$

$$I_B = I_{BC} - I_{AB} = -5.2 - j19.3 - (30 + j0) = -35.2 - j19.3 \text{ A} = 40.1\angle 208.7^\circ \text{ A}$$

$$I_C = I_{CA} - I_{BC} = (-7.7 - j6.4) - (-5.2 - j19.3) = -2.5 + j12.9 \text{ A} = 13.1\angle 101^\circ \text{ A}$$

Unbalanced 3-phase system


Let us solve another example to make things clearer:

Let us have a circuit with load in the configuration delta, with the following values of voltage and impedances:

$$V_{AB} = 300\angle 30^\circ, \quad V_{BC} = 200\angle -60^\circ, \quad V_{CA} = 150\angle 150^\circ, \\ Z_{AB} = 10\angle 30^\circ, \quad Z_{BC} = 10\angle 45^\circ \quad \text{and} \quad Z_{CA} = 15\angle -70^\circ.$$

a) Calculate the phase and line currents.

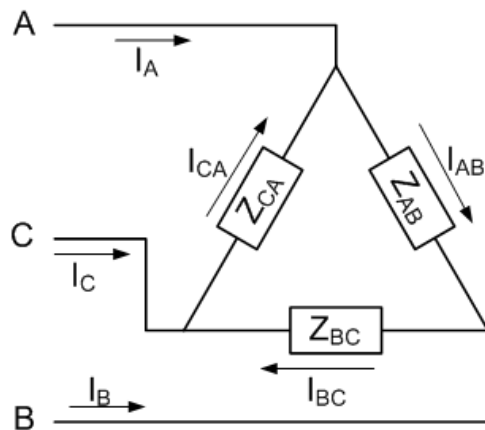b) Calculate the total apparent, real and reactive power and average power factor



b) Apparent power in complex form:

$$S_{AB} = V_{AB} \times I_{AB}^* = 300\angle 30^\circ \times 30\angle -0^\circ = 9000\angle 30^\circ = 7794.2 + j4500 \text{ VA}$$

$$S_{BC} = V_{BC} \times I_{BC}^* = 200\angle -60^\circ \times 20\angle +105^\circ = 4000\angle 45^\circ \\ = 2828.4 + j2828.4 \text{ VA}$$

$$S_{CA} = V_{CA} \times I_{CA}^* = 150\angle 150^\circ \times 10\angle -220^\circ = 1500\angle -70^\circ \\ = 513 - j1409.5 \text{ VA}$$

Total apparent power in complex form:

$$S = S_{AB} + S_{BC} + S_{CA} = 7794.2 + j4500 + 2828.4 + j2828.4 + 513 - j1409.5 \\ = 11135.6 + j5919.4 = 12611.1\angle 28^\circ \text{ VA}$$

Unbalanced 3-phase system


Let us solve another example to make things clearer:

Let us have a circuit with load in the configuration delta, with the following values of voltage and impedances:

$$V_{AB} = 300\angle 30^\circ, \quad V_{BC} = 200\angle -60^\circ, \quad V_{CA} = 150\angle 150^\circ,$$
$$Z_{AB} = 10\angle 30^\circ, \quad Z_{BC} = 10\angle 45^\circ \quad \text{and} \quad Z_{CA} = 15\angle -70^\circ.$$

a) Calculate the phase and line currents.

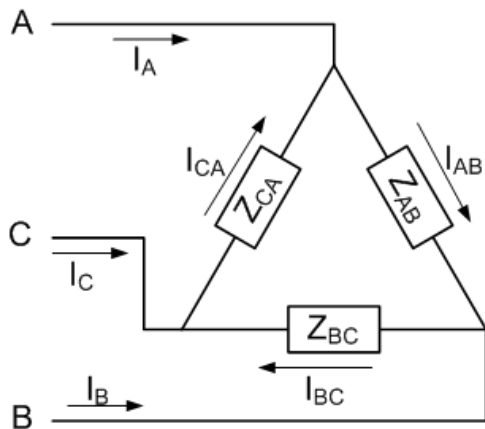b) Calculate the total apparent, real and reactive power and average power factor



Total apparent power in complex form:

$$S = 11135.6 + j5919.4 = 12611.1\angle 28^\circ \text{ VA}$$

Total active power = real part of the complex apparent power:

$$P = \text{Re}(S) = 11135.6 \text{ W}$$

Total reactive power = imaginary part of the complex apparent power:

$$Q = \text{Im}(S) = 5919.4 \text{ VAR}$$

$$\text{Total apparent power: } S = \sqrt{P^2 + Q^2} = \sqrt{11135.6^2 + 5919.4^2} = 12611.1 \text{ VA}$$

$$\text{Overall power factor: } \cos \theta = \frac{P}{S} = \frac{11135.6}{12611.1} = 0.88 \text{ (lag)}$$